

PHYSICAL COMPUTING 3: SENSORS

CSE 590 Ubiquitous Computing | Lecture 6 | May 3

Jon Froehlich • Liang He (TA)

SCHEDULE TODAY: 6:30-9:20

06:30-06:55: Discussion of required reading led by Joe Wandyez

06:55-07:00: Optional discussion led by Abhay Rijhwani ([link](#))

07:00-08:10: Physical Computing 3: Sensors

08:10-08:15: Break

08:15-09:20: Physical Computing 4: Android + Arduino via BLE

SCHEDULE TODAY: 6:30-9:20

06:30-06:55: Discussion of required reading led by Joe Wandyez

06:55-07:00: Optional discussion led by Abhay Rijhwani ([link](#))

07:00-08:10: Physical Computing 3: Sensors

08:10-08:15: Break

08:15-09:20: Physical Computing 4: Android + Arduino via BLE

SCHEDULE TODAY: 6:30-9:20

06:30-06:55: Discussion of required reading led by Joe Wandyez

06:55-07:00: Optional discussion led by Abhay Rijhwani ([link](#))

07:00-08:10: Physical Computing 3: Sensors

08:10-08:15: Break

08:15-09:20: Physical Computing 4: Android + Arduino via BLE

WORKING WITH SENSORS: LEARNING GOALS

How to use variable **resistive sensors**, including **voltage dividers**,
basic **signal smoothing**

Putting it together: **making a simple theremin**

How to use **buttons**, including **pull-up** and **pull-down resistors**,
and **debouncing**

Working with **interrupts**

VARIABLE RESISTORS


LOTS OF DIFFERENT KINDS OF VARIABLE RESISTORS



Potentiometer 10k; \$0.95*



Touch Membrane
Potentiometer; \$12.95

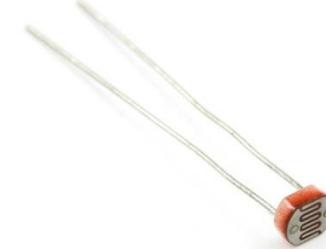

Photocell (aka photodetector
or photo resistor); \$1.50



Thermistor 10k; \$0.75




Force Resistive Sensor
0.5"; \$6.95



Flex Sensor 4.5"; \$12.95


VARIABLE RESISTORS

PHOTOCELL DEMONSTRATION

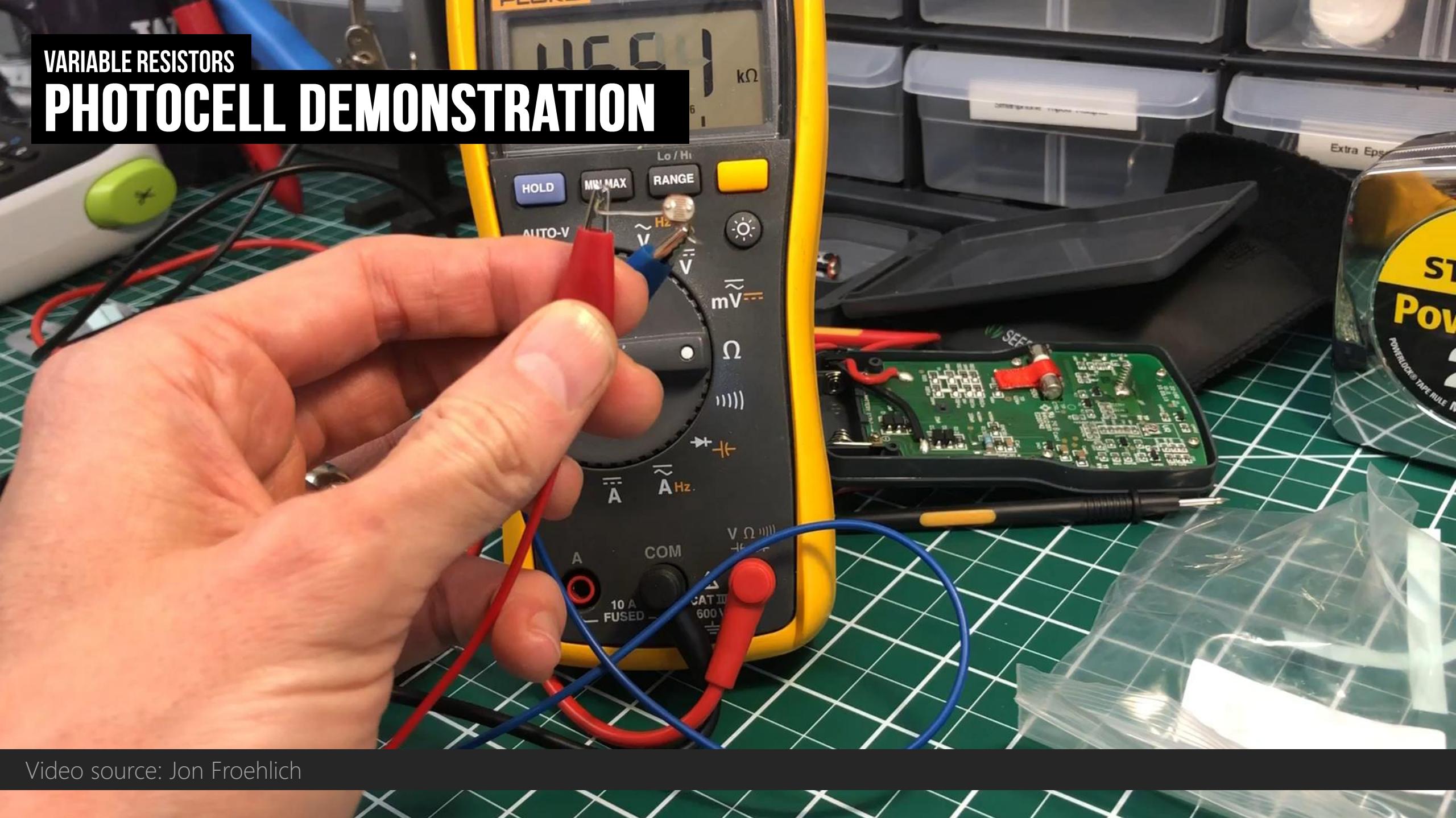


Video source: Jon Froehlich

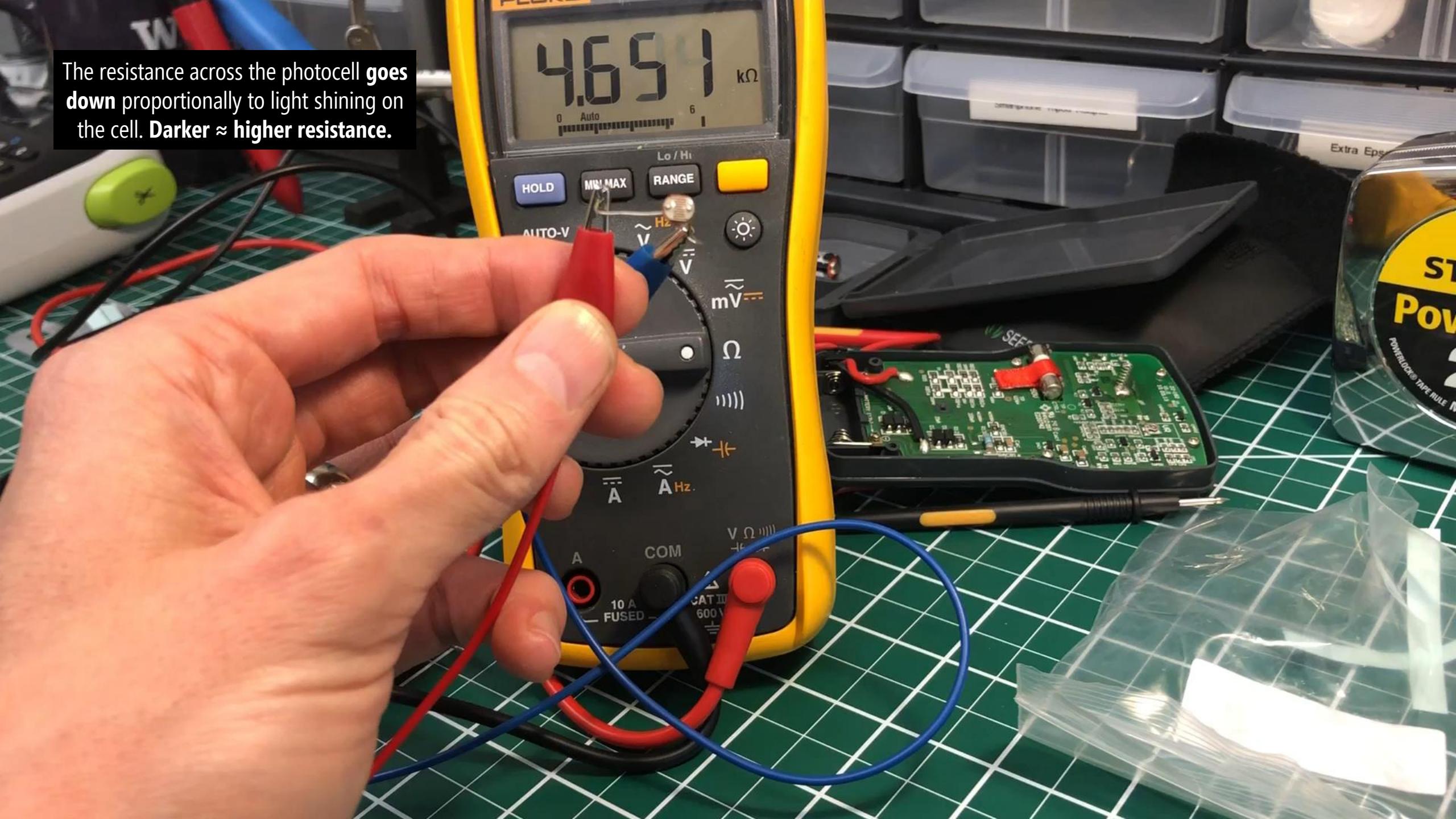The resistance across the photocell **goes down** proportionally to light shining on the cell. **Darker \approx higher resistance.**



VARIABLE RESISTORS

FORCE RESISTIVE SENSOR DEMONSTRATION

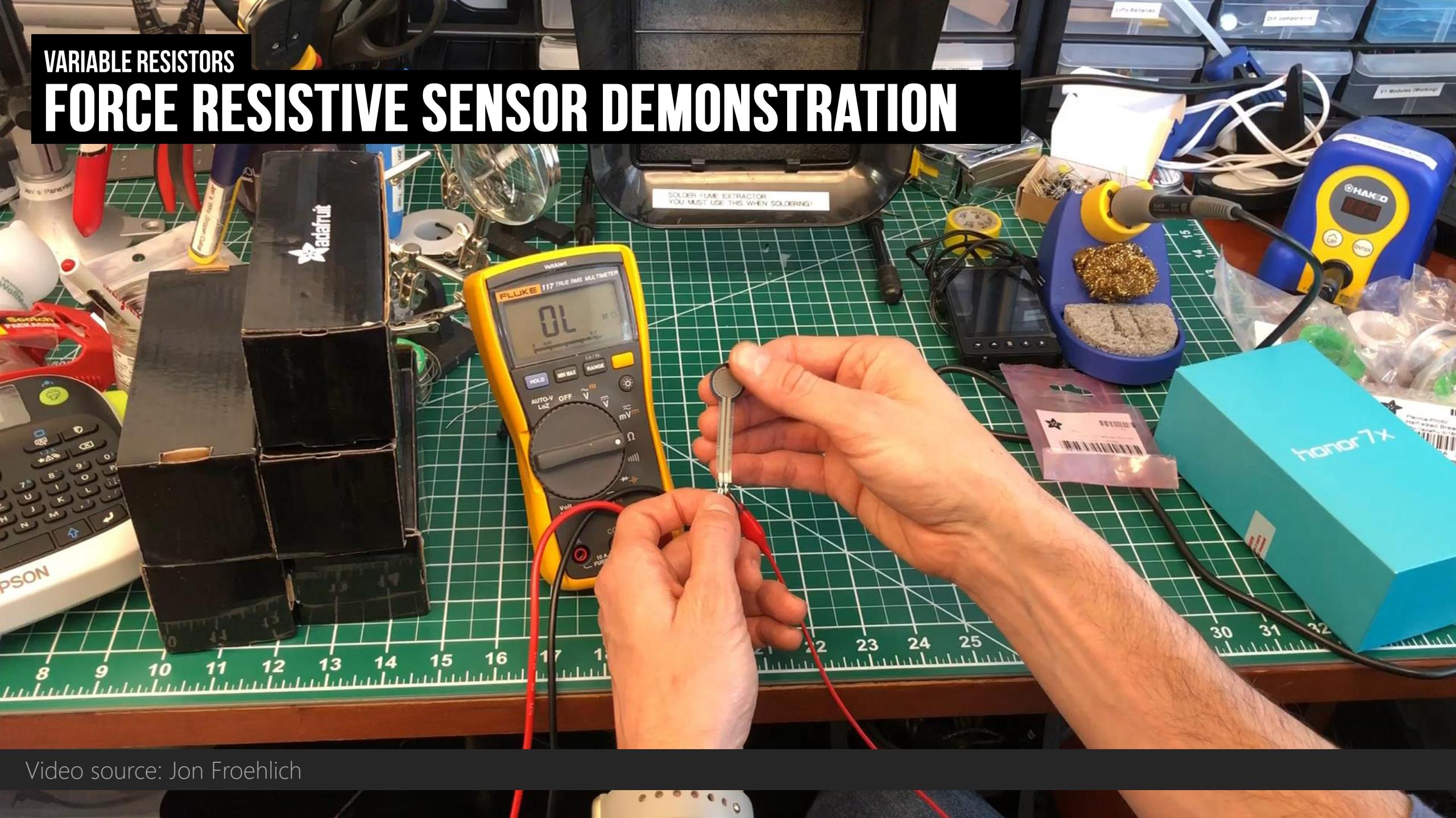

Video source: Jon Froehlich

The resistance across the pressure sensor
goes down proportionally to pressure.
High pressure \approx low resistance.





Awesome! Let's wire up a **photocell**.


USING A VARIABLE RESISTIVE SENSOR

WIRE UP A PHOTOCELL & PRINT VALUE & VOLTAGE

Circuit: Read a photocell

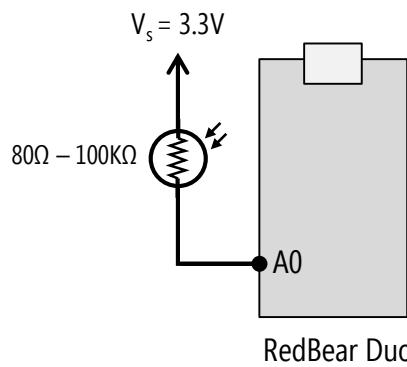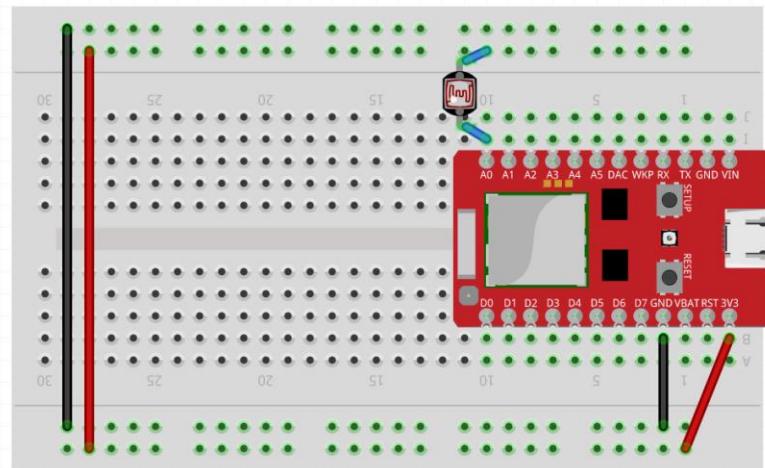


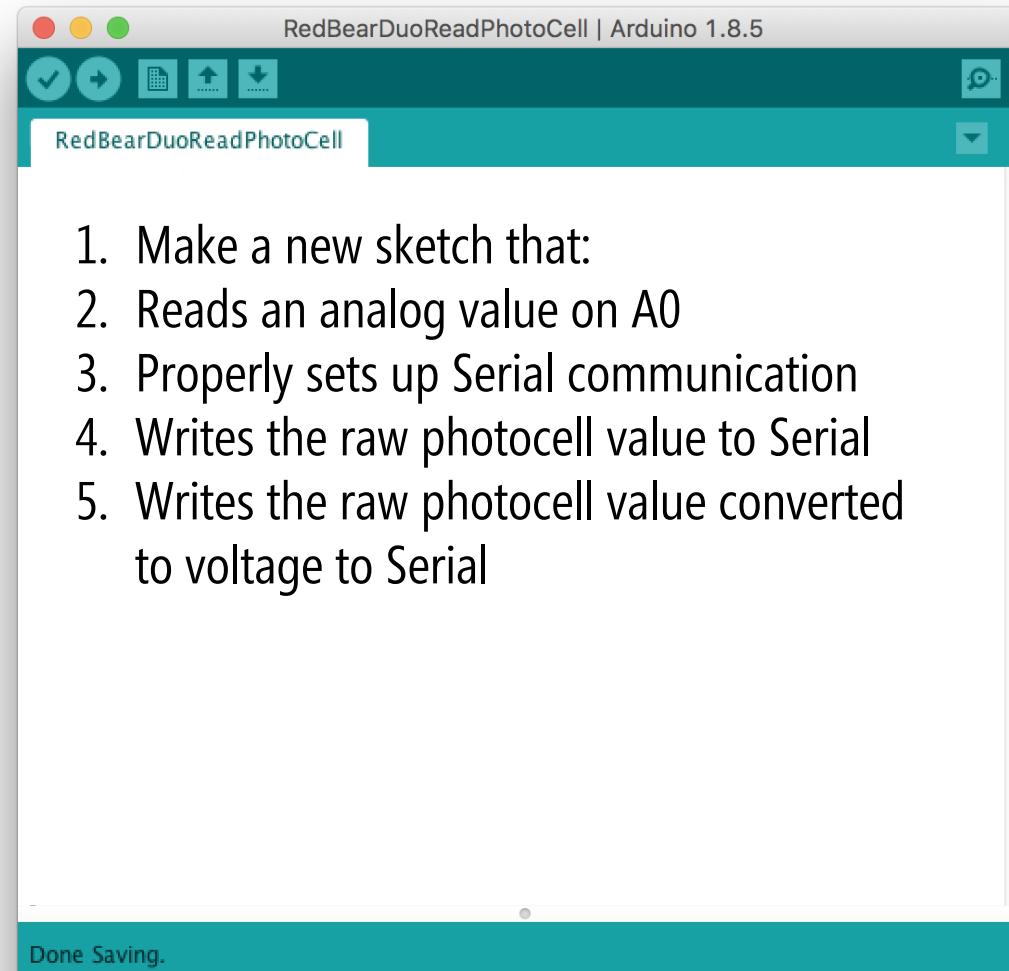
Code: Read a photocell value and print to serial



USING A VARIABLE RESISTIVE SENSOR

WIRE UP A PHOTOCELL & PRINT VALUE & VOLTAGE

Circuit: Read a photocell

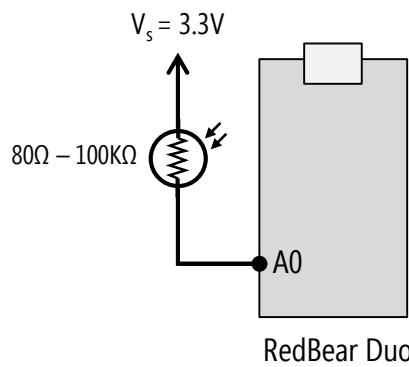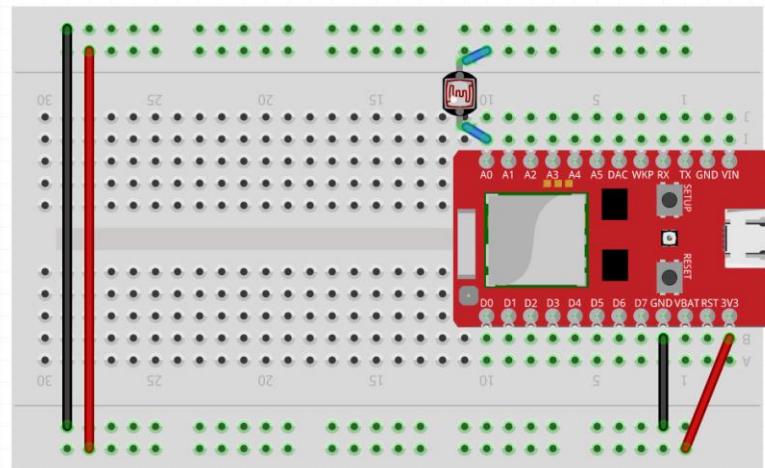

Code: Read a photocell value and print to serial

```
RedBearDuoReadPhotoCell | Arduino 1.8.5

SYSTEM_MODE(MANUAL); // required to use RedBear Duo

const int PHOTOCELL_INPUT_PIN = A0;
const int MAX_ADC_VALUE = 4096; // 12-bit ADC
const float MAX_VOLTAGE = 3.3;

void setup() {
    pinMode(PHOTOCELL_INPUT_PIN, INPUT);
    pinMode(D0, OUTPUT);
    Serial.begin(9600);
}

void loop() {
    // Read the photocell value (which will range from 0 to 4096)
    int photocellVal = analogRead(PHOTOCELL_INPUT_PIN);

    // Convert to a voltage
    float inputVoltage = MAX_VOLTAGE * photocellVal / MAX_ADC_VALUE;


    // Print to serial
    Serial.print(photocellVal);
    Serial.print("\t");
    Serial.println(inputVoltage);
    delay(100);
}
```

Done Saving.

USING A VARIABLE RESISTIVE SENSOR

WIRE UP A PHOTOCELL & PRINT VALUE & VOLTAGE

Circuit: Read a photocell

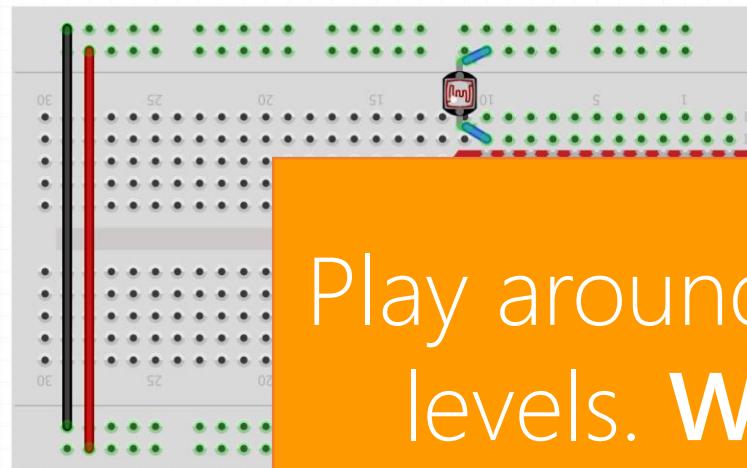


Code: Read a photocell value and print to serial

```
// Read the photocell value (which will range from 0 to 4096)
int photocellVal = analogRead(PHOTOCELL_INPUT_PIN);

// Convert to a voltage
float inputVoltage = MAX_VOLTAGE * photocellVal / MAX_ADC_VALUE;

// Print to serial
Serial.print(photocellVal);
Serial.print("\t");
Serial.println(inputVoltage);
delay(100);
}



Done Saving.
```

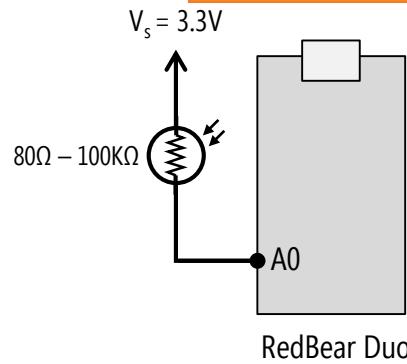


USING A VARIABLE RESISTIVE SENSOR

WIRE UP A PHOTOCELL & PRINT VALUE & VOLTAGE

Circuit: Read a photocell

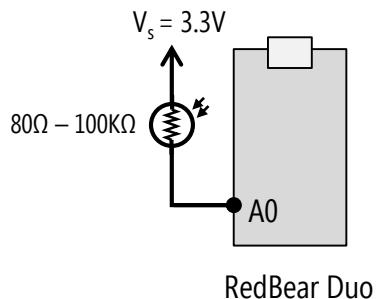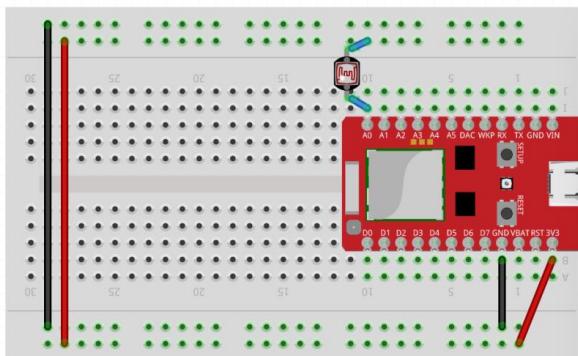

Code: Read a photocell & print to serial

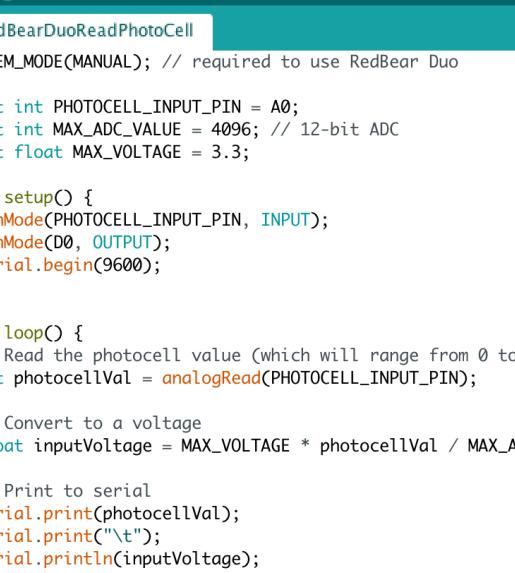

The screenshot shows the Arduino IDE interface with the following details:

- Title Bar:** RedBearDuoReadPhotoCell | Arduino 1.8.5
- Toolbar:** Standard Arduino toolbar with icons for file operations (New, Open, Save, Save As, Print, Import, Export) and project management.
- Code Area:** The main code editor contains the following sketch:

```
RedBearDuoReadPhotoCell
SYSTEM_MODE(MANUAL); // required to use RedBear Duo

const int PHOTOCELL_INPUT_PIN = A0;
const int MAX_ADC_VALUE = 4096; // 12-bit ADC
const float MAX_VOLTAGE = 3.3;

void setup() {
  pinMode(PHOTOCELL_INPUT_PIN, INPUT);
  pinMode(D0, OUTPUT);
  Serial.begin(9600);
}

void loop() {
  // Read the photocell value (which will range from 0 to 4096)
  int photocellVal = analogRead(PHOTOCELL_INPUT_PIN);

  // Convert to a voltage
  float inputVoltage = MAX_VOLTAGE * photocellVal / MAX_ADC_VALUE;

  // Print to serial
  Serial.print(photocellVal);
  Serial.print("\t");
  Serial.println(inputVoltage);
  delay(100);
}
```
- Status Bar:** Done Saving.

Output: analogRead val and voltage


Hmm, the values seem to be **stuck** at ~**4096** (or 3.3V). Why is this?

40931	3.3
4093	3.3
4092	3.3
4092	3.3
4092	3.3
4093	3.3
4092	3.3
4091	3.3
4092	3.3
4092	3.3
4090	3.3
4092	3.3
4091	3.3
4092	3.3
4093	3.3
4090	3.3
4091	3.3
4089	3.2
4091	3.3
4093	3.3
4092	3.3
4093	3.3
4092	3.3
4092	3.3
4093	3.3

No line ending 9600 baud Clear output

USING A VARIABLE RESISTIVE SENSOR


WHY DOESN'T THIS CIRCUIT WORK?

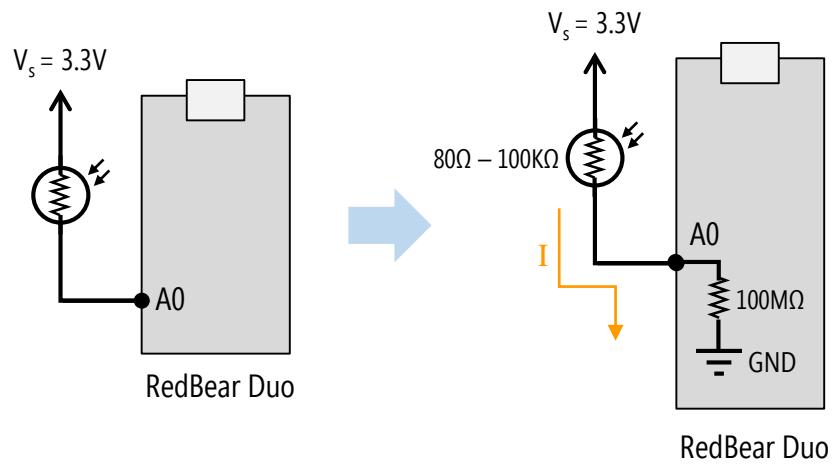

Microcontroller **input pins** have incredibly **high input resistance** (effectively infinite). In fact, you can assume that very little current flows in or out of an input pin.

USING A VARIABLE RESISTIVE SENSOR

WHY DOESN'T THIS CIRCUIT WORK?

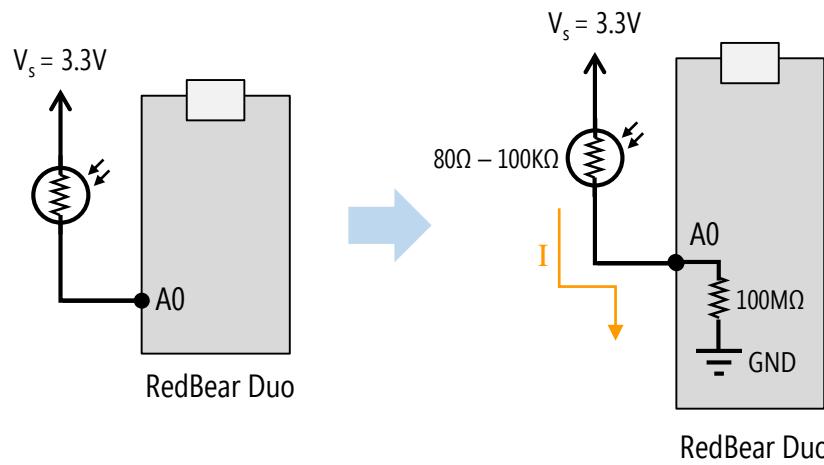

Microcontroller **input pins** have incredibly **high input resistance** (effectively infinite). In fact, you can assume that very little current flows in or out of an input pin. Let's check this!

Solve for current I when $R_{\text{photocell}}=80\Omega$

$$\text{Current} = I = \frac{V_{\text{high potential}} - V_{\text{low potential}}}{R_1 + R_2}$$

$$I = \frac{V_s - GND}{R_1 + R_2} \quad \text{Where } R_1=R_{\text{photocell}} \text{ and } R_2=\text{internal resistance on input pin}$$

$$I = \frac{3.3V - 0}{80\Omega + 100,000,000\Omega} = 0.000000033A = 33nA$$

Solve for the V_{A0}

$$V_s - V_{A0} = I * R_1$$

Ohm's law states that the voltage difference across a resistor is equal to $I * R$

$$V_{A0} = V_s - I * R_1$$

Rearrange the equation a bit to orient things in terms of V_{out}

$$V_{A0} = 3.3V - 33nA * 80\Omega$$

Plugin numbers

$$V_{A0} = 3.3V - 0.00000264V$$

$$V_{A0} = 3.299997V$$

USING A VARIABLE RESISTIVE SENSOR


WHY DOESN'T THIS CIRCUIT WORK?

Solve for current I when $R_{\text{photocell}} = 80\Omega$

$$\text{Current} = I = \frac{V_{\text{high potential}} - V_{\text{low potential}}}{R_1 + R_2}$$

$$I = \frac{V_s - \text{GND}}{R_1 + R_2}$$
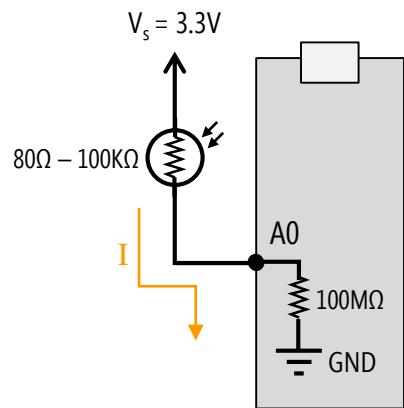
$$I = \frac{3.3V - 0}{80\Omega + 100,000,000\Omega} = 33nA$$



RedBear Duo

Microcontroller **input pins** have **incredibly high input resistance** (effectively infinite). In fact, you can assume that very little current flows in or out of an input pin.

Solve for the V_{A0}

$$V_s - V_{A0} = I * R_1$$

$$V_{A0} = V_s - I * R_1$$

$$V_{A0} = 3.3V - 33nA * 80\Omega$$

$$V_{A0} = 3.3V - 0.00000264V$$

$$V_{A0} = 3.299997V$$

Solve for current I when $R_{\text{photocell}} = 100K\Omega$

$$\text{Current} = I = \frac{V_{\text{high potential}} - V_{\text{low potential}}}{R_1 + R_2}$$

$$I = \frac{V_s - \text{GND}}{R_1 + R_2}$$

$$I = \frac{3.3V - 0}{100K\Omega + 100M\Omega} = 32.97nA$$

Solve for the V_{A0}

$$V_s - V_{A0} = I * R_1$$

$$V_{A0} = V_s - I * R_1$$


$$V_{A0} = 3.3V - 32.97nA * 100,000\Omega$$

$$V_{A0} = 3.3V - 0.00329V$$

$$V_{A0} = 3.2967V$$

USING A VARIABLE RESISTIVE SENSOR

WHY DOESN'T THIS CIRCUIT WORK?

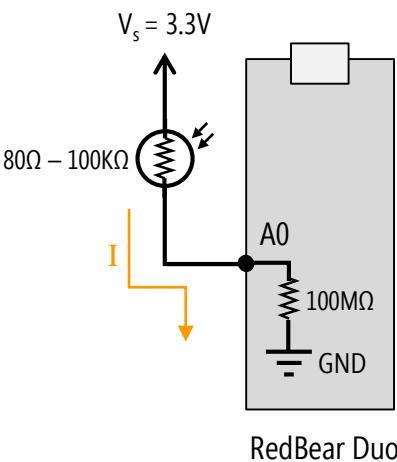

Microcontroller **input pins** have incredibly **high input resistance** (effectively infinite). In fact, you can assume that very little current flows in or out of an input pin.

Solve for current I when $R_{\text{photocell}} = 80\Omega$

$$\text{Current} = I = \frac{V_{\text{high potential}} - V_{\text{low potential}}}{R_1 + R_2}$$

$$I = \frac{V_s - \text{GND}}{R_1 + R_2}$$

$$I = \frac{3.3V - 0}{80\Omega + 100,000,000\Omega} = 33nA$$

Solve for the V_{A0}

Wow, OK, no wonder we are not seeing any changes in our photocell code. Our input voltage is not varying at all! So what do we do?

$$V_{A0} = 3.3V - 0.00000264V$$

$$V_{A0} = 3.299997V$$

Solve for current I when $R_{\text{photocell}} = 100K\Omega$

$$\text{Current} = I = \frac{V_{\text{high potential}} - V_{\text{low potential}}}{R_1 + R_2}$$

$$I = \frac{V_s - \text{GND}}{R_1 + R_2}$$

$$I = \frac{3.3V - 0}{100K\Omega + 100M\Omega} = 32.97nA$$

Solve for the V_{A0}


$$7nA * 100,000\Omega$$

$$V_{A0} = 3.3V - 0.00329V$$

$$V_{A0} = 3.2967V$$

USING A VARIABLE RESISTIVE SENSOR

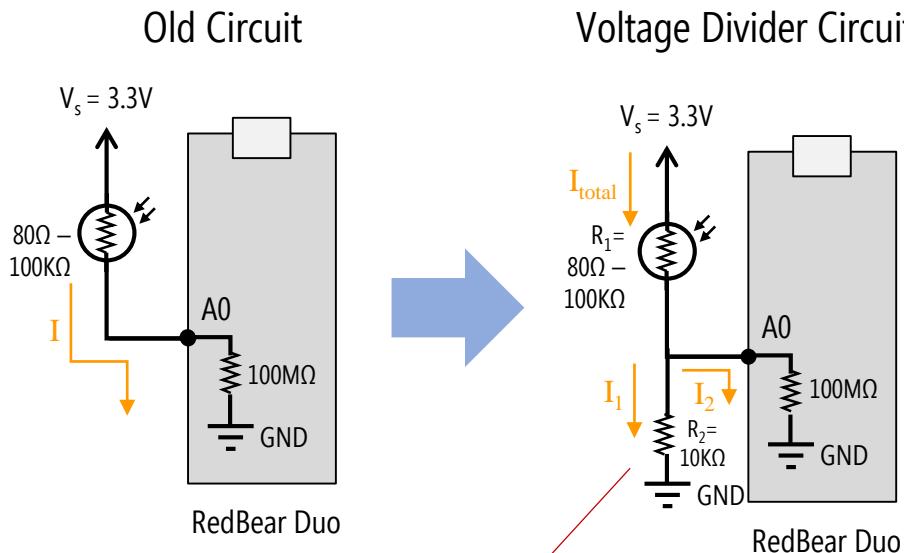
ADD A RESISTOR TO CREATE A VOLTAGE DIVIDER



This is our **voltage divider resistor**. The **ratio** between this resistor and R_1 is what's important.

USING A VARIABLE RESISTIVE SENSOR

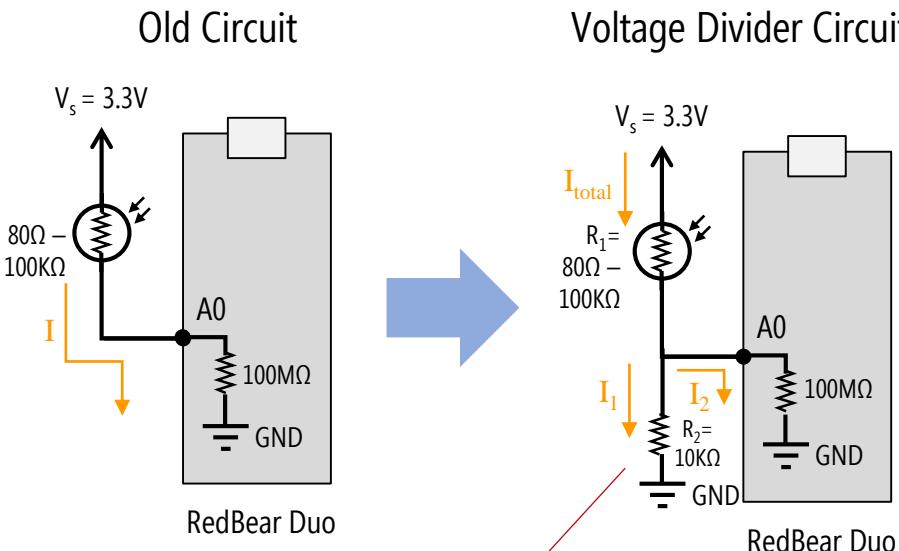ADD A RESISTOR TO CREATE A VOLTAGE DIVIDER




This is our **voltage divider resistor**. The **ratio** between this resistor and R_1 is what's important.

No magic here! We even covered this in our circuit lecture! 😊

SERIES VS. PARALLEL RESISTANCE OHM'S LAW EXERCISE: SOLVE FOR V1, V2, AND V3

How did I know V1 and V3?

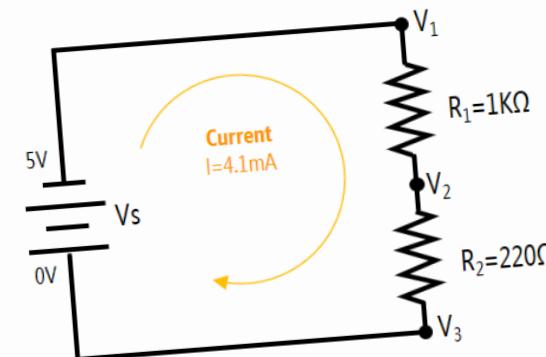

$$\text{Current } I = \frac{V_{\text{high potential}} - V_{\text{low potential}}}{R}$$

$$V_1 - V_2 = I * R_1$$


$$V_2 = V_1 - I * R_1 \quad \text{And we know } V_1 = 5V$$

$$V_2 = 5V - 0.0041A * 1,000\Omega = 0.9V$$

$$V_3 = 0V$$

USING A VARIABLE RESISTIVE SENSOR

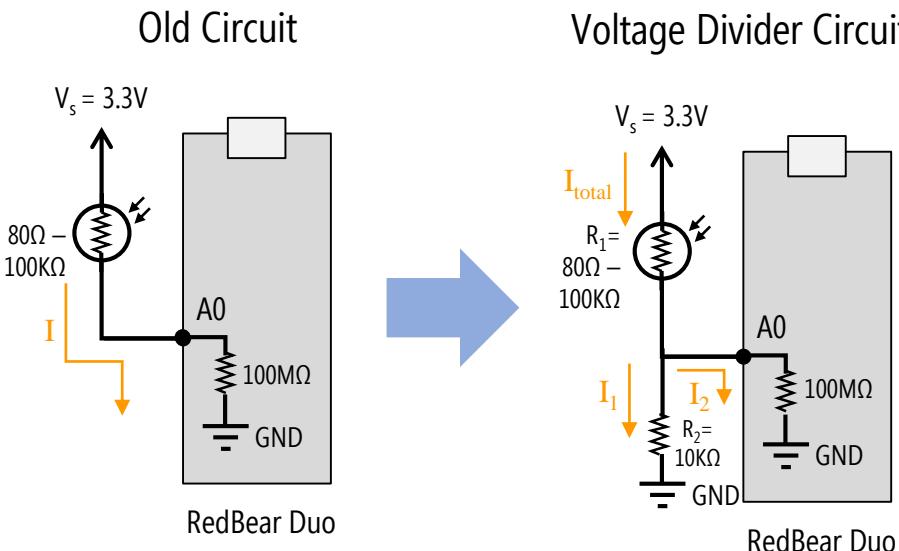ADD A RESISTOR TO CREATE A VOLTAGE DIVIDER



We know that I_2 is super small. So, $I_{total} \approx I_1$
Let's solve for current I_{total} when $R_1=80\Omega$ & $R_2=10k\Omega$

$$Current = I_{total} = \frac{V_{high\ potential} - V_{low\ potential}}{R_1 + R_2}$$

$$I_{total} = \frac{V_s - GND}{R_1 + R_2}$$

$$I_{total} = \frac{3.3V - 0}{80\Omega + 10,000\Omega} = 0.000327A = 0.33mA$$

Solve for the V_{A0}

$$V_s - V_{A0} = I * R_1$$

$$V_{A0} = V_s - I * R_1$$

$$V_{A0} = 3.3V - 0.33mA * 80\Omega$$


$$V_{A0} = 3.3V - 0.0262V$$

$$V_{A0} = 3.27V$$

USING A VARIABLE RESISTIVE SENSOR

ADD A RESISTOR TO CREATE A VOLTAGE DIVIDER

Voltage Divider Circuit

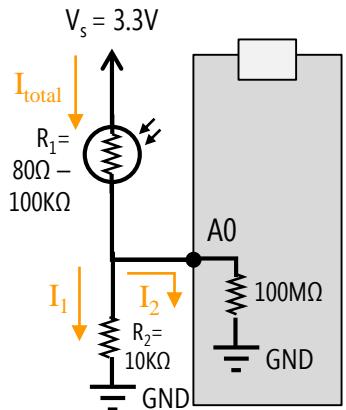

RedBear Duo

Let's solve for current I_{total} when $R_1=80\Omega$ & $R_2=10K\Omega$

$$Current = I_{total} = \frac{V_{high\ potential} - V_{low\ potential}}{R_1 + R_2}$$

$$I_{total} = \frac{V_s - GND}{R_1 + R_2}$$

$$I_{total} = \frac{3.3V - 0}{80\Omega + 10,000\Omega} = 0.33mA$$

Solve for the V_{A0}

$$V_s - V_{A0} = I * R_1$$

$$V_{A0} = V_s - I * R_1$$

$$V_{A0} = 3.3V - 0.33mA * 80\Omega$$

$$V_{A0} = 3.3V - 0.0262V$$

$$V_{A0} = 3.27V$$

Let's solve for current I_{total} when $R_1=100K\Omega$ & $R_2=10K\Omega$

$$Current = I_{total} = \frac{V_{high\ potential} - V_{low\ potential}}{R_1 + R_2}$$

$$I_{total} = \frac{V_s - GND}{R_1 + R_2}$$

$$I_{total} = \frac{3.3V - 0}{100K\Omega + 10,000\Omega} = 0.03mA$$

Solve for the V_{A0}

$$V_s - V_{A0} = I * R_1$$

$$V_{A0} = V_s - I * R_1$$

$$V_{A0} = 3.3V - 0.03mA * 100K\Omega$$


$$V_{A0} = 3.3V - 3V$$

$$V_{A0} = 0.3V$$

USING A VARIABLE RESISTIVE SENSOR

ADD A RESISTOR TO CREATE A VOLTAGE DIVIDER

Voltage Divider Circuit

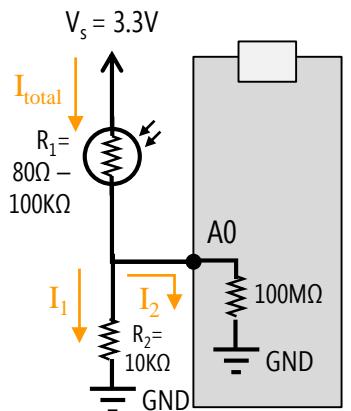

RedBear Duo

Let's solve for current I_{total} when $R_1=80\Omega$ & $R_2=10K\Omega$

$$Current = I_{total} = \frac{V_{high\ potential} + V_{low\ potential}}{R_1 + R_2}$$

$$I_{total} = \frac{V_s - GND}{R_1 + R_2}$$

$$I_{total} = \frac{3.3V - 0}{80\Omega + 10,000\Omega} = 0.33mA$$

Solve for the V_{A0}

This is more like it! Now we are seeing a **nice range of input voltages** in response to the changing resistance of our photocell! Thanks **voltage divider!**

$$V_{A0} = 3.3V - 0.0262V$$

$$V_{A0} = 3.27V$$

Let's solve for current I_{total} when $R_1=100K\Omega$ & $R_2=10K\Omega$

$$Current = I_{total} = \frac{V_{high\ potential} + V_{low\ potential}}{R_1 + R_2}$$

$$I_{total} = \frac{V_s - GND}{R_1 + R_2}$$

$$I_{total} = \frac{3.3V - 0}{100K\Omega + 10,000\Omega} = 0.03mA$$

Solve for the V_{A0}

$$V_{A0} = R_2 / (R_1 + R_2) * V_s$$

$$V_{A0} = R_2 / (R_1 + R_2) * V_s$$

$$V_{A0} = 0.03mA * 100K\Omega$$

$$V_{A0} = 3.3V - 3V$$



$$V_{A0} = 0.3V$$

OK, let's try this again. Wire up a **photocell but with a voltage divider!**




USING A VARIABLE RESISTIVE SENSOR

WIRE UP A PHOTOCELL & PRINT VALUE & VOLTAGE

Incorrect Circuit: Read a photocell

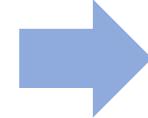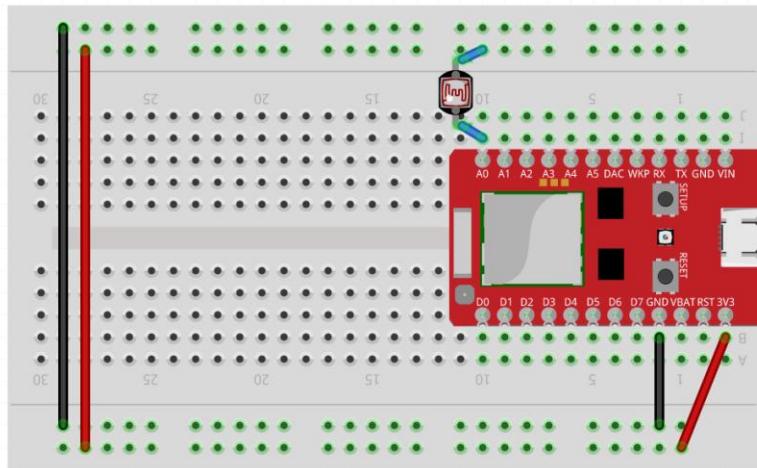

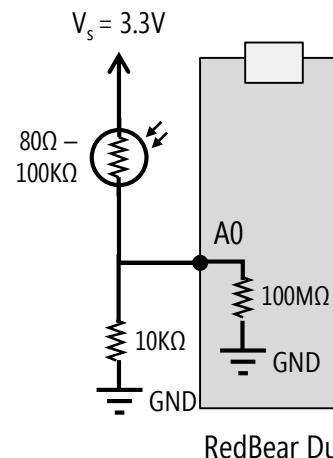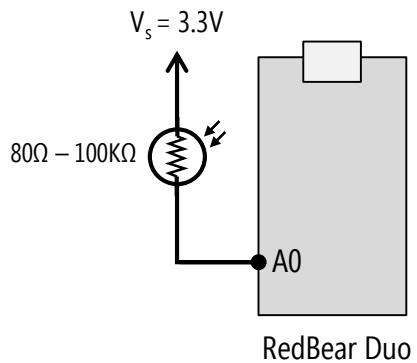
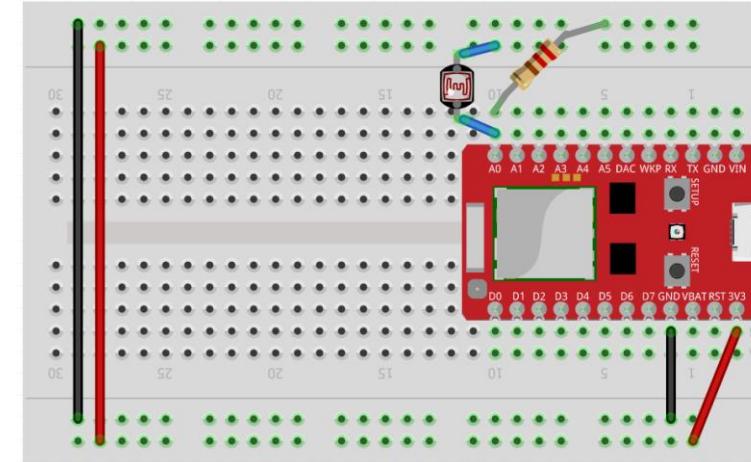
Correct Circuit: Read a photocell via voltage divider



USING A VARIABLE RESISTIVE SENSOR

WIRE UP A PHOTOCELL & PRINT VALUE & VOLTAGE

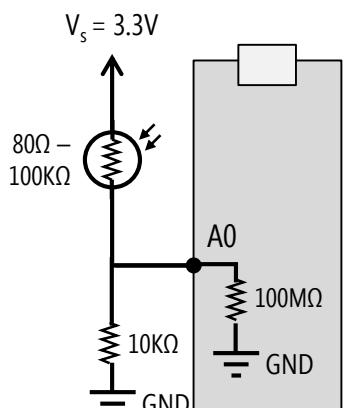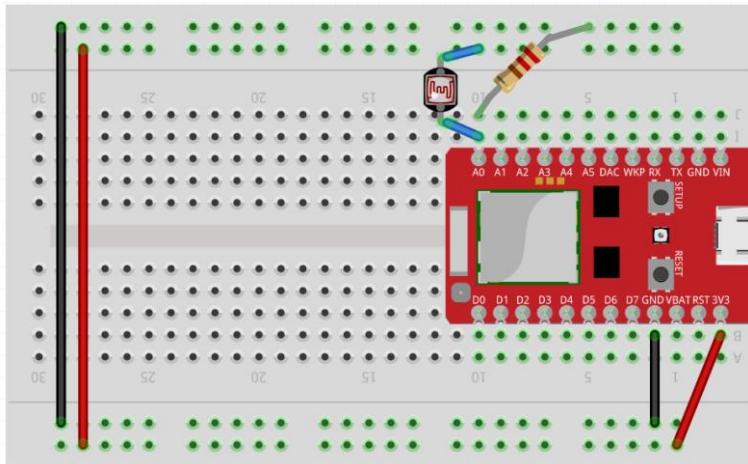Circuit: Read a photocell via voltage divider



RedBear Duo

Code: Same as before (no changes)

```
RedBearDuoReadPhotoCell | Arduino 1.8.5

SYSTEM_MODE(MANUAL); // required to use RedBear Duo

const int PHOTOCELL_INPUT_PIN = A0;
const int MAX_ADC_VALUE = 4096; // 12-bit ADC
const float MAX_VOLTAGE = 3.3;

void setup() {
    pinMode(PHOTOCELL_INPUT_PIN, INPUT);
    pinMode(D0, OUTPUT);
    Serial.begin(9600);
}

void loop() {
    // Read the photocell value (which will range from 0 to 4096)
    int photocellVal = analogRead(PHOTOCELL_INPUT_PIN);

    // Convert to a voltage
    float inputVoltage = MAX_VOLTAGE * photocellVal / MAX_ADC_VALUE;

    // Print to serial
    Serial.print(photocellVal);
    Serial.print("\t");
    Serial.println(inputVoltage);
    delay(100);
}
```

Done Saving.

Output: Now varies from ~0.3V – 3.28V

```
/dev/cu.usbmodem14611





2641 2.13
1998 1.61
1572 1.27
1570 1.26
1289 1.04
1963 1.58
682 0.55
1636 1.32
1368 1.10
3867 3.12
3883 3.13
3880 3.13
3882 3.13
4032 3.25
3998 3.22
4048 3.26
3985 3.21
3308 2.67
1319 1.06
964 0.78
2034 1.64
3893 3.14
3891 3.13
```

Autoscroll No line ending 9600 baud Clear output

VOLTAGE DIVIDERS

VOLTAGE DIVIDER SCHEMATICS

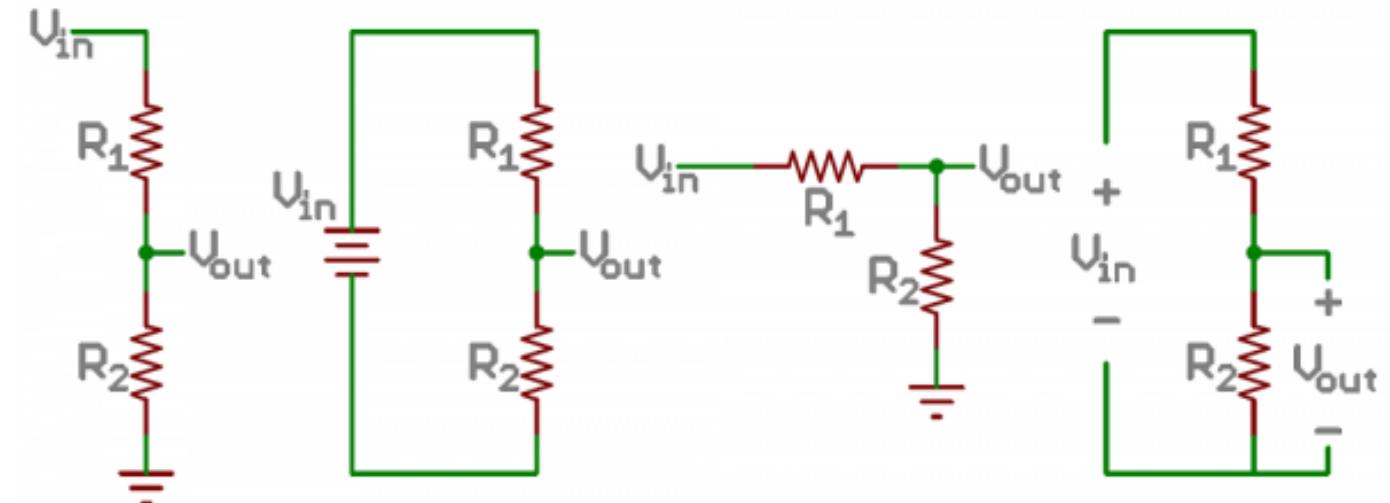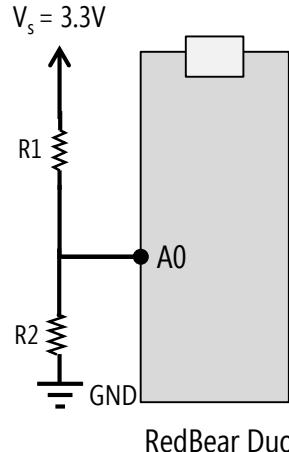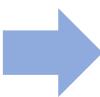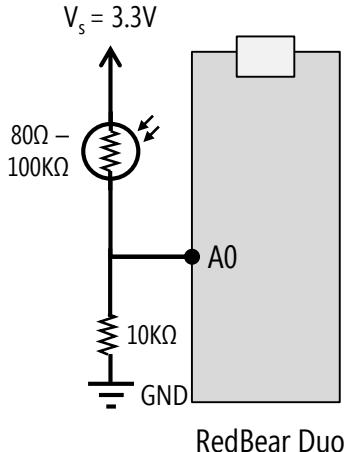
Voltage dividers are often written in a variety of ways (but they are all the same circuit!)



VOLTAGE DIVIDERS

VOLTAGE DIVIDER EQUATION

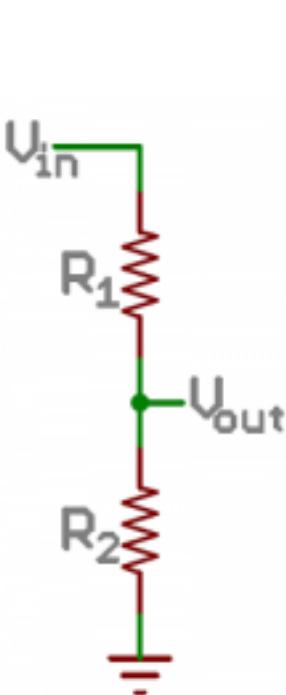The voltage divider equation helps simplify our calculations. Let's see how!



Solve for current I

$$\text{Current} = I = \frac{V_{\text{high potential}} - V_{\text{low potential}}}{R_1 + R_2}$$

$$I = \frac{V_{in} - GND}{R_1 + R_2} = \frac{V_{in} - 0V}{R_1 + R_2} = \frac{V_{in}}{R_1 + R_2}$$

Solve for the V_{out}

$$V_{in} - V_{out} = I * R_1$$

Ohm's law states that the voltage difference across a resistor is equal to $I * R$

$$V_{out} = V_{in} - I * R_1$$

Rearrange the equation a bit to orient things in terms of V_{out}

But we could also write V_{out} in terms of bottom half of circuit

$$V_{out} - GND = I * R_2$$

Or similarly, you could start with V_{out} as high potential and GND as low potential

$$V_{out} = I * R_2$$

$$V_{out} = \frac{V_{in}}{R_1 + R_2} * R_2$$

Replaced I with the equation above.

$$V_{out} = \frac{R_2}{R_1 + R_2} * V_{in}$$


This is how we've been solving for V_{out} on previous slides but there is a simpler way.

This is the canonical **voltage divider** equation

VOLTAGE DIVIDERS

VOLTAGE DIVIDER EQUATION

A few generalizations to keep in mind

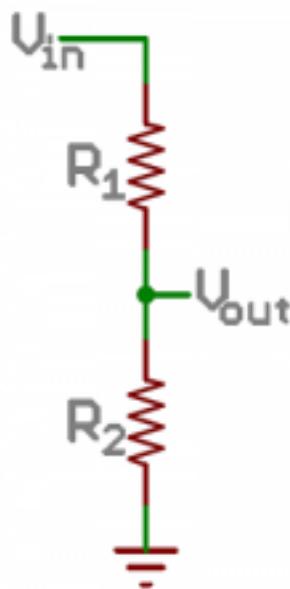

$$V_{out} = \frac{R_2}{R_1 + R_2} * V_{in}$$

$$\text{if } R_1 = R_2 : V_{out} = V_{in} \cdot \frac{R}{2R} = \frac{V_{in}}{2}$$

$$\text{if } R_2 \gg R_1 : V_{out} \approx V_{in} \cdot \frac{R_2}{R_2} = V_{in}$$

$$\text{if } R_2 \ll R_1 : V_{out} \approx V_{in} \cdot \frac{0}{R_1} = 0$$

Let's test and reinforce our knowledge here and **try out multiple different voltage dividers**. We will calculate V_{out} and then test our answer.



Use the same Arduino code as before.

VOLTAGE DIVIDERS

$$V_{out} = V_{in} * \frac{R_2}{R_1 + R_2}$$

VOLTAGE DIVIDER EXERCISE

Build Circuit: Voltage Divider

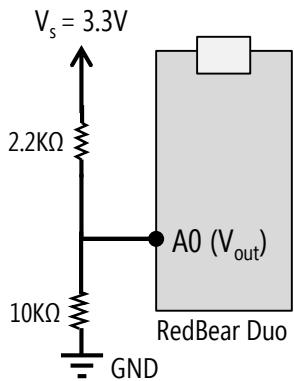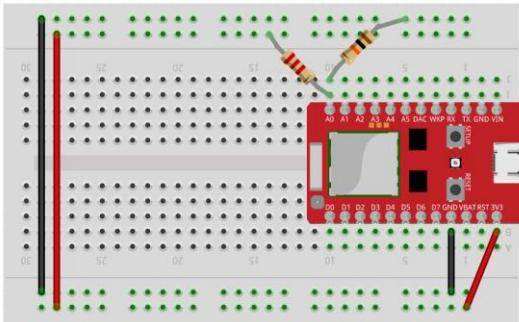



$$V_{out} = ?$$

VOLTAGE DIVIDERS

$$V_{out} = V_{in} * \frac{R_2}{R_1 + R_2}$$

VOLTAGE DIVIDER EXERCISE

Build Circuit: Voltage Divider

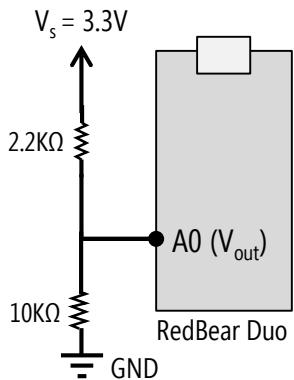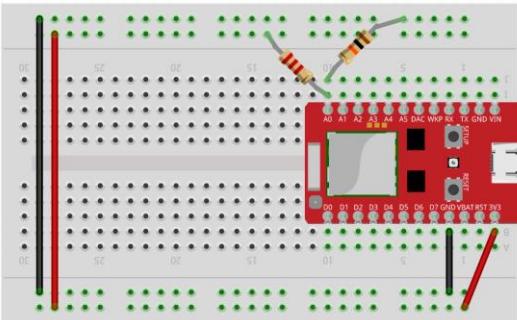

$$V_{out} = \frac{3.3V}{2.2K\Omega + 10K\Omega} * 10K\Omega$$



$$V_{out} = 2.7V$$

VOLTAGE DIVIDERS

$$V_{out} = V_{in} * \frac{R_2}{R_1 + R_2}$$

VOLTAGE DIVIDER EXERCISE

Build Circuit: Voltage Divider

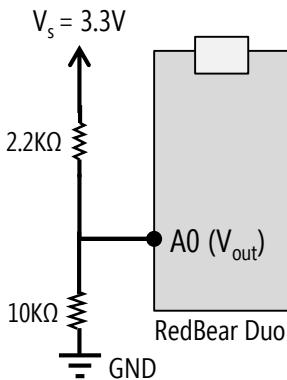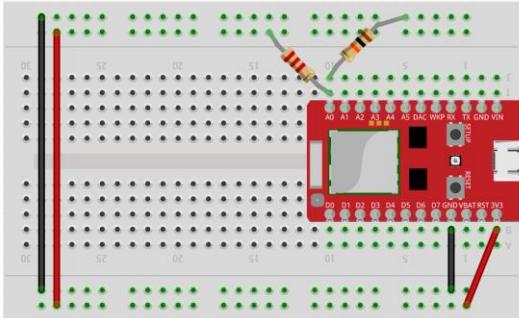

$$V_{out} = \frac{3.3V}{2.2k\Omega + 10k\Omega} * 10k\Omega$$

$$V_{out} = 2.7V$$

Code: Print analog value + voltage (same as before)

```

RedBearDuoAnalogRead | Arduino 1.8.5

RedBearDuoAnalogRead
SYSTEM_MODE(MANUAL); // required to use RedBear Duo

const int ANALOG_INPUT_PIN = A0;
const int MAX_ADC_VALUE = 4096; // 12-bit ADC
const float MAX_VOLTAGE = 3.3;

void setup() {
  pinMode(ANALOG_INPUT_PIN, INPUT);
  pinMode(D0, OUTPUT);
  Serial.begin(9600);
}

void loop() {
  // Read the analog input (which will range from 0 to 4096)
  int analogVal = analogRead(ANALOG_INPUT_PIN);

  // Convert to a voltage
  float inputVoltage = MAX_VOLTAGE * analogVal / MAX_ADC_VALUE;

  // Print to serial
  Serial.print(analogVal);
  Serial.print("\t");
  Serial.println(inputVoltage);
  delay(100);
}

Done uploading.

```

Serial Output: This is how we can verify our calculated answer!

Analog Value	Voltage (V)
3333	2.69
3332	2.68
3331	2.68
3333	2.69
3335	2.69
3333	2.69
3333	2.69
3332	2.68
3332	2.68
3333	2.69
3335	2.69
3333	2.69
3333	2.69
3333	2.69
3333	2.69
3332	2.68
3330	2.68
3335	2.69
3332	2.68
3332	2.68
3333	2.69
3331	2.68
3333	2.69
3335	2.69

/dev/cu.usbmodem14611

Autoscroll

No line ending

9600



VOLTAGE DIVIDERS

$$V_{out} = V_{in} * \frac{R_2}{R_1 + R_2}$$

VOLTAGE DIVIDER EXERCISE

It's the ratio between the two resistors that's important

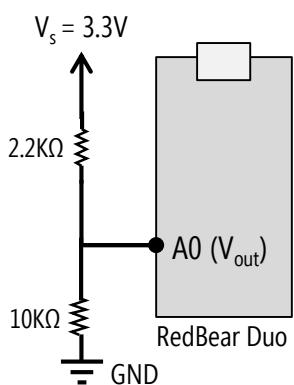
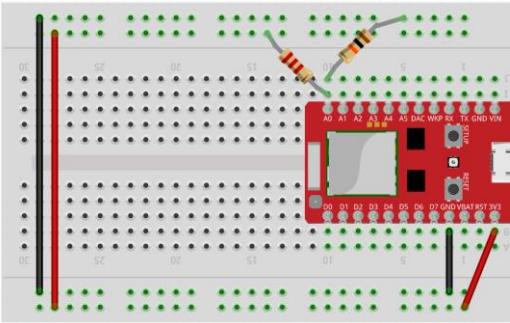
Voltage Divider: (R1, R2) = (2.2KΩ, 10KΩ)



$$V_{out} = \frac{3.3V}{2.2K\Omega + 10K\Omega} * 10K\Omega$$

$$V_{out} = 2.7V$$

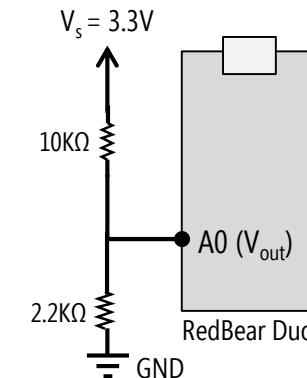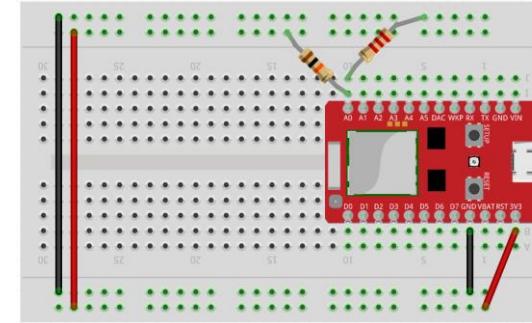Voltage Divider: (R1, R2) = (10KΩ, 2.2KΩ)



$$V_{out} = \frac{3.3V}{10K\Omega + 2.2K\Omega} * 2.2K\Omega$$

$$V_{out} = 0.6V$$



VOLTAGE DIVIDERS

$$V_{out} = V_{in} * \frac{R_2}{R_1 + R_2}$$

VOLTAGE DIVIDER EXERCISE

It's the ratio between the two resistors that's important

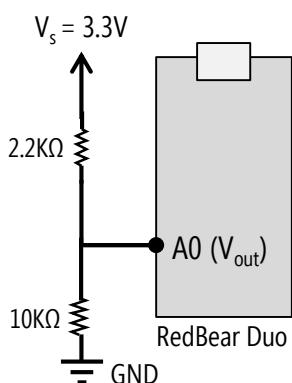
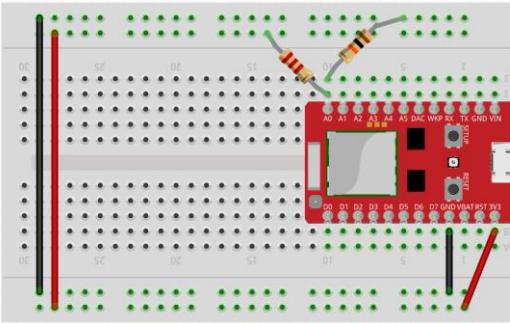
Voltage Divider: (R1, R2) = (2.2KΩ, 10KΩ)



$$V_{out} = \frac{3.3V}{2.2K\Omega + 10K\Omega} * 10K\Omega$$

$$V_{out} = 2.7V$$

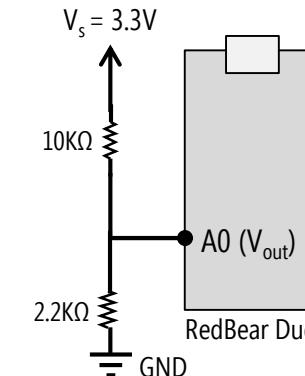
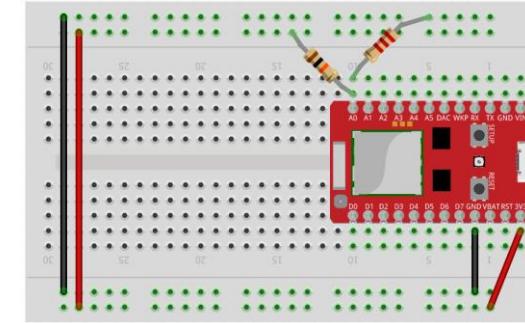
Voltage Divider: (R1, R2) = (10KΩ, 2.2KΩ)



$$V_{out} = \frac{3.3V}{10K\Omega + 2.2K\Omega} * 2.2K\Omega$$

$$V_{out} = 0.6V$$



Voltage Divider: (R1, R2) = (680Ω, 1KΩ)

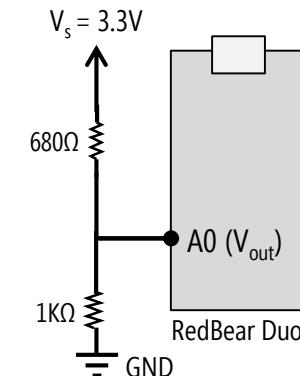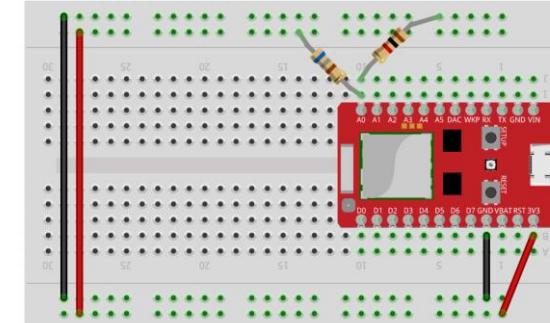

$$V_{out} = \frac{3.3V}{680\Omega + 1K\Omega} * 1K\Omega$$

$$V_{out} = 1.96V$$

Voltage Divider: (R1, R2) = (100Ω, 1KΩ)

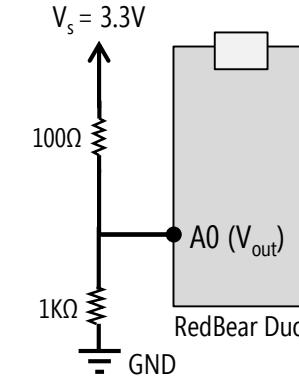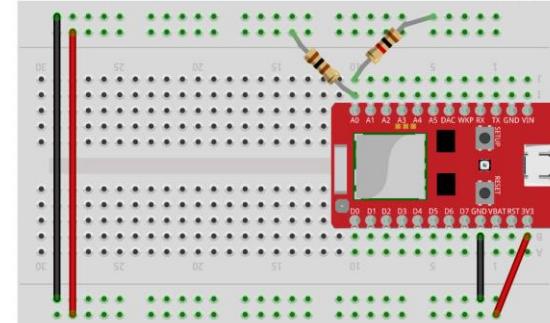


$$V_{out} = \frac{3.3V}{100\Omega + 1K\Omega} * 1K\Omega$$

$$V_{out} = 3V$$

$$V_{out} = V_{in} * \frac{R_2}{R_1 + R_2}$$


CHOOSING R2 IN VOLTAGE DIVIDER CIRCUITS

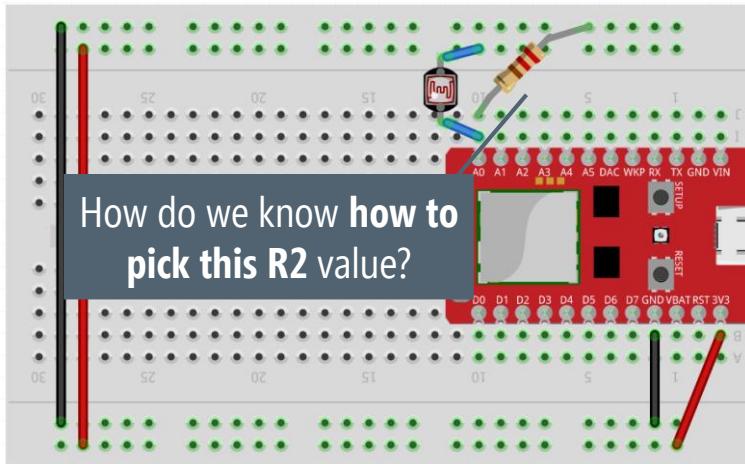Circuit: Read a photocell via voltage divider



It depends on the resistance range of your variable resistor (R1)


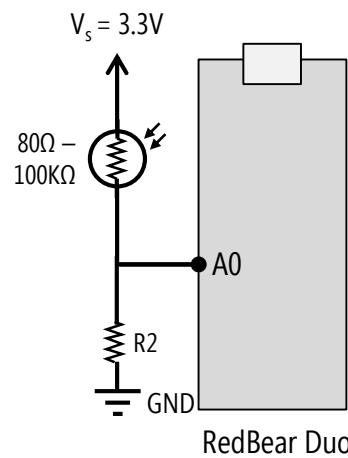
It depends on the context of use (what's the expected resistance range of R1)



USING A VARIABLE RESISTIVE SENSOR

$$V_{out} = V_{in} * \frac{R_2}{R_1 + R_2}$$



GRAPHING V_{OUT} FOR PHOTOCELL

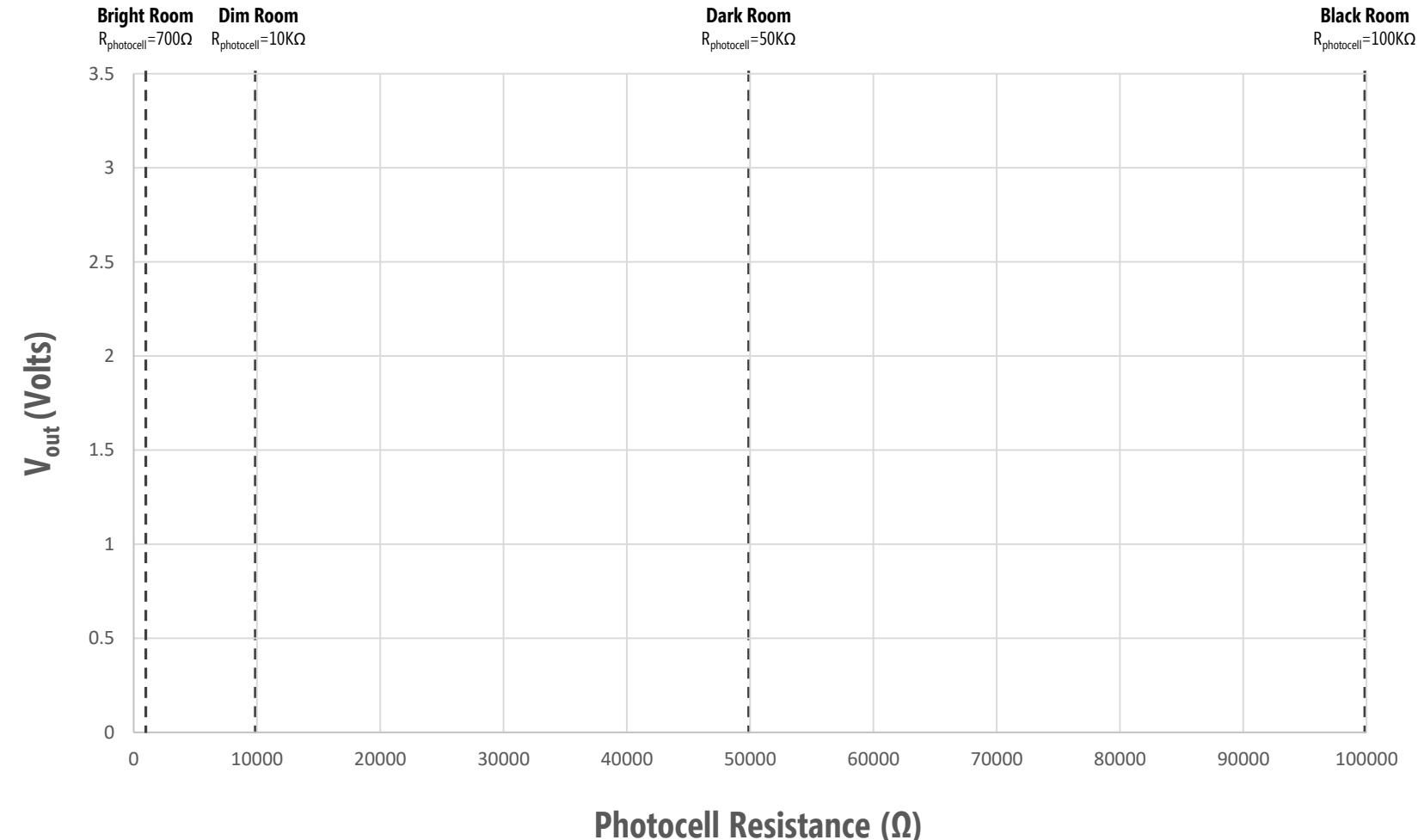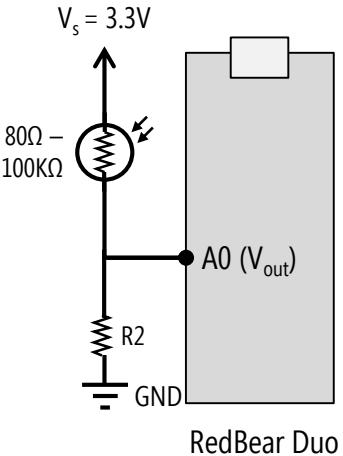

USING A VARIABLE RESISTIVE SENSOR

$$V_{out} = V_{in} * \frac{R_2}{R_1 + R_2}$$



GRAPHING V_{OUT} FOR PHOTOCELL

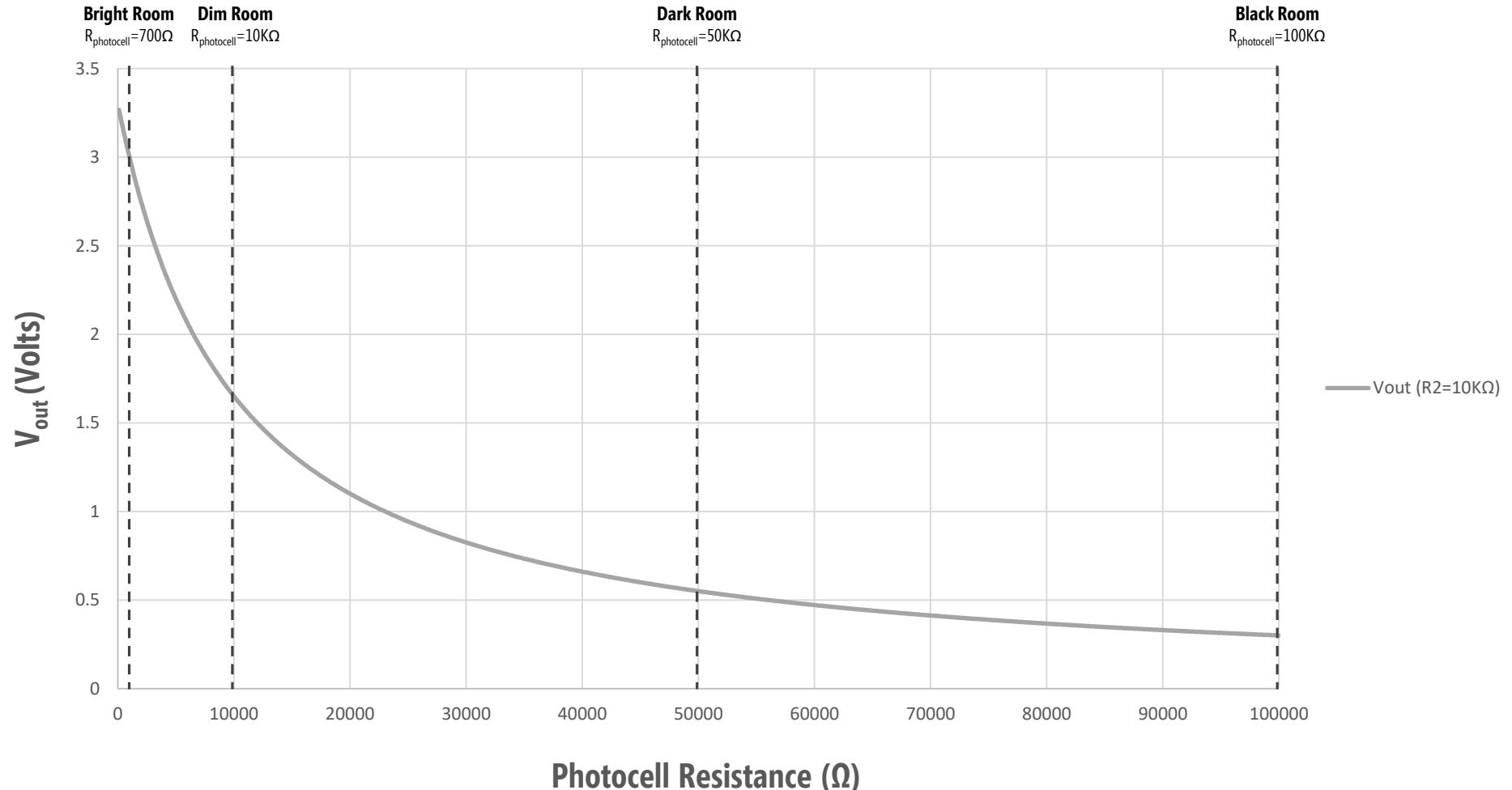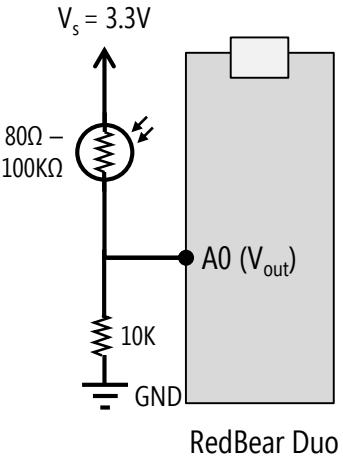

USING A VARIABLE RESISTIVE SENSOR

$$V_{out} = V_{in} * \frac{R_2}{R_1 + R_2}$$



GRAPHING V_{OUT} FOR PHOTOCELL

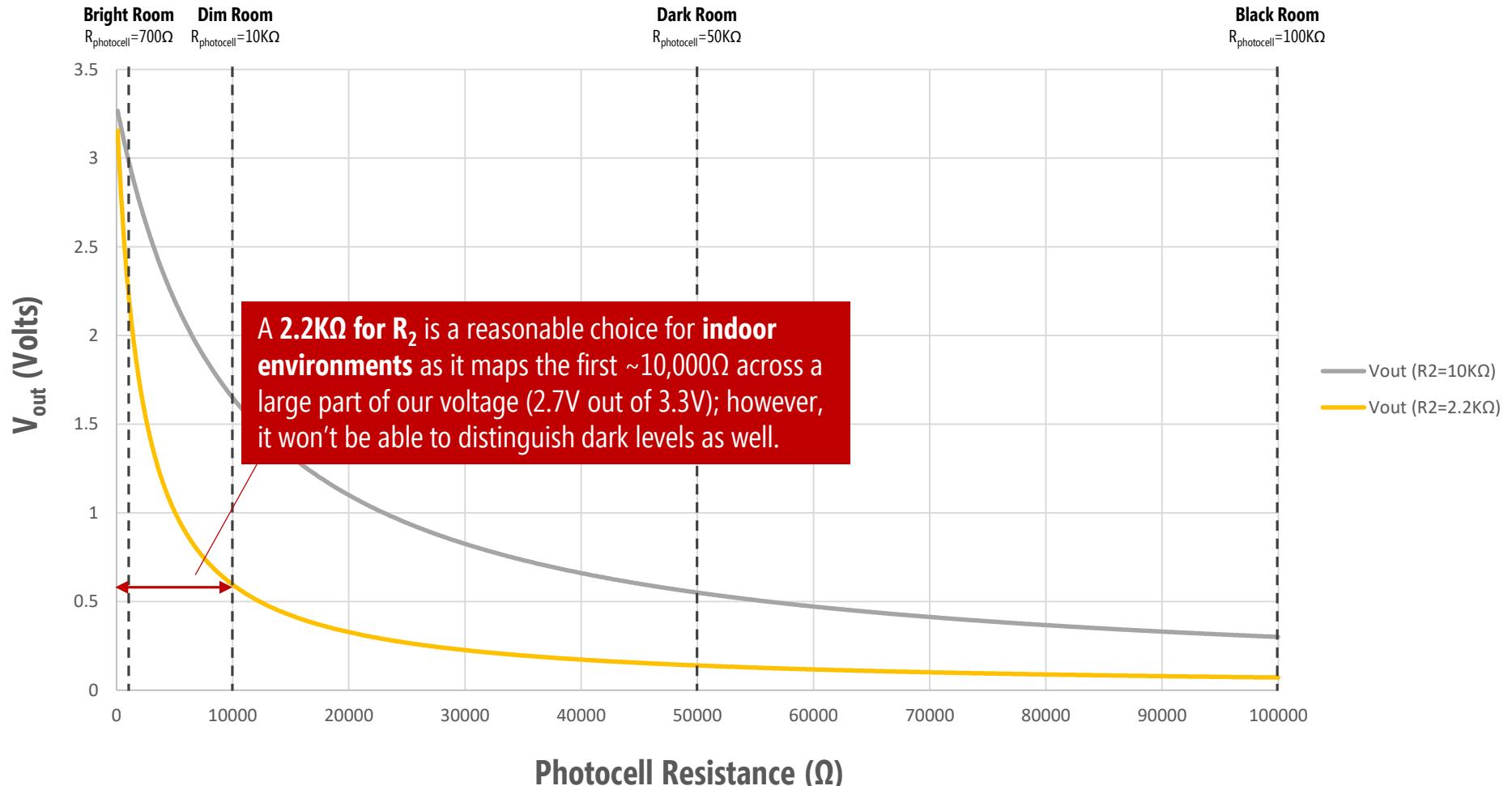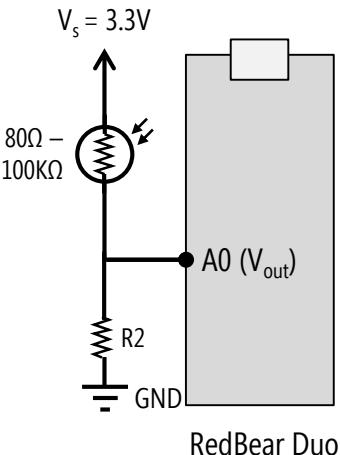

USING A VARIABLE RESISTIVE SENSOR

$$V_{out} = V_{in} * \frac{R_2}{R_1 + R_2}$$



GRAPHING VOUT FOR PHOTOCELL

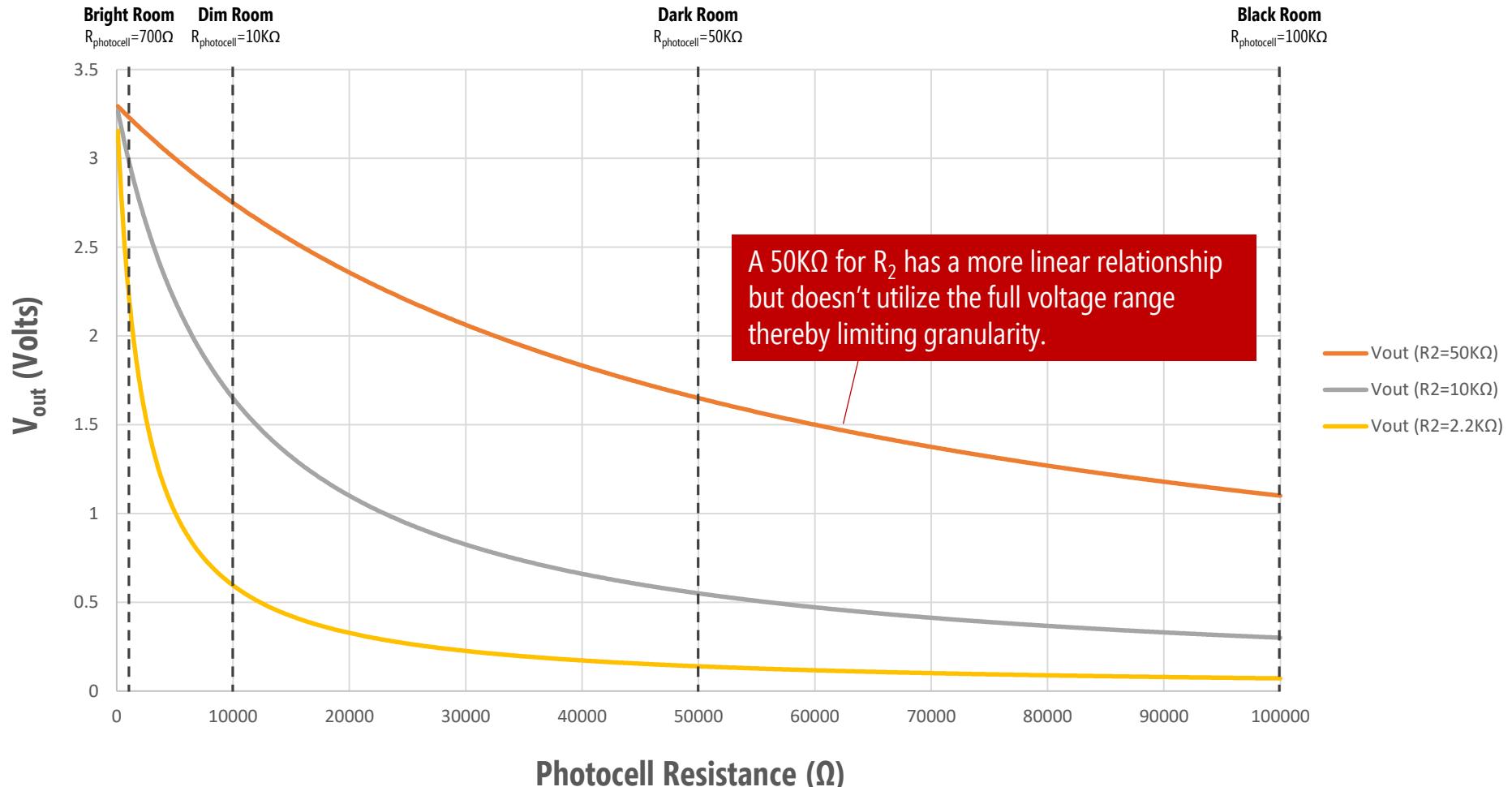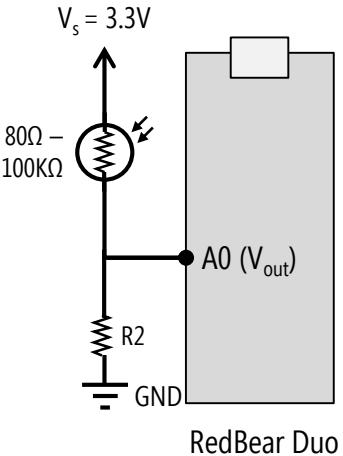

USING A VARIABLE RESISTIVE SENSOR

$$V_{out} = V_{in} * \frac{R_2}{R_1 + R_2}$$

GRAPHING V_{OUT} FOR PHOTOCELL

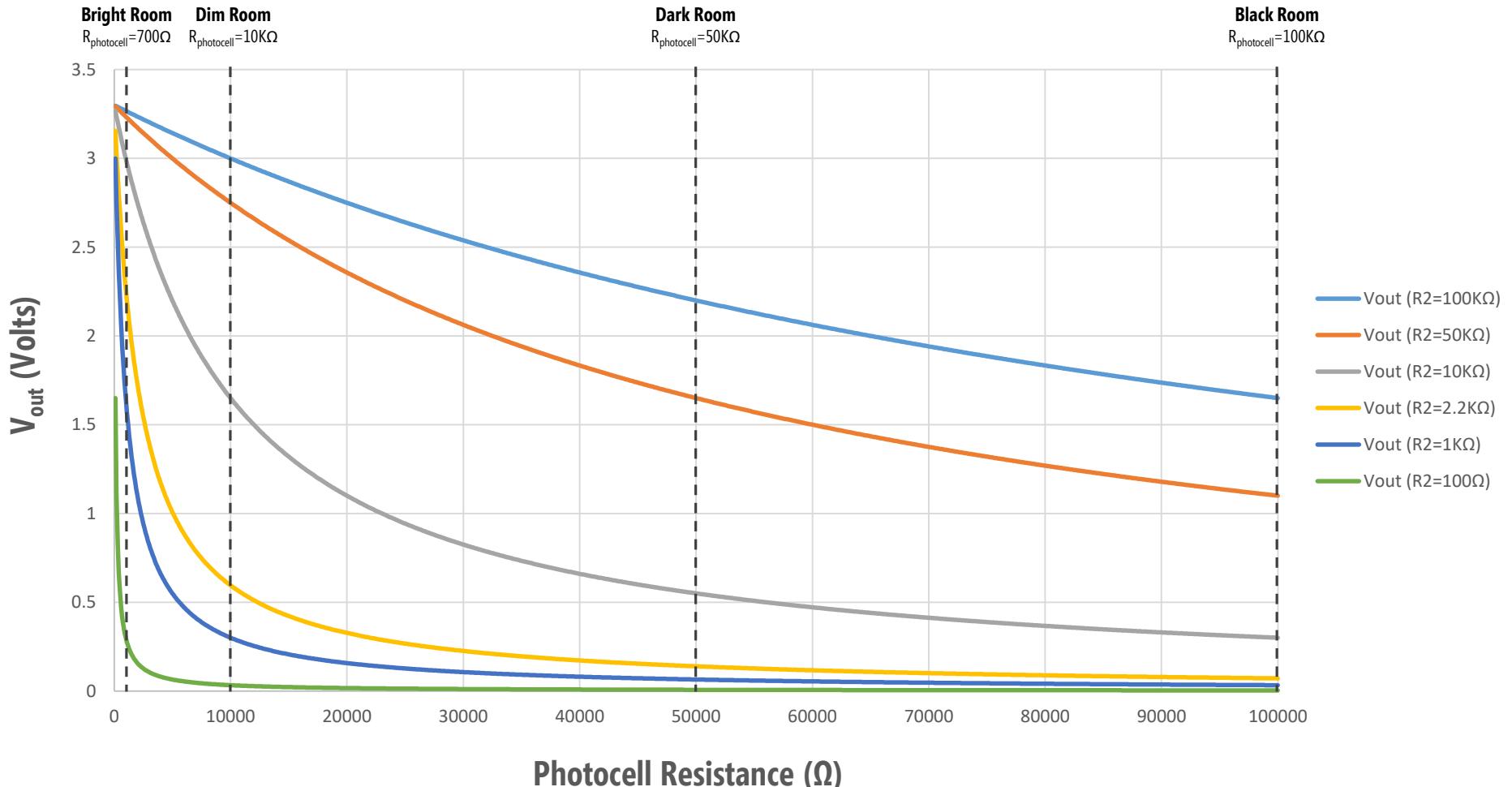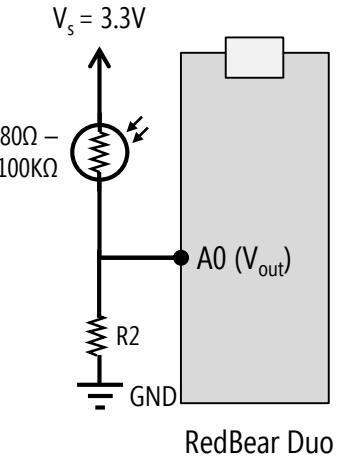


USING A VARIABLE RESISTIVE SENSOR

$$V_{out} = V_{in} * \frac{R_2}{R_1 + R_2}$$

AXEL BENZ FORMULATION FOR R2

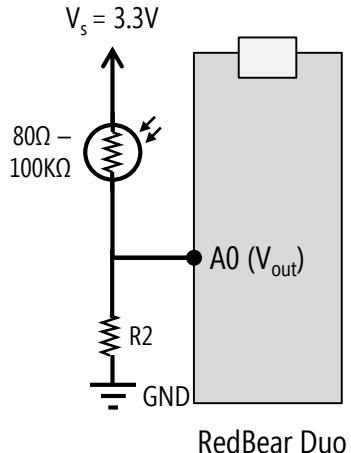First, measure the R_{min} and R_{max} values for your specific environment using a multimeter



Then use these measurements to find the value for R_2

$$R_2 = \sqrt{R_{1min} * R_{1max}}$$

$$R_2 = \sqrt{80\Omega * 10,000\Omega}$$

$$R_2 = \sim 900\Omega$$

USING A VARIABLE RESISTIVE SENSOR

EXPERIMENTATION

You'll also experiment with setting thresholds in the mapping function based on empirical observation

RedBearDuoReadPhotocellFadeLED

```
SYSTEM_MODE(MANUAL);

const int LED_OUTPUT_PIN = D0;
const int PHOTOCELL_INPUT_PIN = A0;

// Set the min and max photocell values (this will be based on
// the brightness of your environment and the size of the voltage-divider
// resistor that you selected).
const int MIN_PHOTOCELL_VAL = 1200; // Photocell reading in dark
const int MAX_PHOTOCELL_VAL = 3700; // Photocell reading in ambient light (tested in my office)
```

```
void setup() {
  pinMode(LED_OUTPUT_PIN, OUTPUT);
  pinMode(PHOTOCELL_INPUT_PIN, INPUT);
  Serial.begin(9600);
}
```

```
void loop() {
  // Read the photo-sensitive resistor value
  int photocellVal = analogRead(PHOTOCELL_INPUT_PIN);
```

```
// Remap the value for output.
int ledVal = map(photocellVal, MIN_PHOTOCELL_VAL, MAX_PHOTOCELL_VAL, 0, 255);
```

```
// The map function does not constrain output outside of the provided range
// so, we need to make sure that things are within range for the led
ledVal = constrain(ledVal, 0, 255);
```

```
// We want to invert the LED (it should be brighter when environment is darker)
ledVal = 255 - ledVal;
```

```
// Print the raw photocell value and the converted led value (e.g., for Serial Plotter)
Serial.print(photocellVal);
Serial.print(",");
Serial.println(ledVal);
```

Use Serial Plotter to figure out good min and max values for map

EXERCISE: USE A VARIABLE RESISTOR TO FADE LED


Read variable resistor

Fade LED

Can use photocell or force resistive sensor (easy to swap them)

ANALOG INPUT

PHOTOCELL INVERSELY FADES LED

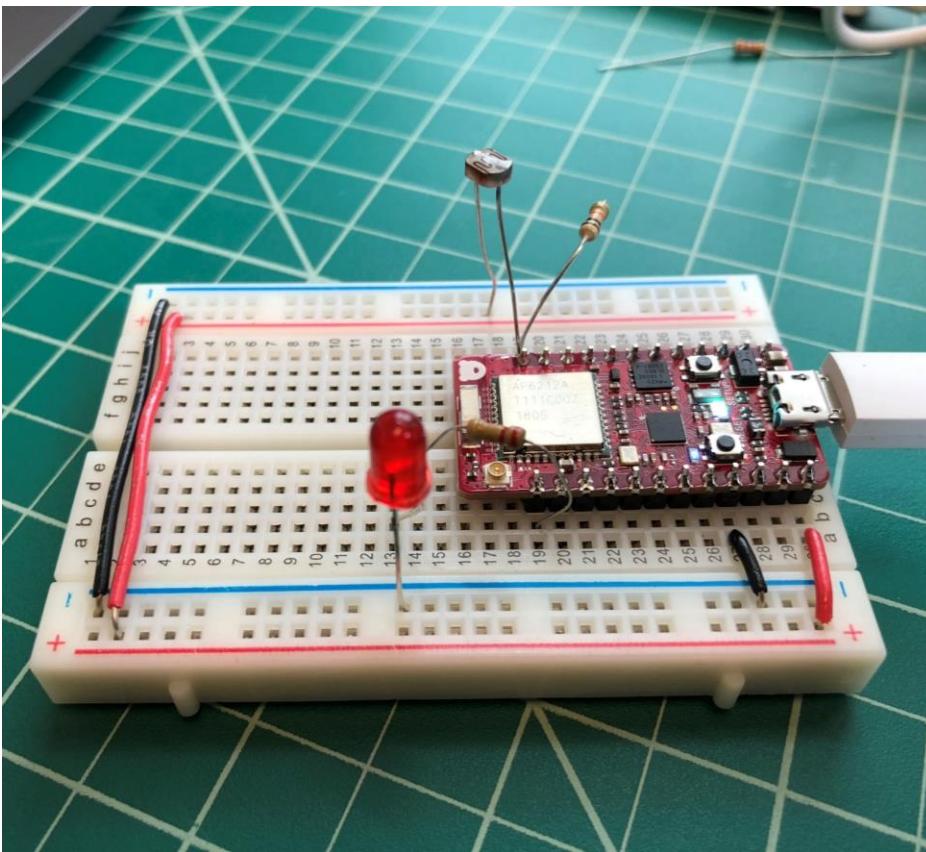

<https://github.com/jonfroehlich/CSE590Sp2018/tree/master/L06-Arduino/RedBearDuoReadPhotocellFadeLED>

RedBearDuoReadPhotocellFadeLED

```
SYSTEM_MODE(MANUAL);

const int LED_OUTPUT_PIN = D0;
const int PHOTOCELL_INPUT_PIN = A0;

// Set the min and max photocell values (this will be based on
// the brightness of your environment and the size of the voltage-divider
// resistor that you selected).
const int MIN_PHOTOCELL_VAL = 1200; // Photocell reading in dark
const int MAX_PHOTOCELL_VAL = 3700; // Photocell reading in ambient light (tested in my office)

void setup() {
    pinMode(LED_OUTPUT_PIN, OUTPUT);
    pinMode(PHOTOCELL_INPUT_PIN, INPUT);
    Serial.begin(9600);
}

void loop() {

    // Read the photo-sensitive resistor value
    int photocellVal = analogRead(PHOTOCELL_INPUT_PIN);

    // Remap the value for output.
    int ledVal = map(photocellVal, MIN_PHOTOCELL_VAL, MAX_PHOTOCELL_VAL, 0, 255);

    // The map function does not constrain output outside of the provided range
    // so, we need to make sure that things are within range for the led
    ledVal = constrain(ledVal, 0, 255);

    // We want to invert the LED (it should be brighter when environment is darker)
    ledVal = 255 - ledVal;

    // Print the raw photocell value and the converted led value (e.g., for Serial Plotter)
    Serial.print(photocellVal);
    Serial.print(",");
    Serial.println(ledVal);

    // Write out the LED value.
    analogWrite(LED_OUTPUT_PIN, ledVal);

    delay(100);
}
```

```
RedBearDuoReadPhotocellfadeLED
// Set the min and max photocell values (this will be based on
// the brightness of your environment and the size of the voltage-divider
// resistor that you selected).
const int MIN_PHOTOCELL_VAL = 1200; // Photocell reading in dark
const int MAX_PHOTOCELL_VAL = 3700; // Photocell reading in ambient light (tested in my offi

void setup() {
  pinMode(LED_OUTPUT_PIN, OUTPUT);
  pinMode(PHOTOCELL_INPUT_PIN, INPUT);
  Serial.begin(9600);
}

void loop() {

  // Read the potentiometer value
  int photocellVal = analogRead(PHOTOCELL_INPUT_PIN);

  // Remap the value for output.
  int ledVal = map(photocellVal, MIN_PHOTOCELL_VAL, MAX_PHOTOCELL_VAL, 0, 255);

  // The map function does not constrain output outside of the provided range
  // so, we need to make sure that things are within range for the led
  ledVal = constrain(ledVal, 0, 255);

  // We want to invert the LED (it should be brighter when environment is darker)
  ledVal = 255 - ledVal;


  // Print the raw photocell value and the converted led value (e.g., for Serial Plotter)
  Serial.print(photocellVal);
  Serial.print(",");
  Serial.println(ledVal);

  // Write out the LED value.
  analogWrite(LED_OUTPUT_PIN, ledVal);


  delay(100);
}
```

Done Saving.

53 RedBear Duo (Native USB Port) on

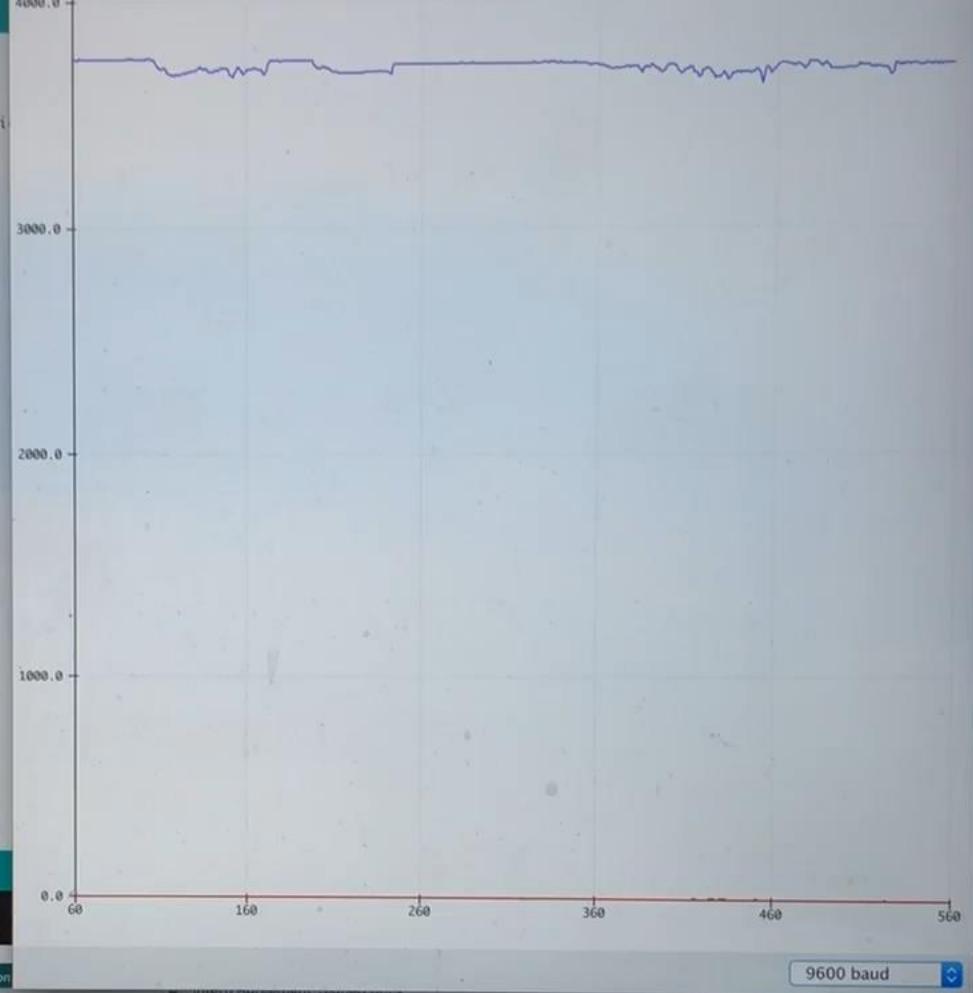


MacBook Pro

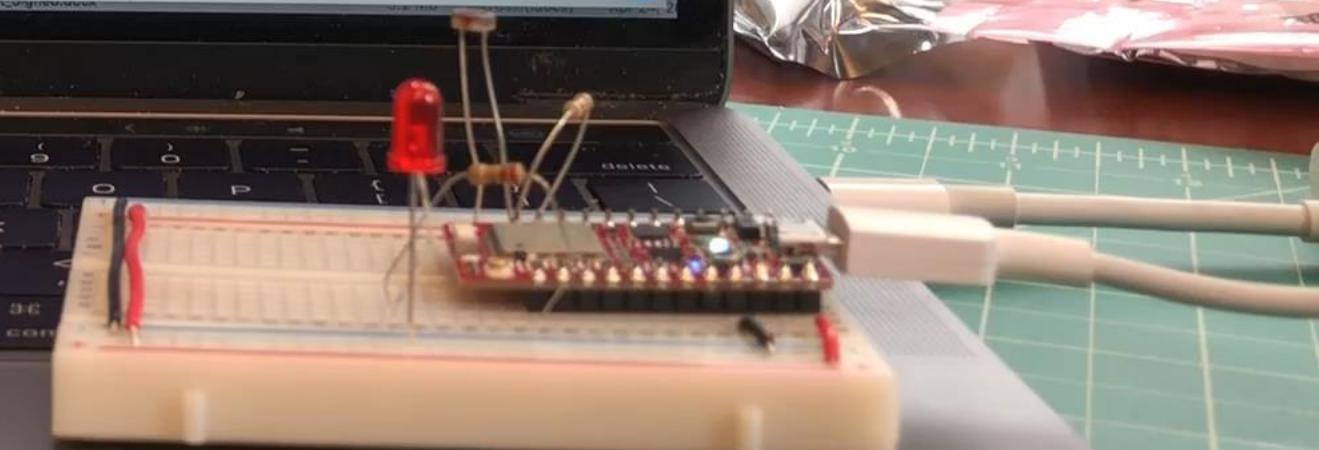

ANALOG INPUT

FSR FADES LED

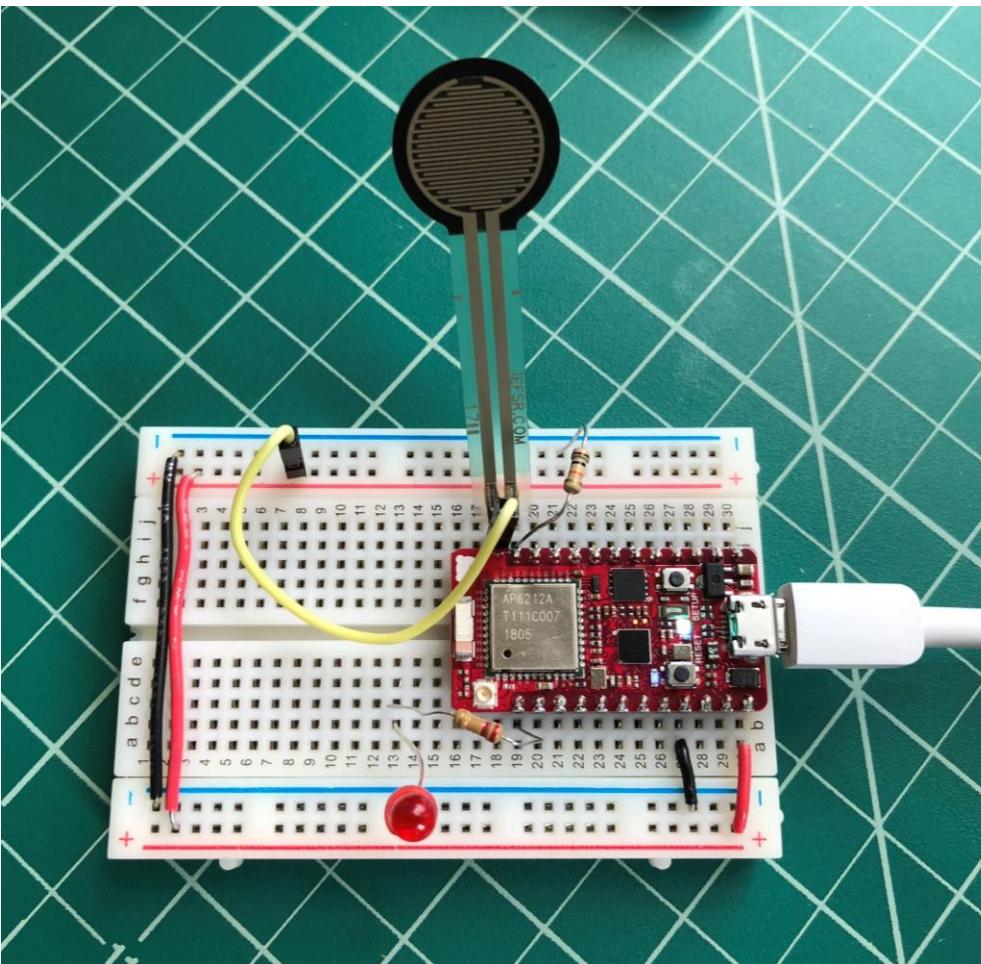

<https://github.com/jonfroehlich/CSE590Sp2018/tree/master/L06-Arduino/RedBearDuoReadForceSensitiveResistorLED>

RedBearDuoReadForceSensitiveResistorLED §

SYSTEM_MODE(MANUAL);

```
const int LED_OUTPUT_PIN = D0;
const int FORCESENSOR_INPUT_PIN = A0;
```

```
// Set the min and max force sensitive resistor values
const int MIN_FORCE_VAL = 0;
const int MAX_FORCE_VAL = 4000;
```

```
void setup() {
    pinMode(LED_OUTPUT_PIN, OUTPUT);
    pinMode(FORCESENSOR_INPUT_PIN, INPUT);
    Serial.begin(9600);
}
```

```
void loop() {
```

```
    // Read the force-sensitive resistor value
    int forceVal = analogRead(FORCESENSOR_INPUT_PIN);
```

```
    // Remap the value for output.
    int ledVal = map(forceVal, MIN_FORCE_VAL, MAX_FORCE_VAL, 0, 255);
```

```
    // The map function does not constrain output outside of the provided range
    // so, we need to make sure that things are within range for the led
    ledVal = constrain(ledVal, 0, 255);
```

```
    // Print the raw force sensor value and the converted led value so we can
    // see them in Serial Monitor and Serial Plotter
```

```
    Serial.print(forceVal);
```

```
    Serial.print(",");
```

```
    Serial.println(ledVal);
```

```
    // Write out the LED value.
```

```
    analogWrite(LED_OUTPUT_PIN, ledVal);
```



```
    delay(100);
}
```

This will be based on
the size of the voltage-divider
all reading in dark
all reading in ambient light (tested in my office)

```
value  
INPUT_PIN);  
  
VAL, MAX_FORCE_VAL, 0, 255);  
in output outside of the provided range  
ings are within range for the led  
and the converted led value (e.g., for Serial Plotter)  
0;
```

RedBear Duo (Native USB Port) on /dev

MacBook Pro

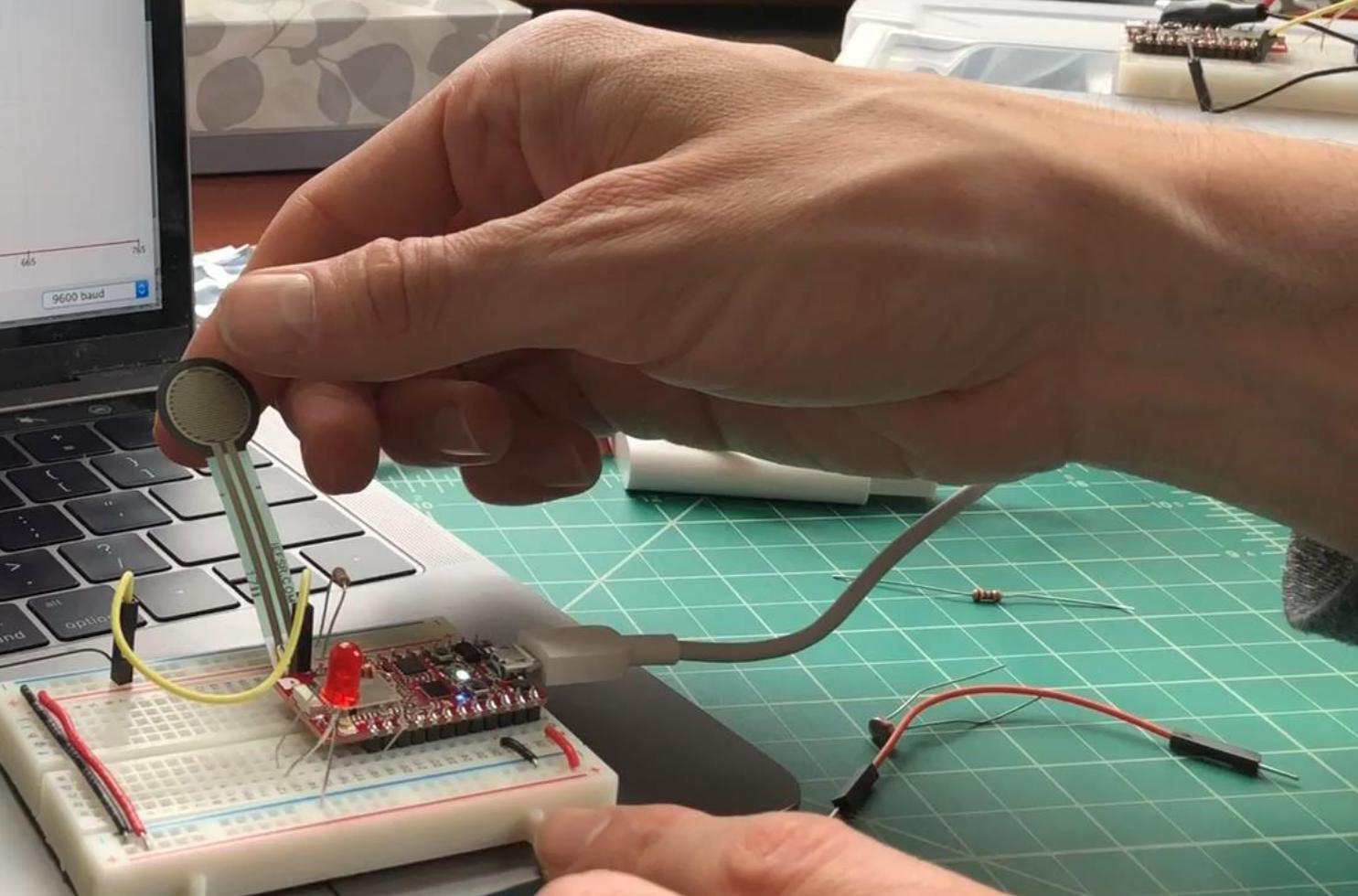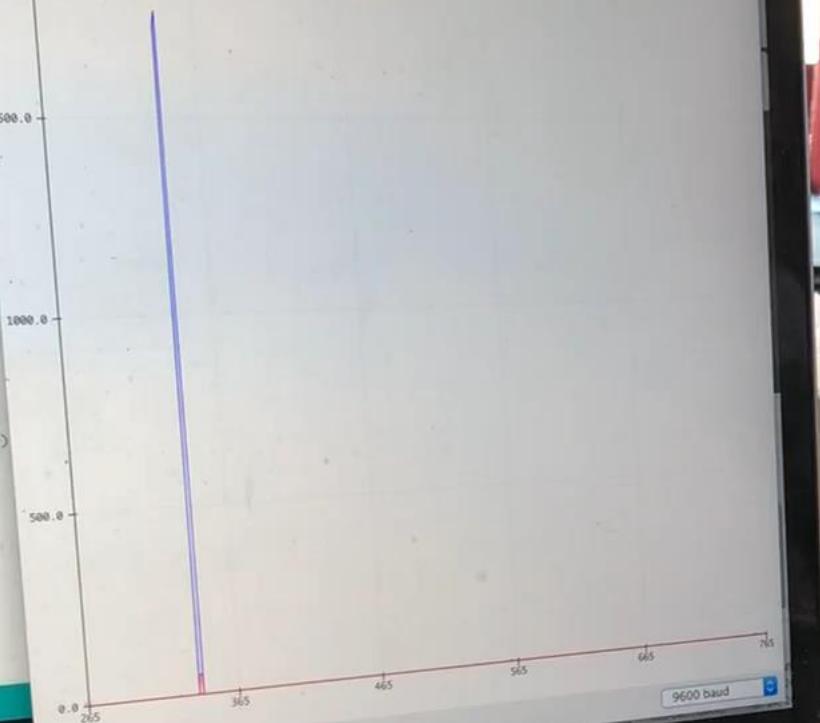

WORKING WITH SENSORS: LEARNING GOALS

How to use variable **resistive sensors**, including **voltage dividers**,
basic **signal smoothing**

Putting it together: **making a simple theremin**

How to use **buttons**, including **pull-up** and **pull-down resistors**,
and **debouncing**

Working with **interrupts**

Let's extend this to build a **theremin-like** instrument.

THEREMIN

ZELDA'S LULLABY ON THEREMIN



Source: Theremin Hero, <https://youtu.be/H-iUZD8wfjs>





To do this, we need to use the **piezoelectric buzzers** & the **tone()** function

USING PIEZO BUZZER

PIEZO ELECTRIC BUZZERS




Piezoelectric elements produce electric charge in response to mechanical stress. They can also work in the other direction: an applied current can distort material.

PIEZO BUZZER

WHAT IS A PIEZO BUZZER?

piezo ceramic element

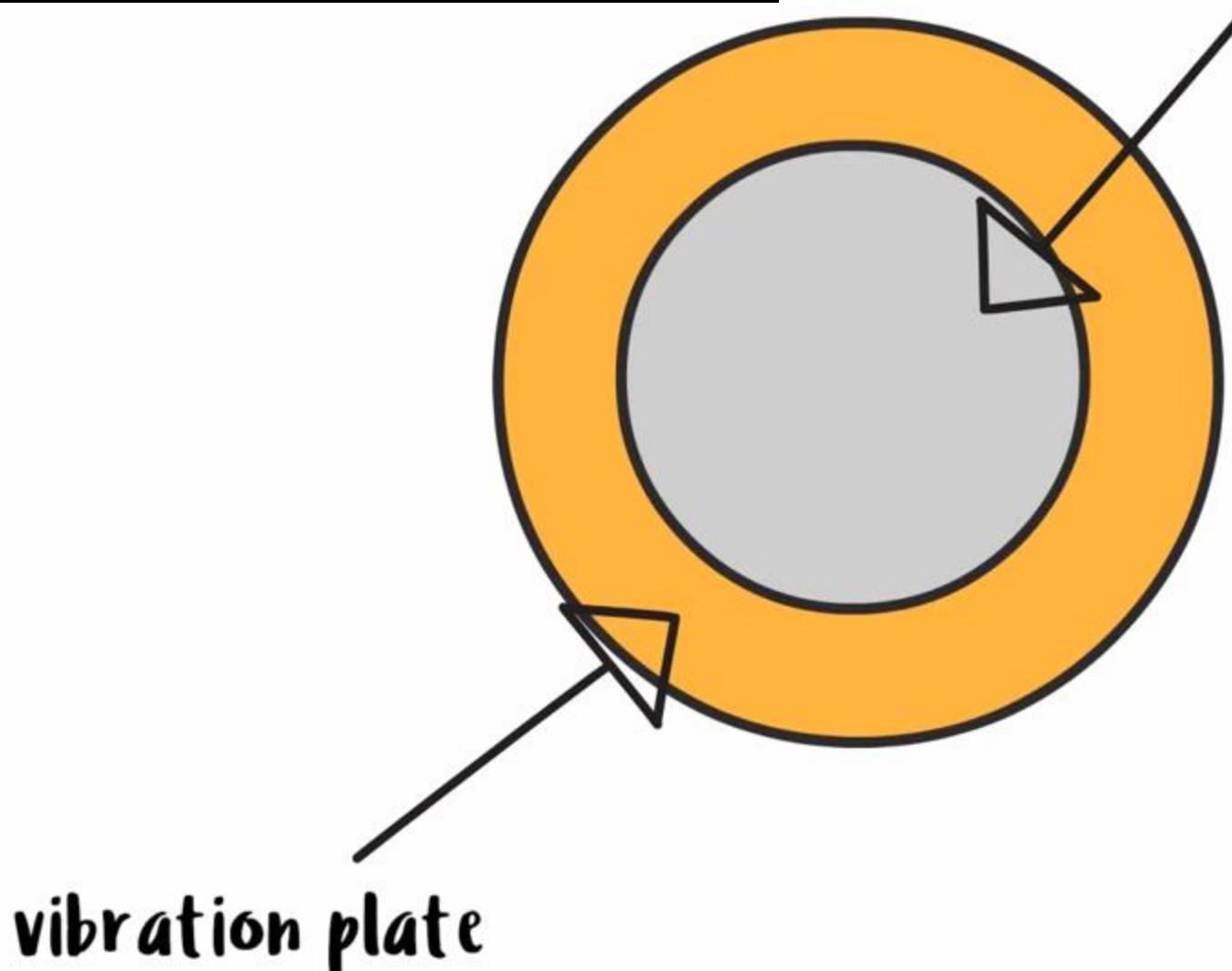


vibration plate

VIBRATION DISC.

Source: MakeCrate, <https://youtu.be/77h1JhD9Syw>

piezo ceramic element

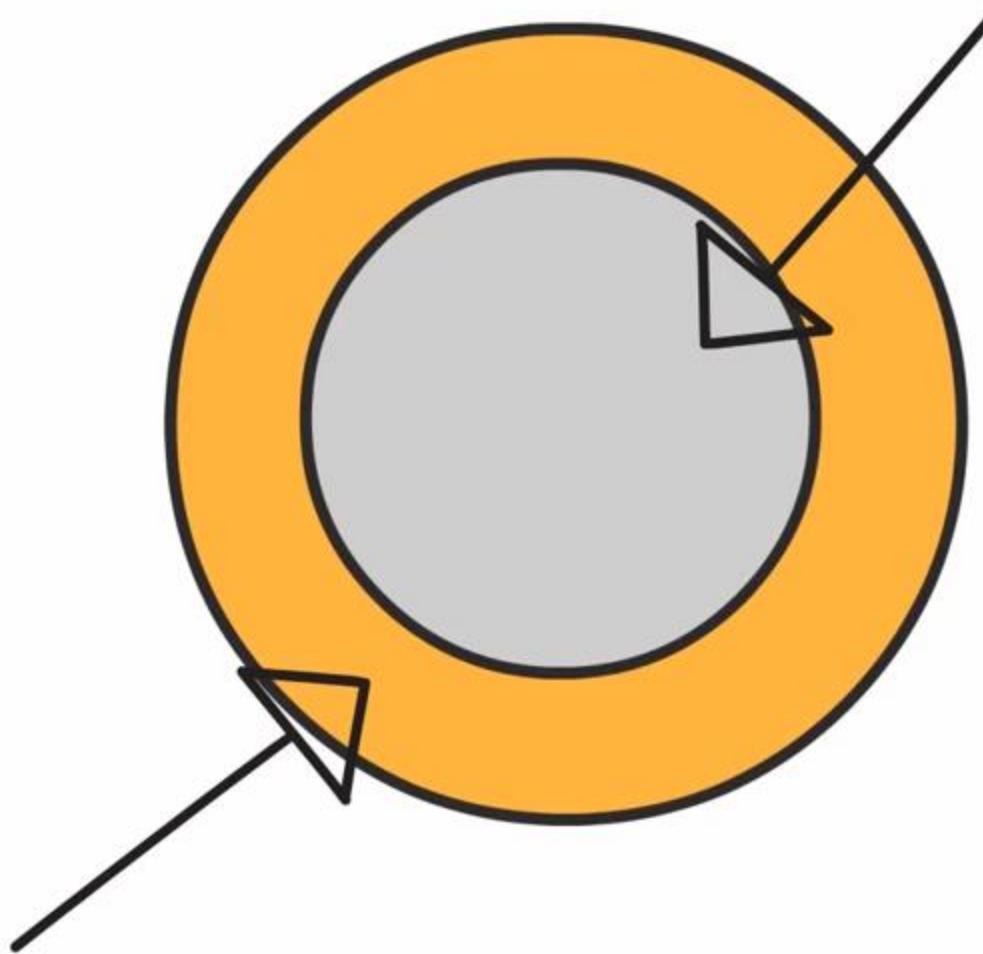

vibration plate

vibration disc.

GENERATE FREQUENCY: TONE()

Generates a square wave of the specified frequency on a pin. The duty cycle is fixed at 50%.

Syntax

`tone(pin, frequency)`

`tone(pin, frequency, duration)`

Parameters

`pin`: the pin on which to generate the tone

`frequency`: the frequency of the tone in hertz - unsigned int


`duration`: the duration of the tone in milliseconds (optional) - unsigned long

Returns


Nothing

TONE FUNCTION

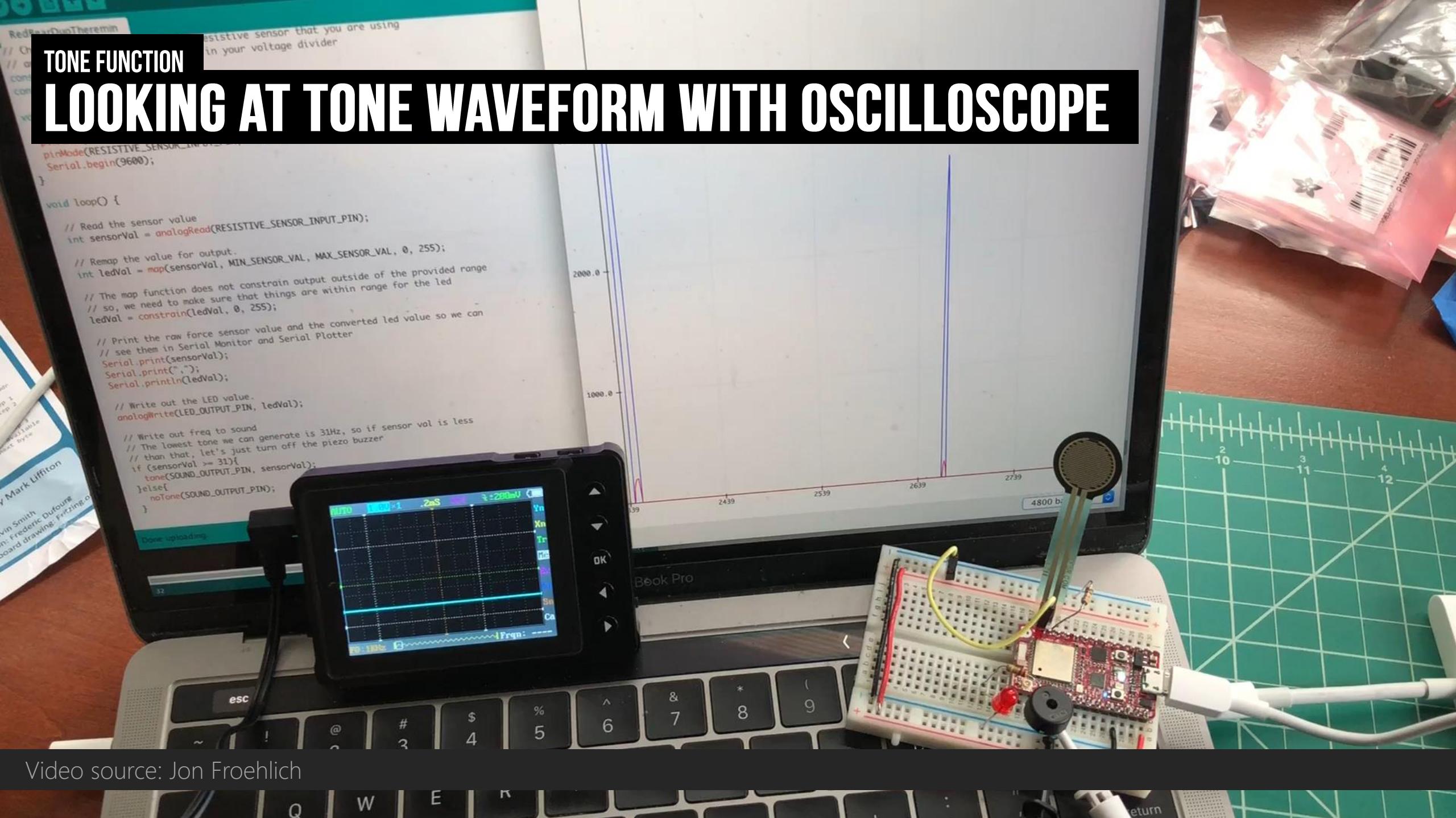LOOKING AT TONE WAVEFORM WITH OSCILLOSCOPE



Video source: Jon Froehlich

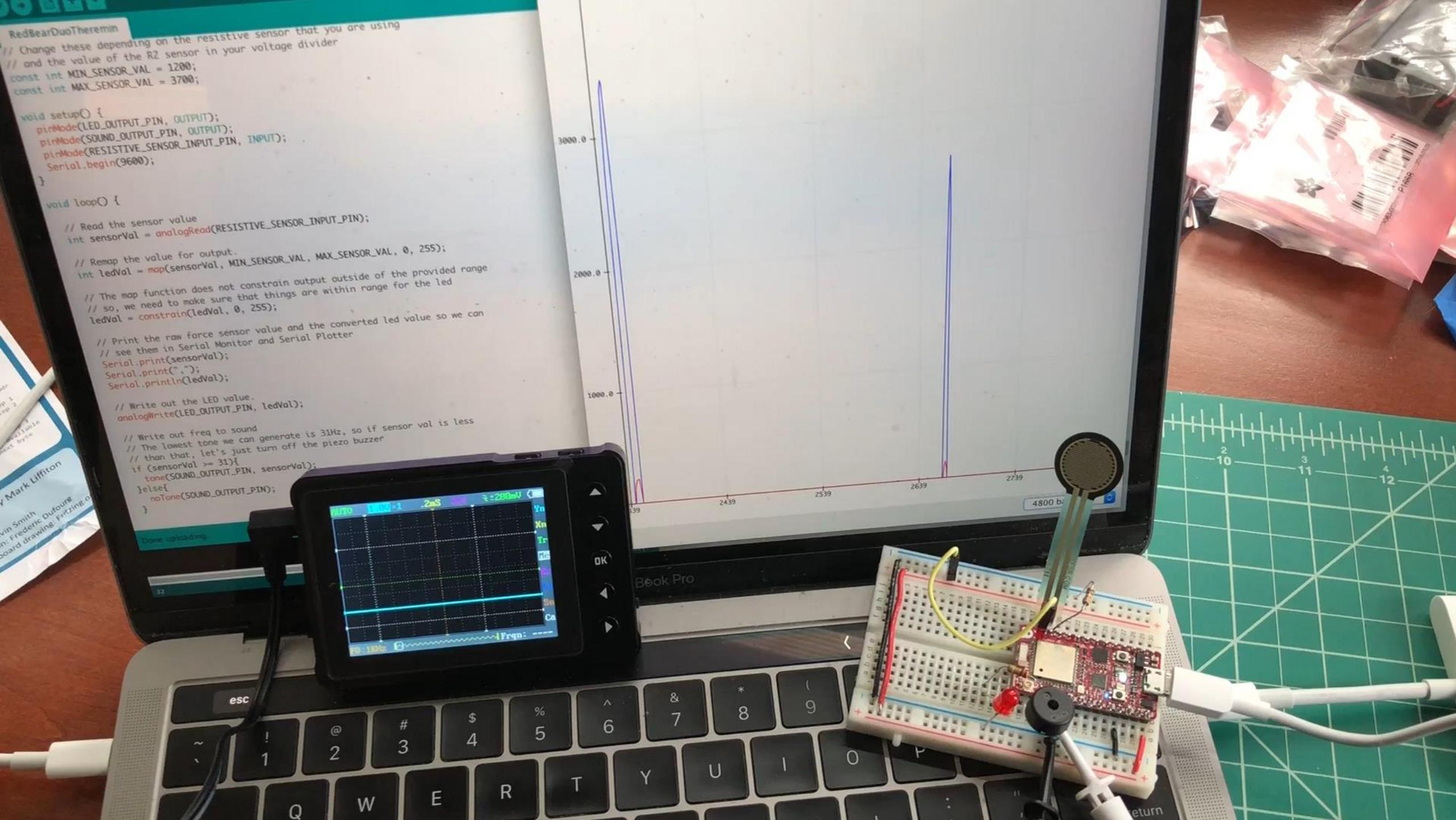

USING PIEZO BUZZER


EXERCISE: CREATE THEREMIN!

Add a piezoelectric buzzer to your circuit


Output tone proportional to variable resistor

USING PIEZO BUZZER

EXAMPLE SOLUTION

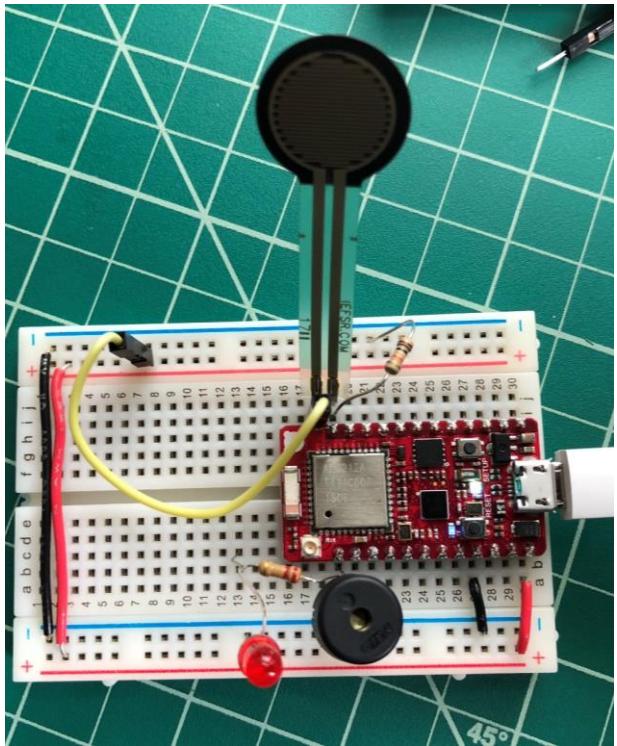
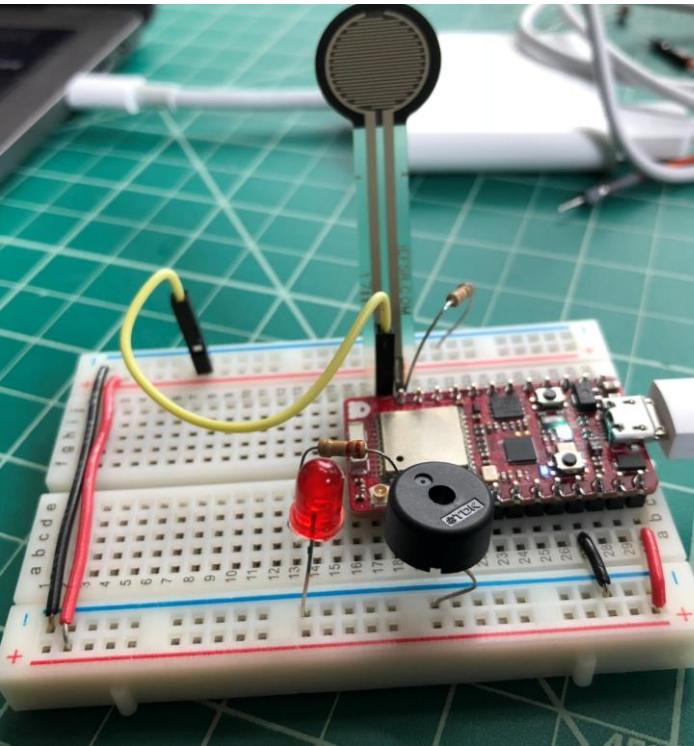
<https://github.com/jonfroehlich/CSE590Sp2018/tree/master/L06-Arduino/RedBearDuoTheremin>



```
RedBearDuoTheremin
SYSTEM_MODE(MANUAL);

const int LED_OUTPUT_PIN = D0;
const int SOUND_OUTPUT_PIN = D1;
const int RESISTIVE_SENSOR_INPUT_PIN = A0;

// Change these depending on the resistive sensor that you are using
// and the value of the R2 sensor in your voltage divider
const int MIN_SENSOR_VAL = 1200;
const int MAX_SENSOR_VAL = 3700;

void setup() {
    pinMode(LED_OUTPUT_PIN, OUTPUT);
    pinMode(SOUND_OUTPUT_PIN, OUTPUT);
    pinMode(RESISTIVE_SENSOR_INPUT_PIN, INPUT);
    Serial.begin(9600);
}

void loop() {

    // Read the sensor value
    int sensorVal = analogRead(RESISTIVE_SENSOR_INPUT_PIN);

    // Remap the value for output.
    int ledVal = map(sensorVal, MIN_SENSOR_VAL, MAX_SENSOR_VAL, 0, 255);

    // The map function does not constrain output outside of the provided range
    // so, we need to make sure that things are within range for the led
    ledVal = constrain(ledVal, 0, 255);

    // Print the raw force sensor value and the converted led value so we can
    // see them in Serial Monitor and Serial Plotter
    Serial.print(sensorVal);
    Serial.print(",");
    Serial.println(ledVal);

    // Write out the LED value.
    analogWrite(LED_OUTPUT_PIN, ledVal);

    // Write out freq to sound
    // The lowest tone we can generate is 31Hz, so if sensor val is less
    // than that, let's just turn off the piezo buzzer
    if (sensorVal >= 31){
        tone(SOUND_OUTPUT_PIN, sensorVal);
    }else{
        noTone(SOUND_OUTPUT_PIN);
    }

    delay(100);
}
```

ANALOG INPUT

PHOTOCELL “THEREMIN” DEMO




Video source: Jon Froehlich



One last thing before we move on: analog inputs tend to be **noisy**. To fix this, even a simple smoothing filter like a moving average will work nicely.


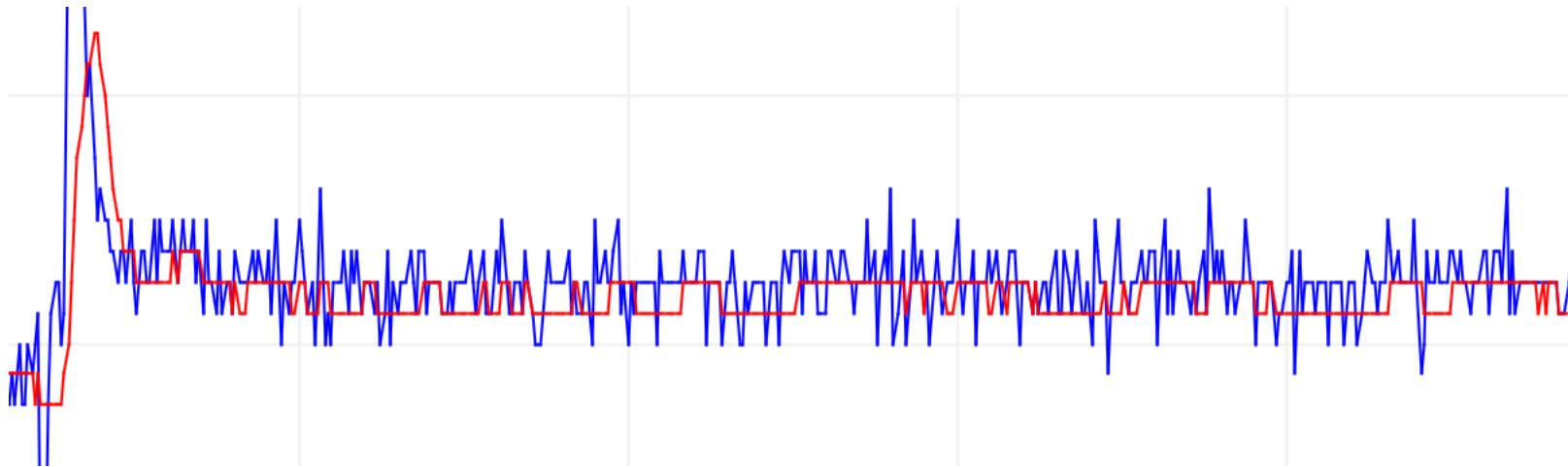
(Note: You also get “basic” smoothing when you compress values from a large range like 0-4096 to a small integer range like 0-255)



ANALOG INPUT

SMOOTHING THE SIGNAL

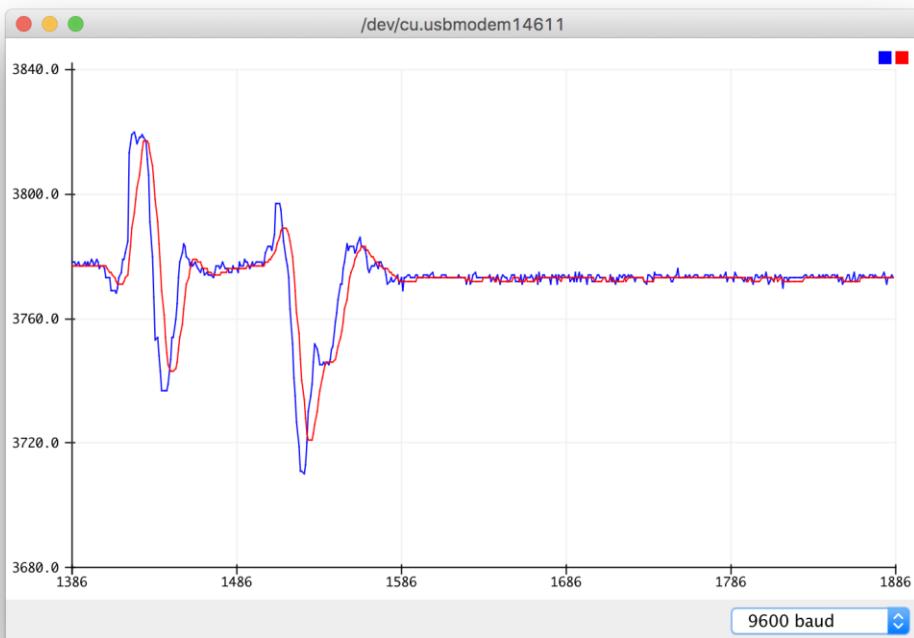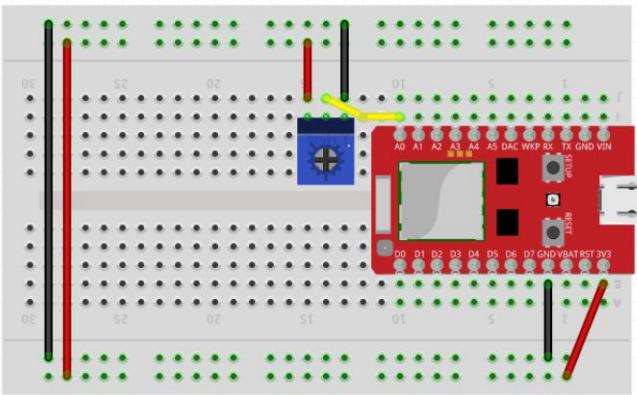Even a simple circuit with a potentiometer can be noisy



Basic sliding window mean filter

```
RedBearDuoSmoothing
SYSTEM_MODE(MANUAL);

// Define the smoothing window size
const int SMOOTHING_WINDOW_SIZE = 10;
const int ANALOG_INPUT_PIN = A0;

int _readings[SMOOTHING_WINDOW_SIZE]; // the readings from the analog input
int _readIndex = 0; // the index of the current reading
int _total = 0; // the running total
int _average = 0; // the average

void setup() {
    pinMode(ANALOG_INPUT_PIN, INPUT);
    // initialize serial communication with computer
    Serial.begin(9600);

    // initialize all the readings to 0
    for (int i = 0; i < SMOOTHING_WINDOW_SIZE; i++) {
        _readings[i] = 0;
    }
}

void loop() {
    // subtract the last reading
    _total = _total - _readings[_readIndex];

    // read from the sensor
    int curReading = analogRead(ANALOG_INPUT_PIN);
    _readings[_readIndex] = curReading;

    // add the reading to the total
    _total = _total + _readings[_readIndex];

    // advance to the next position in the array...
    _readIndex = _readIndex + 1;

    // if we're at the end of the array...
    if (_readIndex >= SMOOTHING_WINDOW_SIZE) {
        // ...wrap around to the beginning:
        _readIndex = 0;
    }

    // calculate the average
    _average = _total / SMOOTHING_WINDOW_SIZE;

    // send it to the computer as ASCII digits
    Serial.print(curReading);
    Serial.print(",");
    Serial.println(_average);

    delay(50); // delay in between reads for stability
}
```

<https://github.com/jonfroehlich/CSE590Sp2018/tree/master/L06-Arduino/RedBearDuoSmoothing>

WORKING WITH SENSORS: LEARNING GOALS

How to use variable **resistive sensors**, including **voltage dividers**,
basic **signal smoothing**

Putting it together: **making a simple theremin**


How to use **buttons**, including **pull-up** and **pull-down resistors**,
and **debouncing**

Working with **interrupts**


INPUT

DIGITAL INPUT

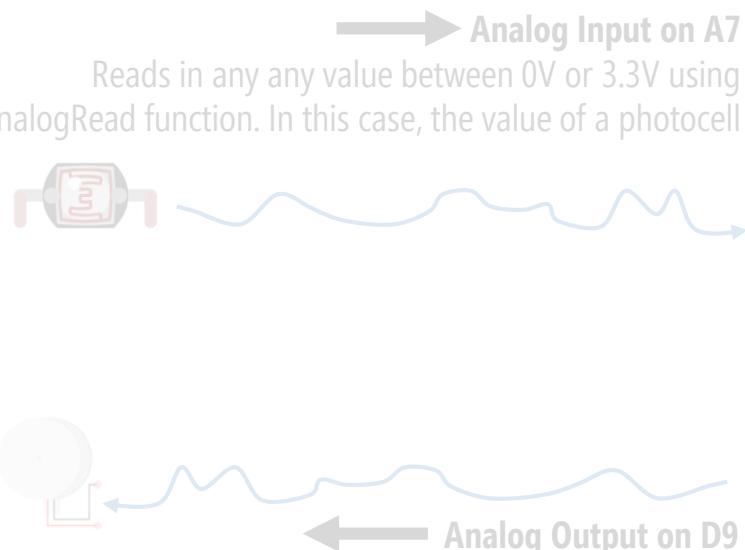We went over this in the last lecture (L05-PhysicalComputing2-Arduino.pptx) but here's a quick review



VIN	
GND	
TX	D17
RX	D16
A7	D15
A6	D14
A5	D13
A4	D12
A3	D11
A2	D10
A1	D9
A0	D8

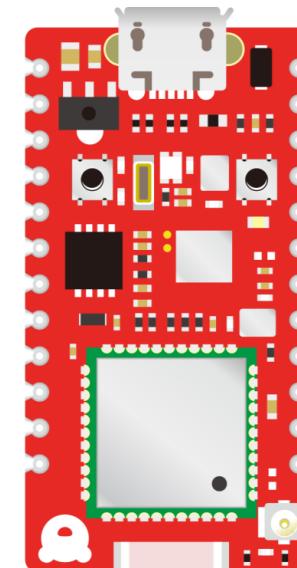

3.3V	
RST	
VBAT	
GND	
D7	
D6	
D5	
D4	
D3	
D2	
D1	
D0	

← **Digital Input on D7**
Reads in a digital input signal (anything below 1.65V converted to LOW, anything above 1.65V converted to HIGH). In this case, the value of switch.




→ **Digital Output on D0**
Writes out 0V or 3.3V using digitalWrite function. In this case, turning on and off an LED.



DIGITAL INPUT

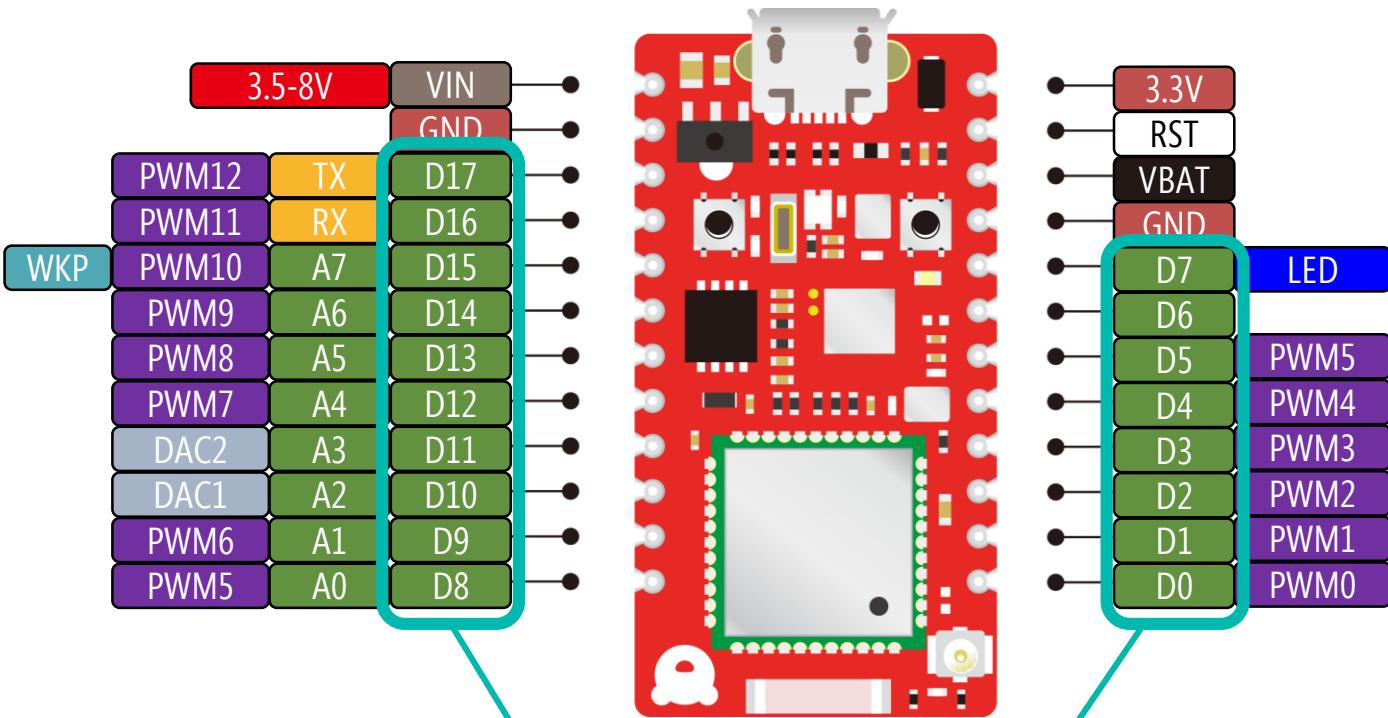ANY OF THE D PINS CAN BE SET FOR DIGITAL INPUT OR OUTPUT



Legend

- AX Analog Input Pin
- DX Digital Input/output Pin
- PWM Supports Analog Out via Pulse Width Modulation

Any of the D pins can be set for input or output
in setup() using pinMode()

DIGITAL INPUT

SWITCHES


Switches are a common form of digital input. There is variety of switches from toggle to rotary to DIP to push-button to DIP to rocker. Switches differ in how they are actuated and how many circuits they can control



SWITCHES: MOMENTARY VS. MAINTAINED



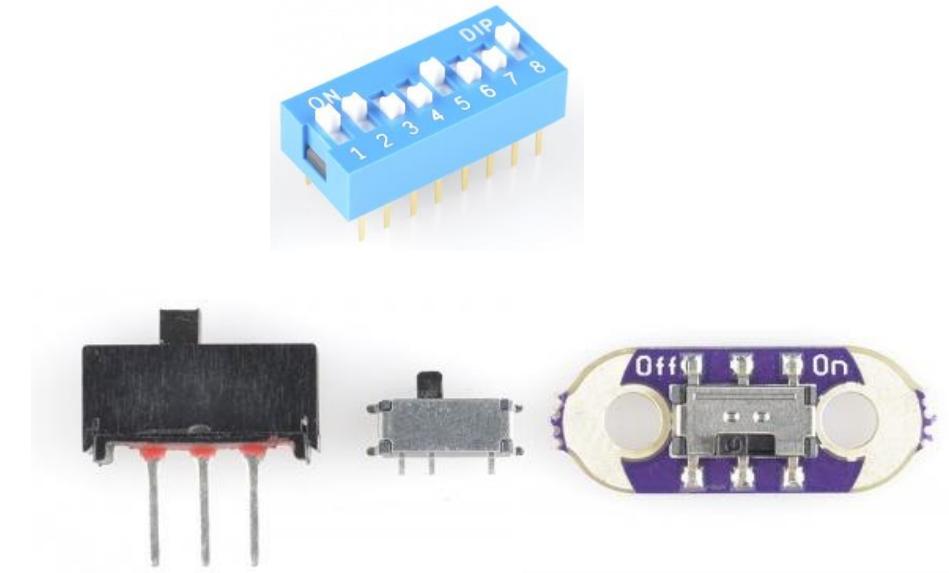Momentary: remain active only as long as they are actuated (e.g., keys on a keyboard, buttons)




Maintained: Stay in one state until actuated into a new one (e.g., light switches, DIP switches)

Let's design a circuit & write code to
turn **on** and **off** an **LED** with a **button**.

DIGITAL INPUT




TURN ON/OFF LED WITH A BUTTON

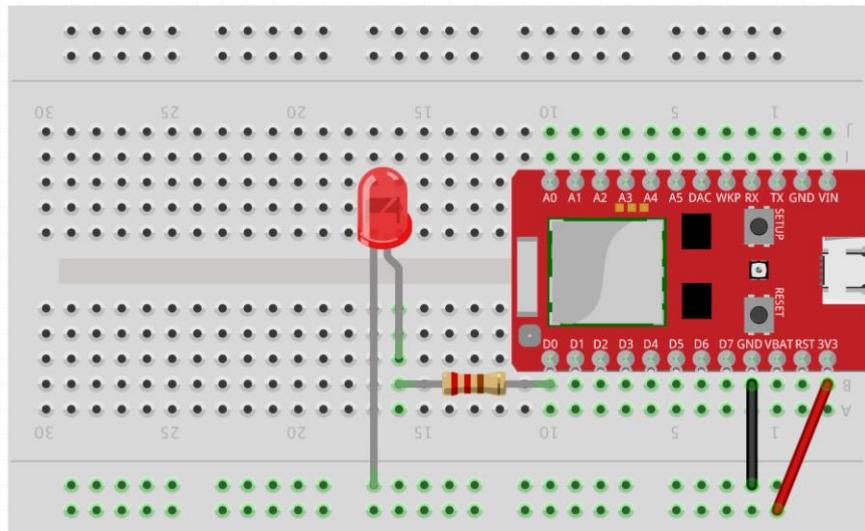Basic Circuit: Control LED via the D0 pin



How do we know how to hook up this button? It has **four legs**.

New Circuit: Control LED via a button

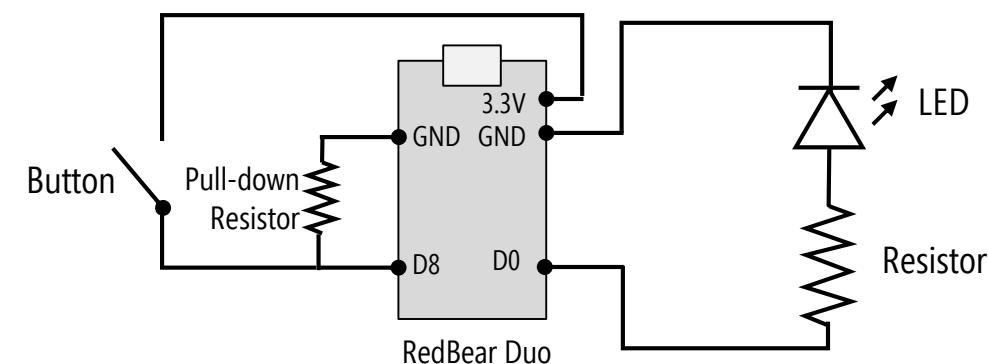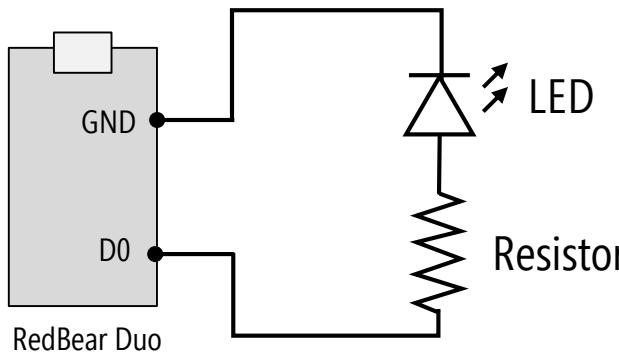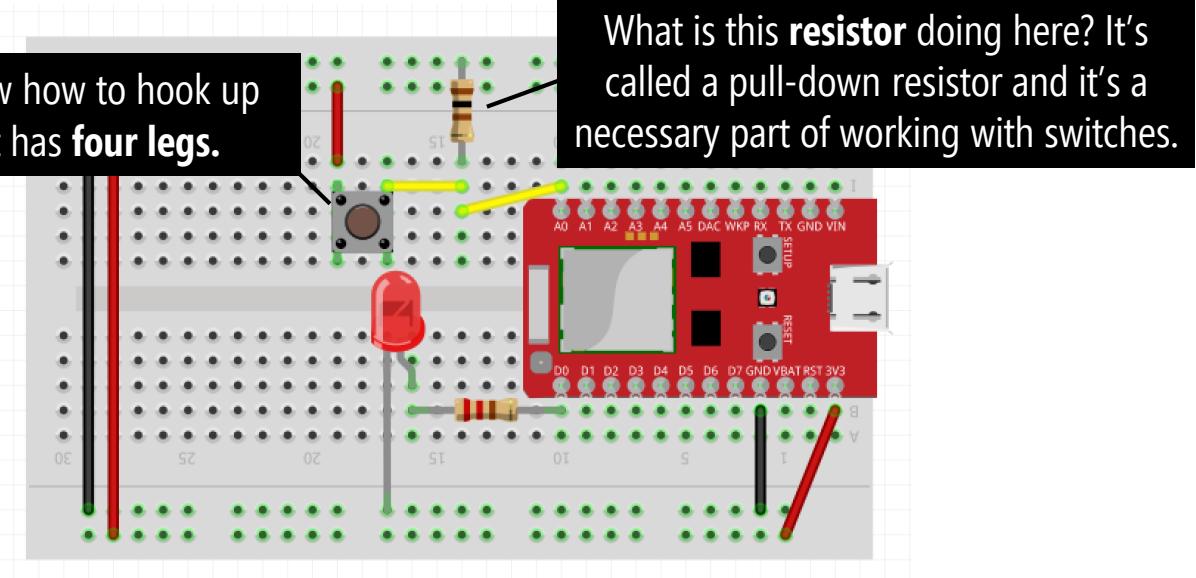

DIGITAL INPUT

HOOKING UP BUTTON: CONSULT THE DATASHEET

OMRON

**Tactile Switch
B3F**

Miniature, Space-Saving Tactile Switch
Provides Long Service Life and Easy Mounting

Extended mechanical/electrical service life: 10×10^6 operations for 12×12 mm type and 1×10^6 operations for the 6×6 mm type

- Ideal for applications such as audio, office and communications equipment, measuring instruments, TVs, VCRs, etc.
- Taped radial type, vertical type and high force types are available as series versions
- Flux-tight base structure allows automatic soldering of the tactile switches onto a PC board
- Gold plated models available for increased contact reliability, resistance to corrosive gas and insulation fault prevention for ion migration in harsh environments
- RoHS Compliant

Ordering Information


■ B3F-1□□□, B3F-3□□□

6 x 6 mm type



Type	Plunger	Switch height x pitch	Operating force	Model	
				Without ground terminal With ground terminal	
				Bags Sticks* Bags Sticks*	
Standard	Flat	4.3 x 6.5 mm	General-purpose: 100 g	B3F-1000 B3F-1000S B3F-1100 B3F-1100S	
			High-force: 150 g	B3F-1002 B3F-1002S B3F-1102 B3F-1102S	
		5.0 x 6.5 mm	General-purpose: 100 g	B3F-1005 B3F-1005S B3F-1105 B3F-1105S	
	High-force: 260 g		B3F-1008 B3F-1008S B3F-1108 B3F-1108S		
	Projected	5.0 x 7.5 mm	General-purpose: 100 g	B3F-1020 B3F-1020S B3F-1120 B3F-1120S	
			High-force: 150 g	B3F-1022 B3F-1022S B3F-1122 B3F-1122S	
		7.3 x 6.5 mm	General-purpose: 100 g	B3F-1025 B3F-1025S B3F-1125 B3F-1125S	
	Vertical	Flat	3.15 mm	General-purpose: 100 g	B3F-1050 B3F-1050S B3F-1150 B3F-1150S
				High-force: 150 g	B3F-1052 B3F-1052S B3F-1152 B3F-1152S
Projected		3.85 mm	General-purpose: 100 g	B3F-1055 B3F-1055S B3F-1155 B3F-1155S	
	High-force: 260 g		— — — —		
	Flat	6.15 mm	General-purpose: 100 g	B3F-3100 B3F-3102 — —	
High-force: 150 g			B3F-3105 B3F-3107 — —		
Projected		260 g	B3F-3120 B3F-3122 — —		
	General-purpose: 100 g	B3F-3125 B3F-3127 — —			
* Number of switches per stick:				Without ground terminal 90/stick	
				With ground terminal 75/stick	

Important Note: Switches cannot be water-washed.

1128 Tactile Switch B3F

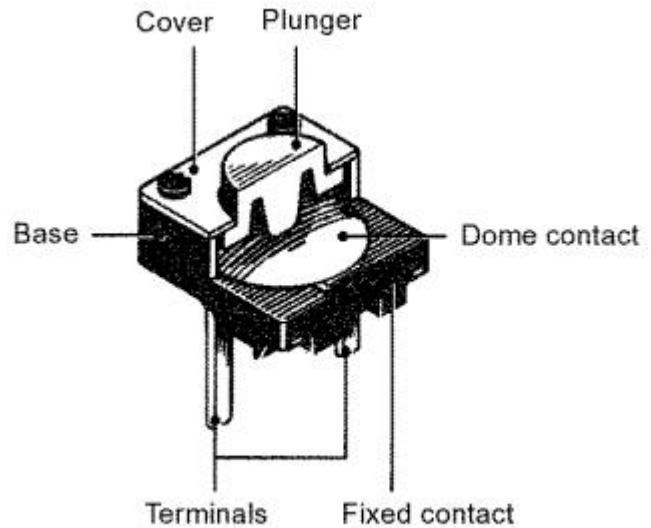

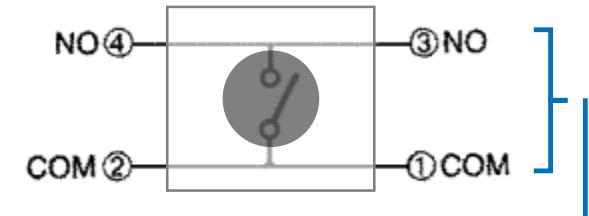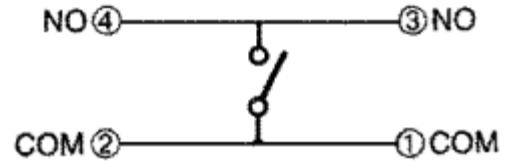
These two sides
become connected
when button is
pressed down



These two sides
become connected
when button is
pressed down

DIGITAL INPUT

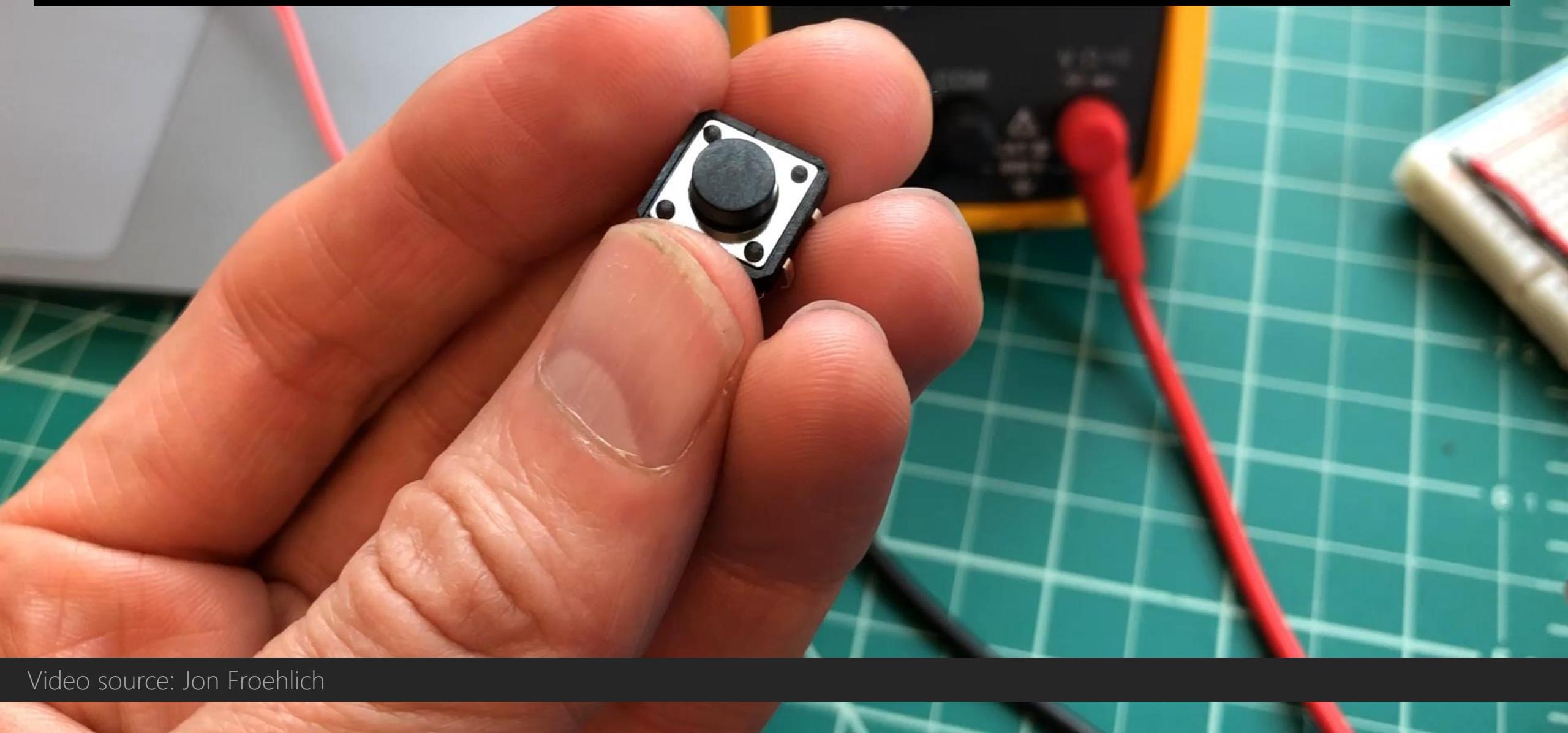
WHICH LEGS FORM A CONNECTION WHEN BUTTON PRESSED?






HOOKING UP A BUTTON: PULL-DOWN RESISTORS

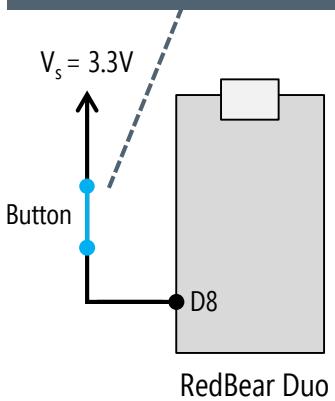When this button is closed (as it is below), what would the **microcontroller** (MCU) **read** from the **input pin**?




Answer: The MCU would read 3.3V (or HIGH)

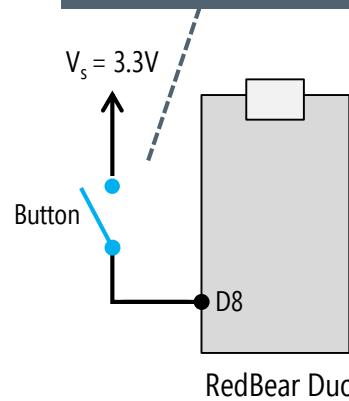Now, when the **button switches to open**, what would the MCU read?




Answer: Uh, oh, the input pin is in an unknown state (commonly called "floating")—this is bad!

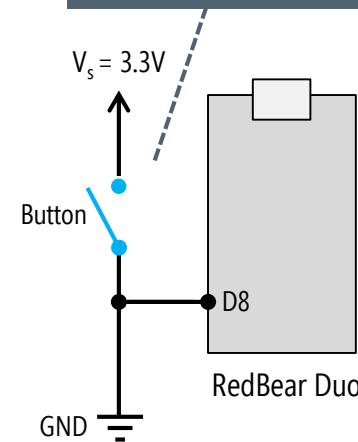Well, can't we just solve that by **adding GND** here that "pulls" D8 to 0V when the switch is open?



Answer: You're on the right track but this will create a short circuit when the button is closed!

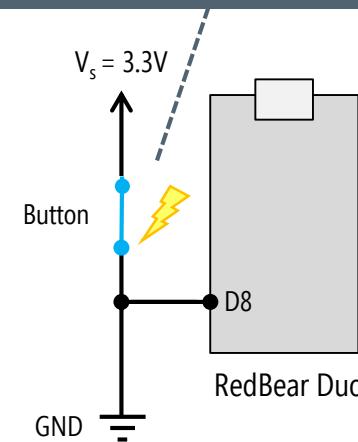
Now, when the button is closed, we have a **short circuit** (V_s is connected to GND). This could damage our power supply, circuit components, etc.)!



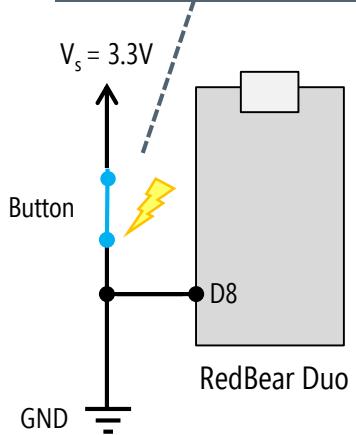Question: So, what do we do? We add what's called a pull-down resistor.


HOOKING UP A BUTTON: PULL-DOWN RESISTORS

Now, when the button is closed, we have a **short circuit** (V_s is connected to GND. This could damage our MCU)!



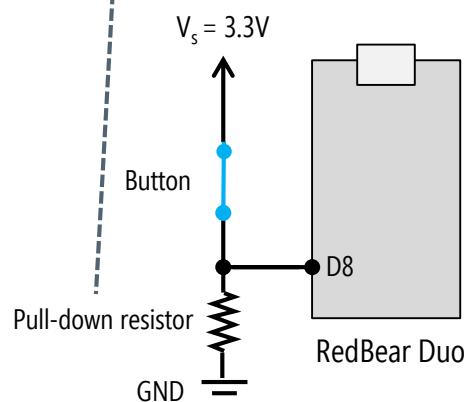Question: So, what do we do?
We add what's called a pull-down resistor.

This resistor is called a "**pull-down resistor**" because it biases the input low (to GND) when the switch is open.



Now, when the switch is open,
the MCU is pulled to GND.
When the switch is closed, the
MCU is 3.3V (HIGH).


How do you choose the resistor value for the pull-down?

If you choose a low resistor value, more current will be “wasted” by flowing from V_s to GND when the button is closed. In contrast, a high resistor value (e.g., $4M\Omega$) may not work as a pull-down (not enough current will flow).

Arduino recommends using a $10K\Omega$ resistor.

PULL-DOWN VS. PULL-UP RESISTORS

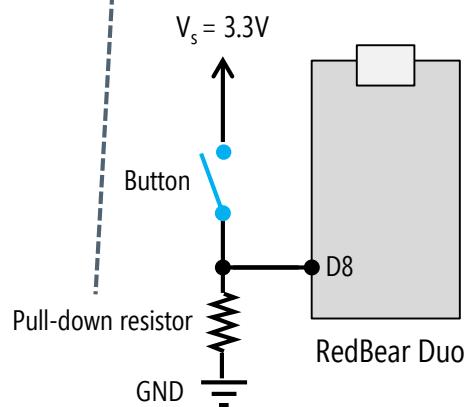
This resistor is called a “**pull-down resistor**” because it biases the input low (to GND) when the switch is open.



Pull-Down Resistor Configuration

When the switch is open, the MCU is pulled to GND. When the switch is closed, the MCU is 3.3V (HIGH) as it becomes directly connected to V_s .

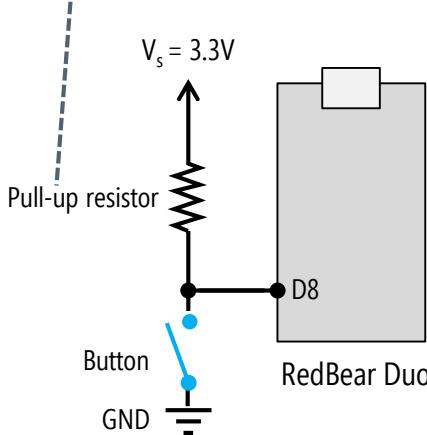This resistor is called a “**up resistor**” because it biases the input high (to V_s) when the switch is open.



Pull-Up Resistor Configuration

When the switch is open, the MCU is pulled to V_s . When the switch is closed, the MCU is 0V (LOW) as it becomes directly connected to GND.

You can wire up either pull-down resistor configurations or pull-up resistor configurations.


I have a preference towards pull-down resistors because it makes more sense to me that a switch is 0V (LOW) when open and 3.3 (HIGH) when closed.


DIGITAL INPUT

VIDEO DEMONSTRATING PULL-DOWN VS. PULL-UP RESISTORS

Pull-down resistor configuration.
When button is **not pressed**, the input signal is LOW. When **pressed**, the input signal goes HIGH.

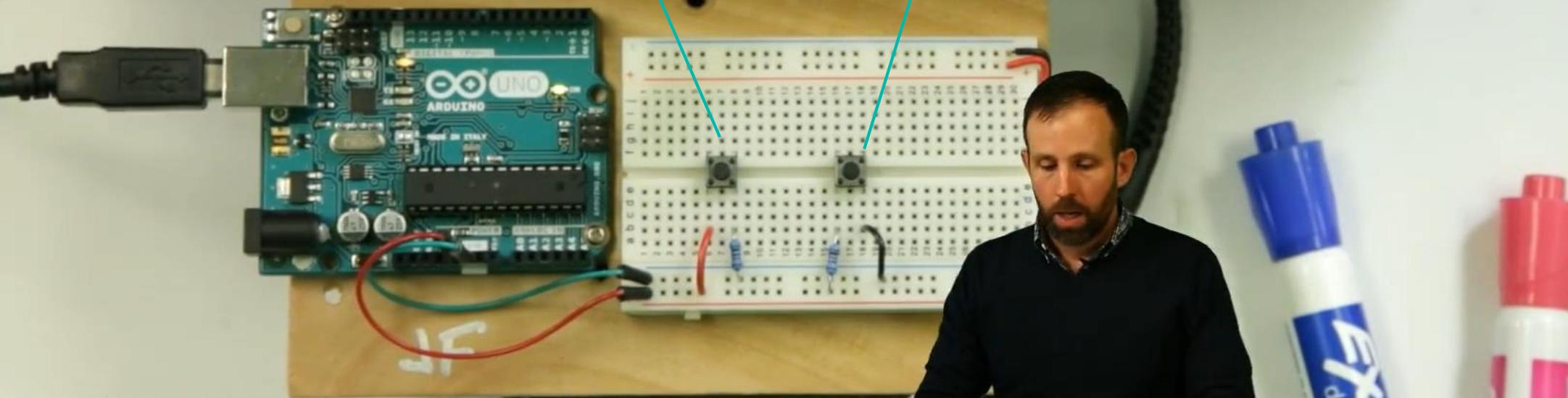Pull-up resistor configuration.
When button is **not pressed**, the input signal is HIGH. When **pressed**, the input signal goes LOW.



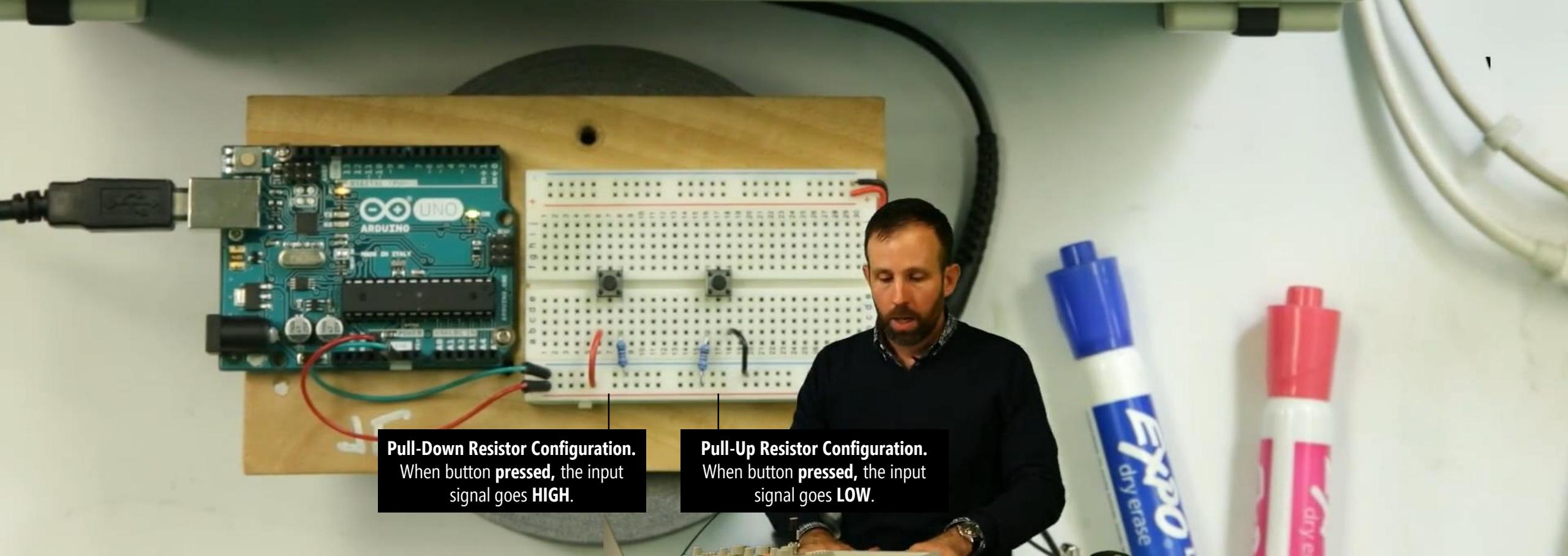

EXERCISE: TURN ON/OFF LED WITH A BUTTON

Build circuit and write code to turn on/off button

Use a pull-down resistor

Use the digitalRead method

ACTIVITY: LEARN DIGITAL INPUT

digitalRead()

Reads the value from a specified digital ping and returns either HIGH or LOW

Syntax

```
digitalRead(pin)
```

Parameters

pin: the digital I/O pin you want to read

Returns

HIGH or LOW

EXERCISE: TURN ON/OFF LED WITH A BUTTON


Build circuit and write code to turn on/off button

Use a pull-down resistor


DIGITAL INPUT

TURN ON/OFF LED WITH A BUTTON

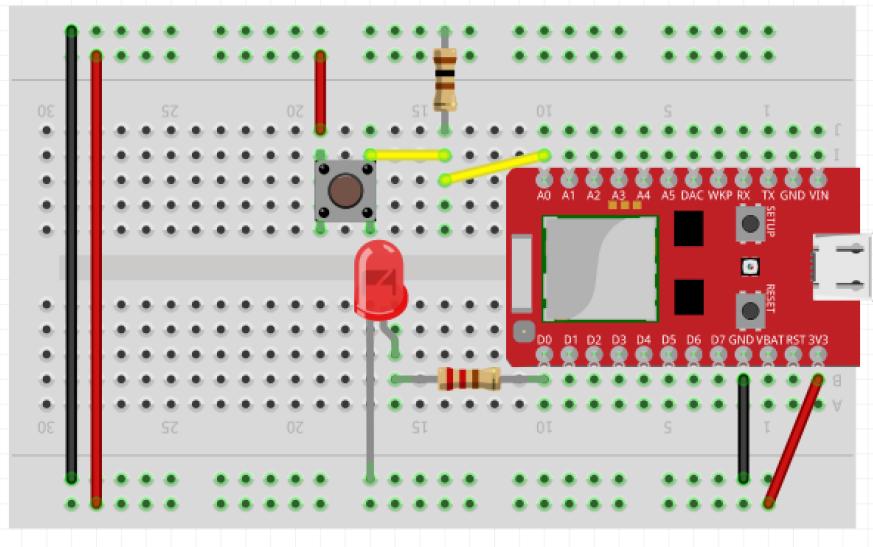Circuit: Control LED via a button & pull-down resistor




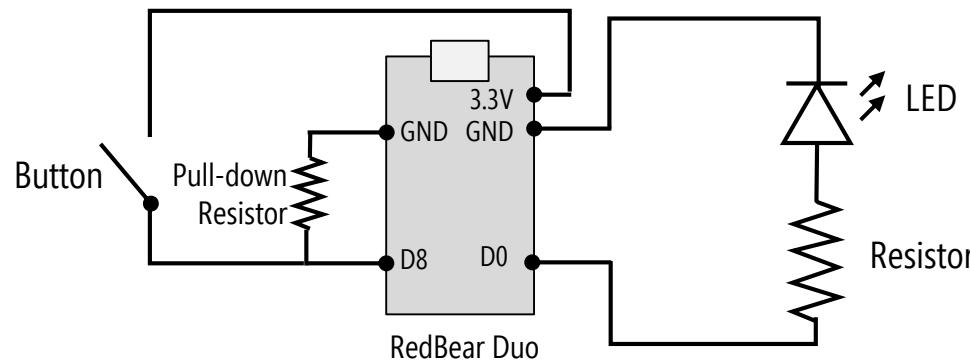
Now we just have to write the Arduino code to read in the button state and turn on/off the LED accordingly.



DIGITAL INPUT

TURN ON/OFF LED WITH A BUTTON

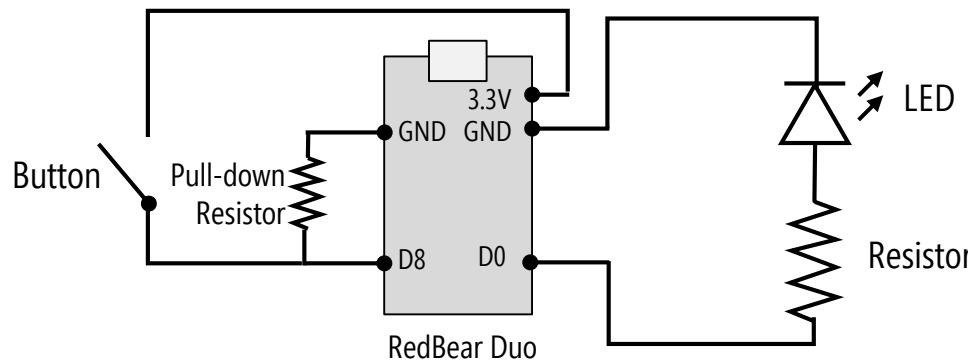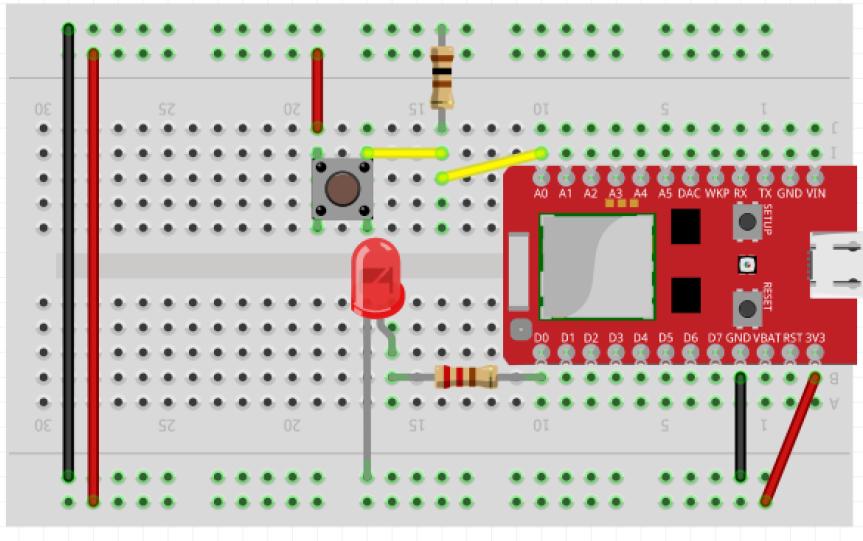Circuit: Control LED via a button & pull-down resistor



Code: Read button state and set LED on/off accordingly

```
RedBearDuoReadButtonSetLED | Arduino 1.8.5
File Edit Sketch Tools Help
RedBearDuoReadButtonSetLED §
/*
 * This example reads in a button input on D8 (with a pull-down resistor configuration)
 * and turns on/off an LED on D0 accordingly
 *
 * By Jon Froehlich for CSE590
 * http://makeabilitylab.io
 */
SYSTEM_MODE(MANUAL);

const int LED_OUTPUT_PIN = D0;
const int BUTTON_INPUT_PIN = D8;

void setup() {
  pinMode(LED_OUTPUT_PIN, OUTPUT);
  pinMode(BUTTON_INPUT_PIN, INPUT);
  Serial.begin(9600);
}


void loop() {

  // read the button value. It will be HIGH when pressed and
  // LOW when not pressed
  int buttonVal = digitalRead(BUTTON_INPUT_PIN);

  // Write out HIGH or LOW
  digitalWrite(LED_OUTPUT_PIN, buttonVal);


  // Check for new input every 100ms
  delay(100);
}
```
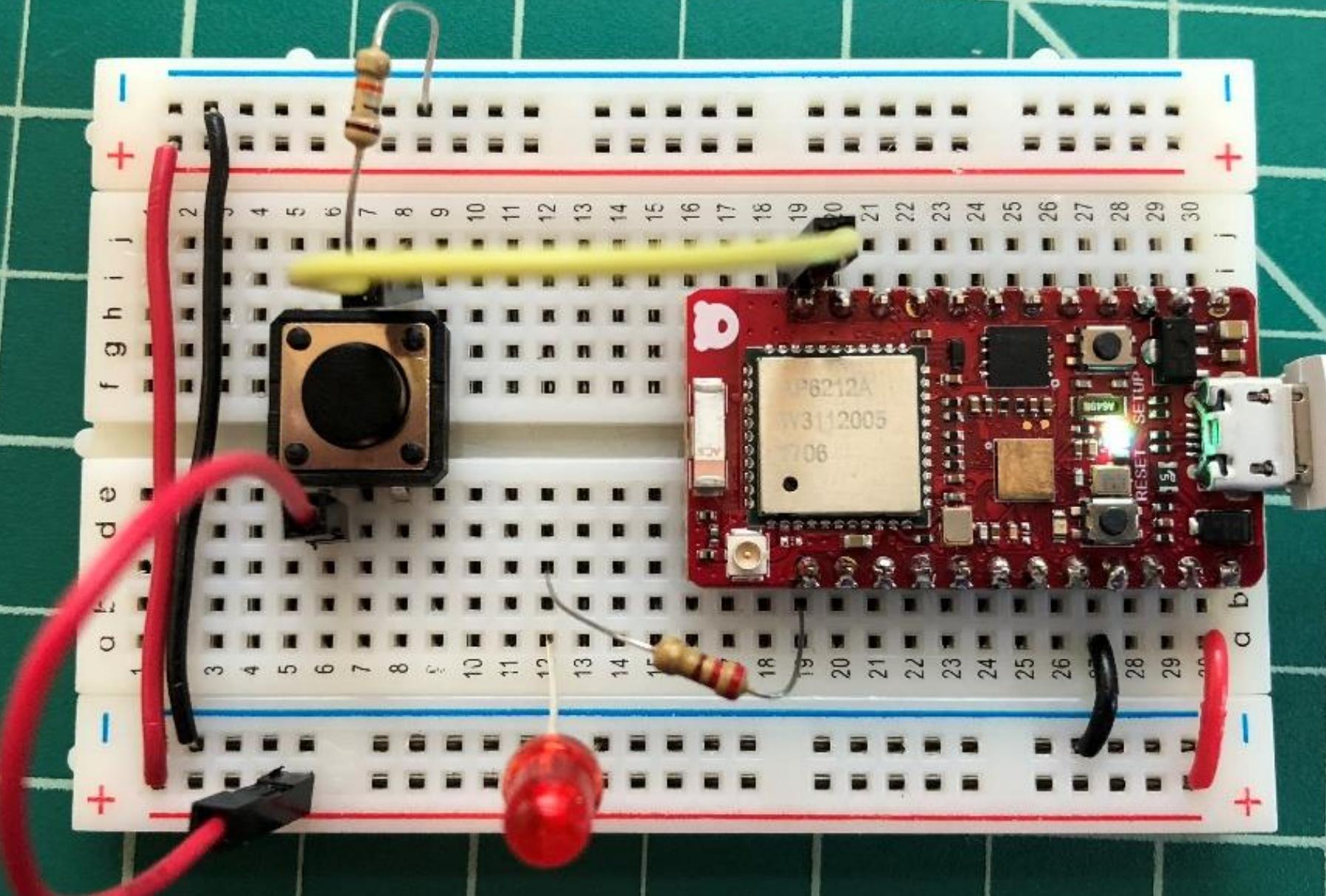
<https://github.com/jonfroehlich/CSE590Sp2018/tree/master/L05-Arduino/RedBearDuoReadButtonSetLED>




DIGITAL INPUT

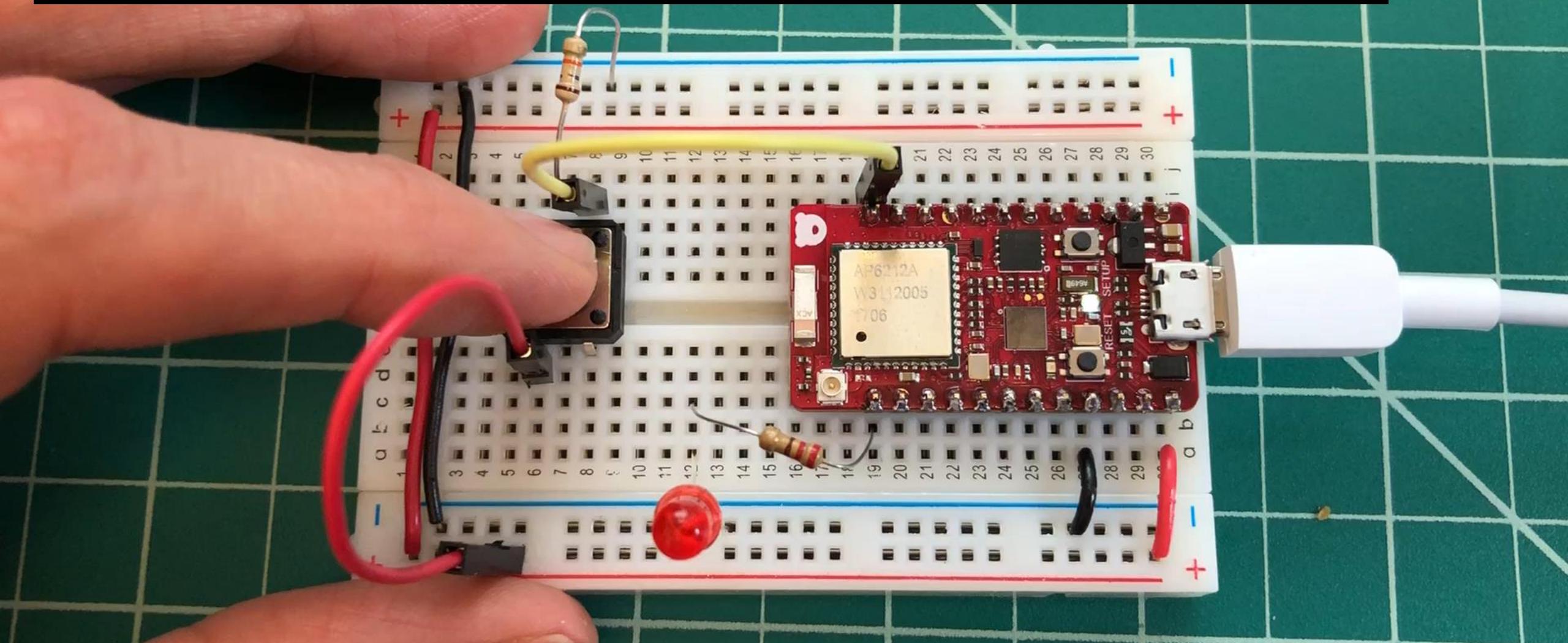DEMONSTRATION OF BUTTON WITH PULL-DOWN RESISTOR




Video source: Jon Froehlich

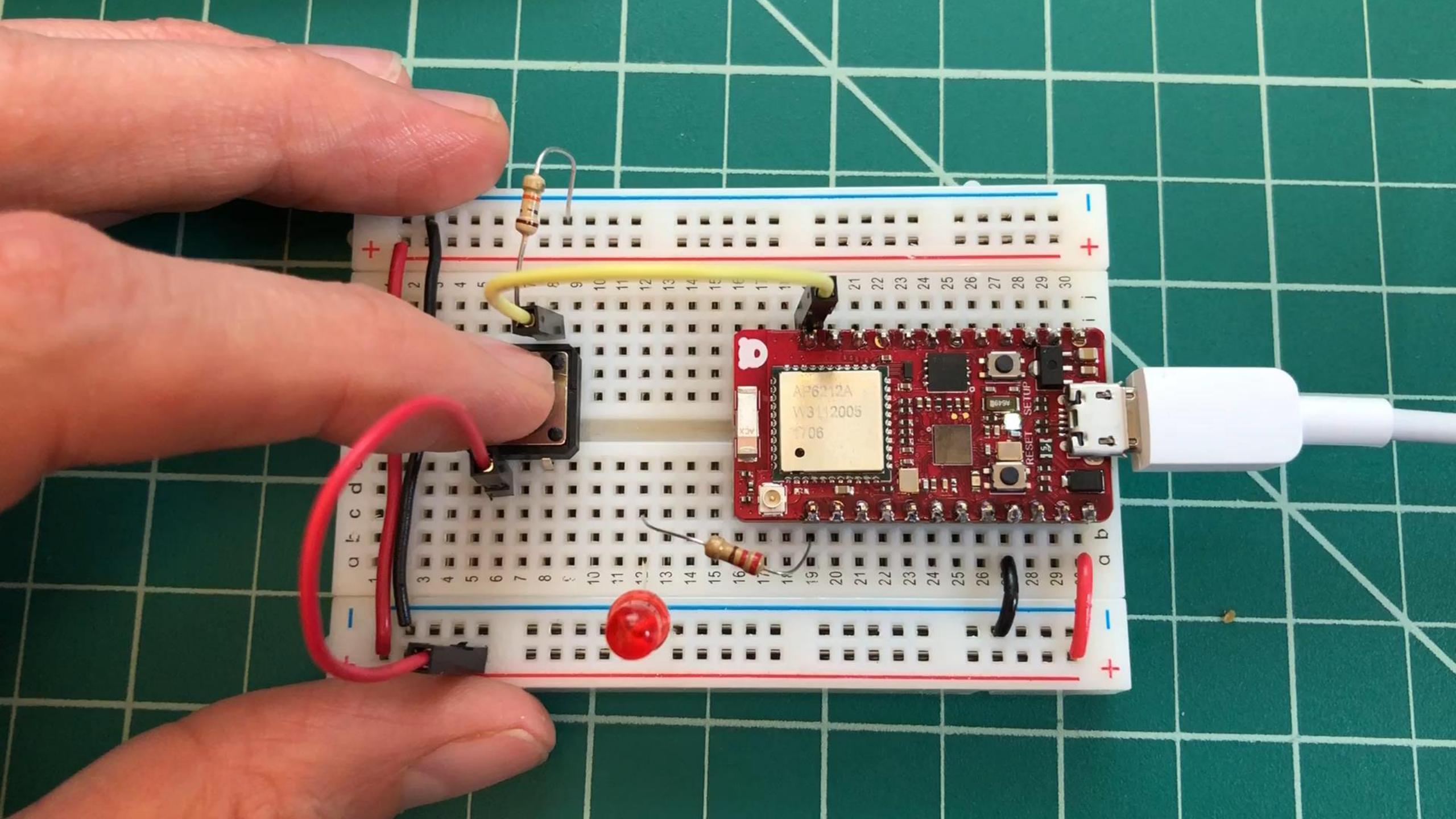

MANY MCUS HAVE THESE RESISTORS BUILT IN

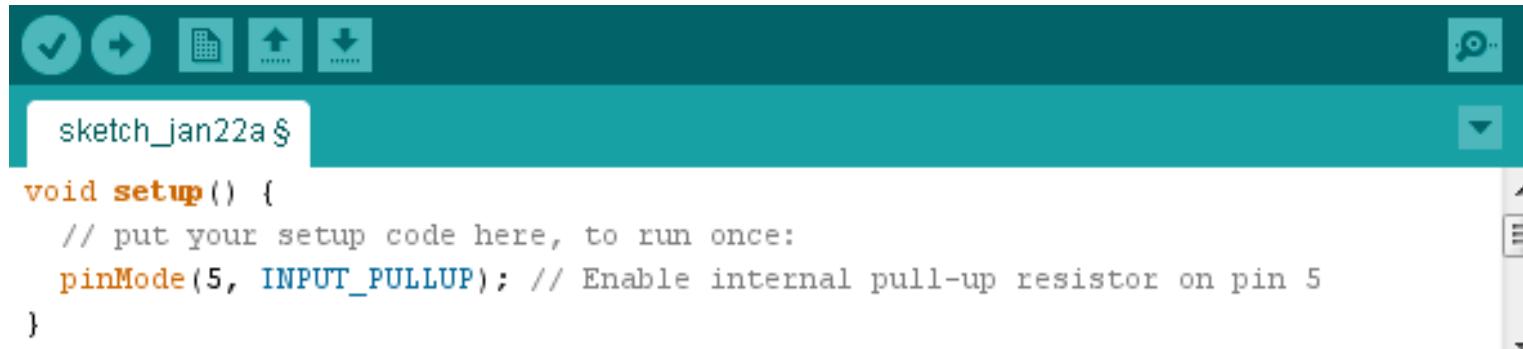Pull-up and pull-down resistors are so commonly needed that many MCUs have them built-in. The ATmega328 microcontroller on the Arduino Uno has internal pull-up resistors ($20\text{k}\Omega$). The RedBear Duo has both internal pull-up and pull-down resistors!




The image shows a screenshot of the Arduino IDE. The top menu bar includes File, Edit, Tools, Sketch, Help, and a language selection dropdown. Below the menu is a toolbar with icons for Save, Run, Open, Upload, Download, and a Print icon. The central workspace contains a code editor with the following text:

```
sketch_jan22a.ino
void setup() {
    // put your setup code here, to run once:
    pinMode(5, INPUT_PULLUP); // Enable internal pull-up resistor on pin 5
}
```




DIGITAL INPUT

MODIFY YOUR CIRCUIT TO USE INTERNAL PULL-DOWN

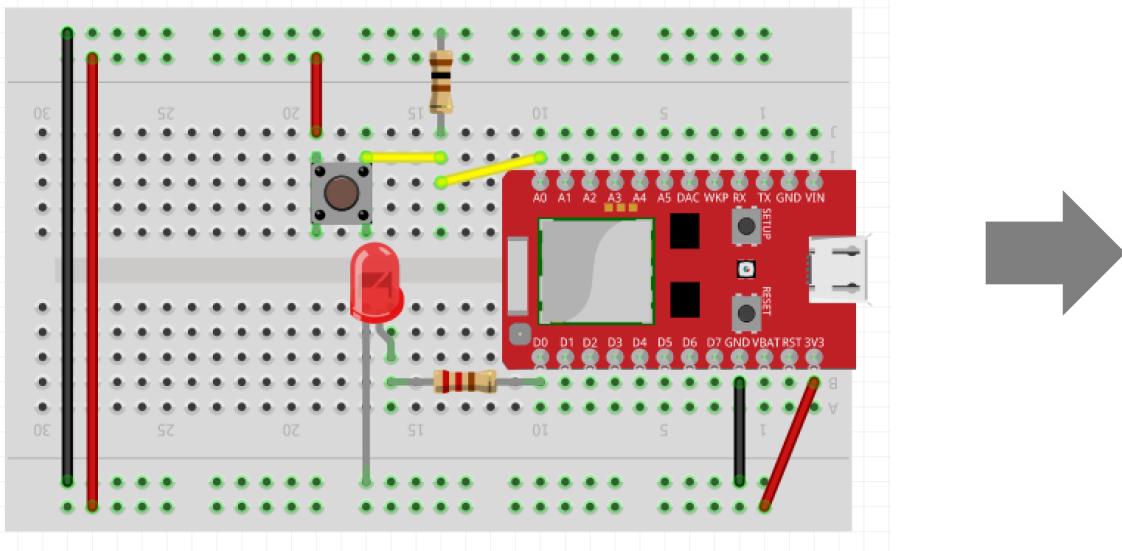Old Circuit: Control LED via a button & pull-down resistor



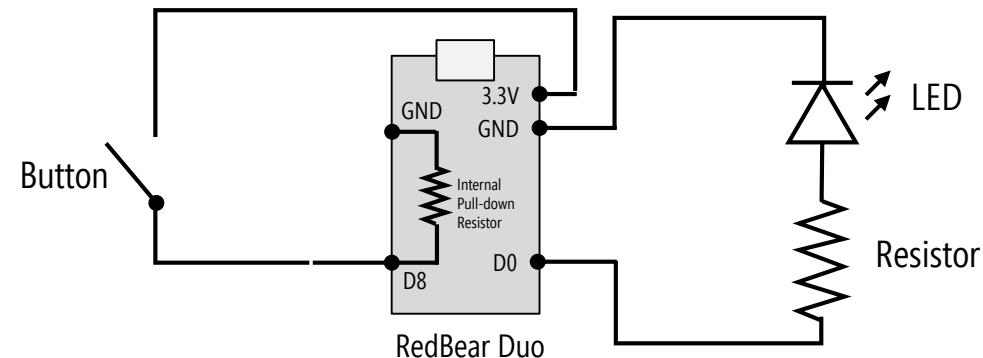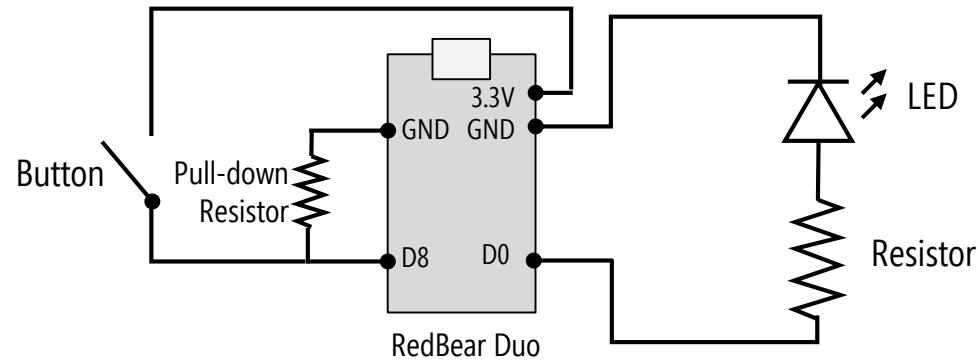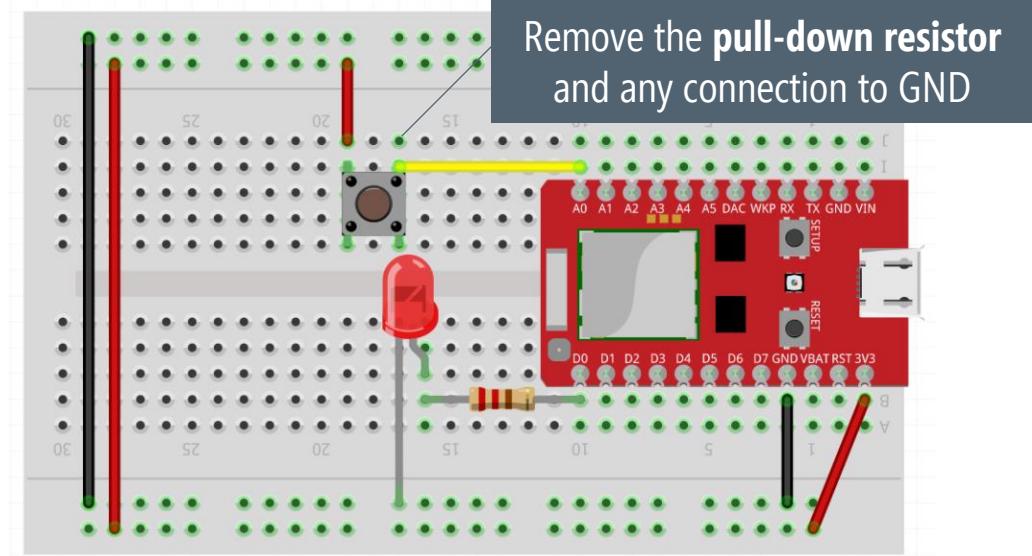
New Circuit: Control LED via a button & internal pull-down resistor



DIGITAL INPUT

MODIFY CODE TO USE INTERNAL PULL-DOWN

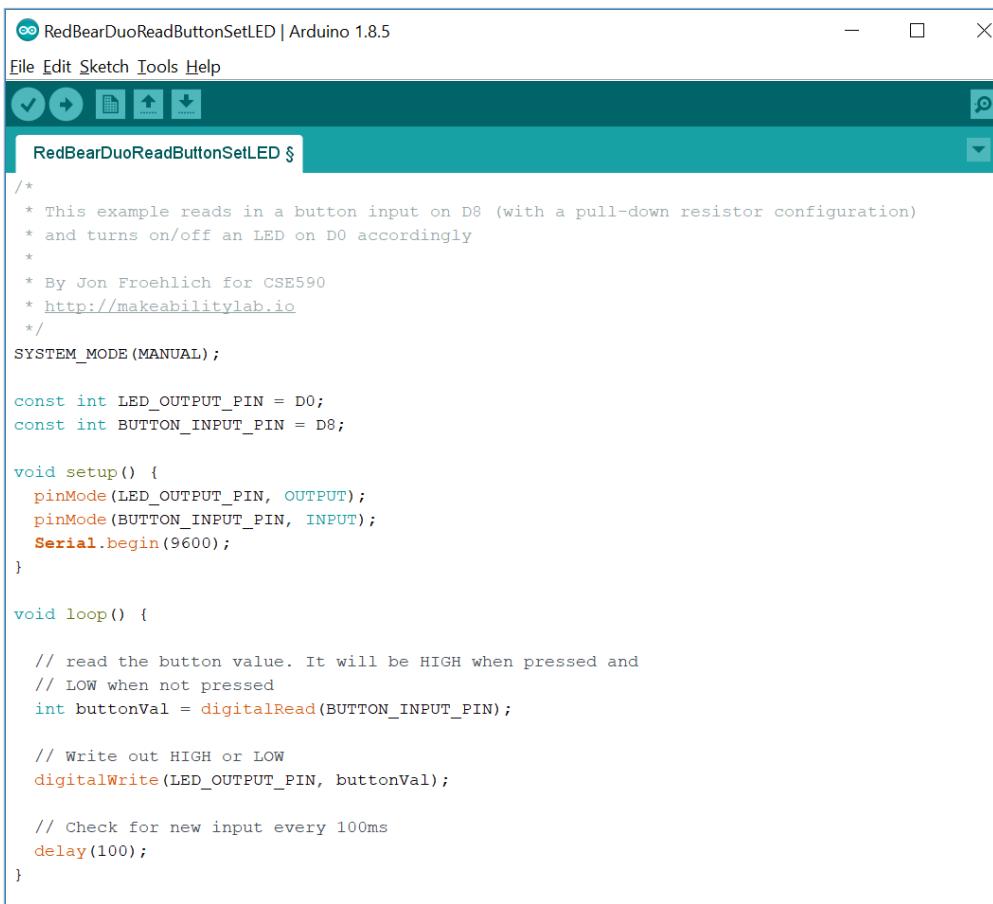Old Code: Read button state and set LED on/off accordingly.
Circuit uses an external pull-down resistor



The screenshot shows the Arduino IDE interface with the title bar "RedBearDuoReadButtonSetLED | Arduino 1.8.5". The code editor contains the following code:

```
/*
 * This example reads in a button input on D8 (with a pull-down resistor configuration)
 * and turns on/off an LED on D0 accordingly
 *
 * By Jon Froehlich for CSE590
 * http://makeabilitylab.io
 */
SYSTEM_MODE(MANUAL);

const int LED_OUTPUT_PIN = D0;
const int BUTTON_INPUT_PIN = D8;

void setup() {
    pinMode(LED_OUTPUT_PIN, OUTPUT);
    pinMode(BUTTON_INPUT_PIN, INPUT);
    Serial.begin(9600);
}

void loop() {

    // read the button value. It will be HIGH when pressed and
    // LOW when not pressed
    int buttonVal = digitalRead(BUTTON_INPUT_PIN);


    // Write out HIGH or LOW
    digitalWrite(LED_OUTPUT_PIN, buttonVal);

    // Check for new input every 100ms
    delay(100);
}
```

The code is identical to the one shown in the second screenshot, except for the line highlighted in the callout box.

<https://github.com/jonfroehlich/CSE590Sp2018/tree/master/L05-Arduino/RedBearDuoReadButtonSetLED>

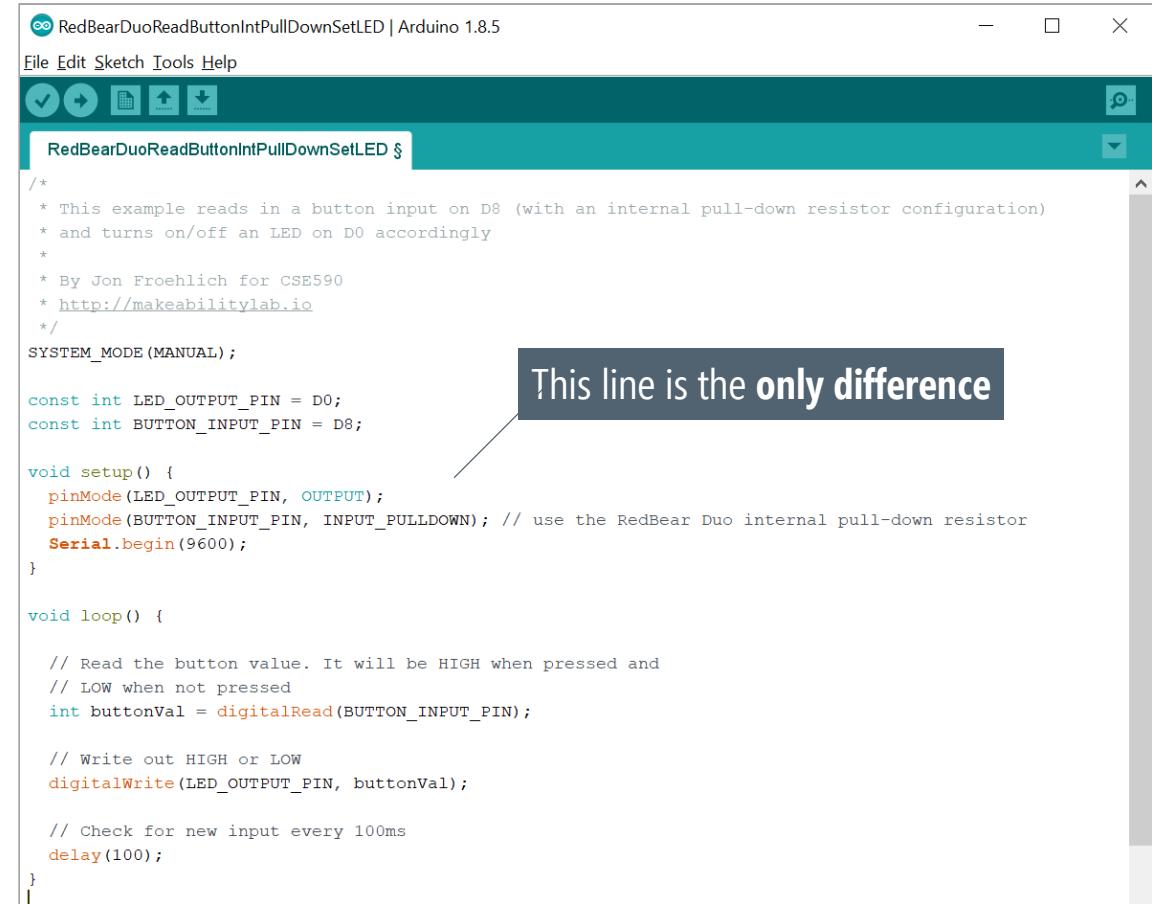New Code: Read button state and set LED on/off accordingly.
Circuit uses an internal pull-down resistor.



The screenshot shows the Arduino IDE interface with the title bar "RedBearDuoReadButtonIntPullDownSetLED | Arduino 1.8.5". The code editor contains the following code:

```
/*
 * This example reads in a button input on D8 (with an internal pull-down resistor configuration)
 * and turns on/off an LED on D0 accordingly
 *
 * By Jon Froehlich for CSE590
 * http://makeabilitylab.io
 */
SYSTEM_MODE(MANUAL);

const int LED_OUTPUT_PIN = D0;
const int BUTTON_INPUT_PIN = D8;

void setup() {
    pinMode(LED_OUTPUT_PIN, OUTPUT);
    pinMode(BUTTON_INPUT_PIN, INPUT_PULLDOWN); // use the RedBear Duo internal pull-down resistor
    Serial.begin(9600);
}

void loop() {

    // Read the button value. It will be HIGH when pressed and
    // LOW when not pressed
    int buttonVal = digitalRead(BUTTON_INPUT_PIN);

    // Write out HIGH or LOW
    digitalWrite(LED_OUTPUT_PIN, buttonVal);

    // Check for new input every 100ms
    delay(100);
}
```



A callout box with the text "This line is the only difference" points to the line "pinMode(BUTTON_INPUT_PIN, INPUT_PULLDOWN);".

<https://github.com/jonfroehlich/CSE590Sp2018/tree/master/L05-Arduino/RedBearDuoReadButtonSetLED>

DIGITAL INPUT

RUN THE PROGRAM

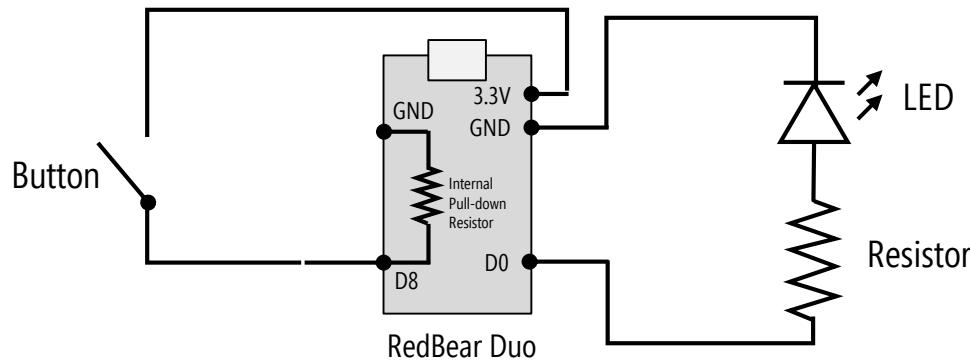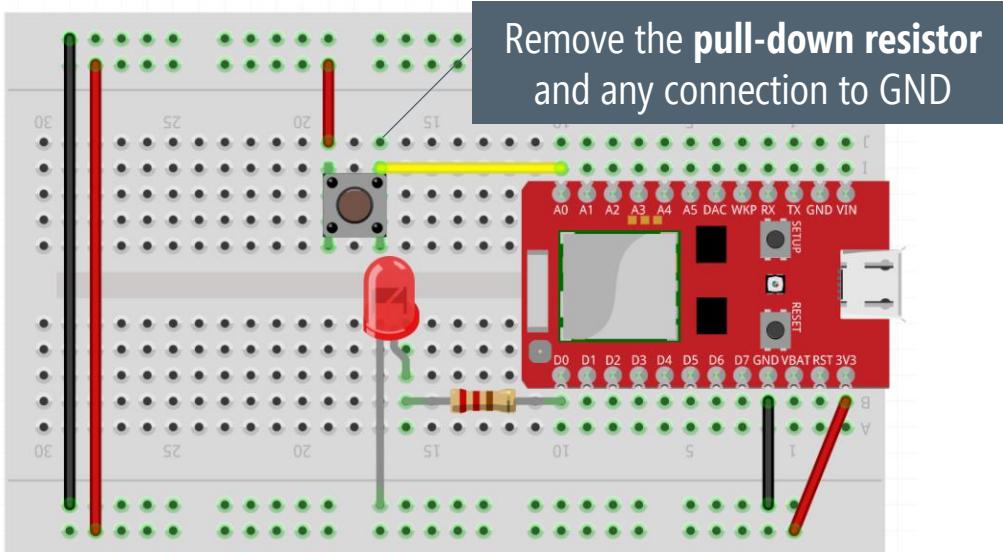New Circuit: Control LED via a button & internal pull-down resistor



New Code: Read button state and set LED on/off accordingly.
Circuit uses an internal pull-down resistor.

RedBearDuoReadButtonIntPullDownSetLED | Arduino 1.8.5

```
/*
 * This example reads in a button input on D8 (with an internal pull-down resistor configuration)
 * and turns on/off an LED on D0 accordingly
 *
 * By Jon Froehlich for CSE590
 * http://makeabilitylab.io
 */
SYSTEM_MODE(MANUAL);

const int LED_OUTPUT_PIN = D0;
const int BUTTON_INPUT_PIN = D8;

void setup() {
  pinMode(LED_OUTPUT_PIN, OUTPUT);
  pinMode(BUTTON_INPUT_PIN, INPUT_PULLDOWN); // use the RedBear Duo internal pull-down resistor
  Serial.begin(9600);
}

void loop() {

  // Read the button value. It will be HIGH when pressed and
  // LOW when not pressed
  int buttonVal = digitalRead(BUTTON_INPUT_PIN);


  // Write out HIGH or LOW
  digitalWrite(LED_OUTPUT_PIN, buttonVal);

  // Check for new input every 100ms
  delay(100);
}
```

This is the only difference


The screenshot shows the Arduino IDE with the sketch "RedBearDuoReadButtonIntPullDownSetLED" open. The code is identical to the previous one, except for the line `pinMode(BUTTON_INPUT_PIN, INPUT_PULLDOWN);` which is highlighted in red. A callout box with a black border and white text reads: "This is the only difference".
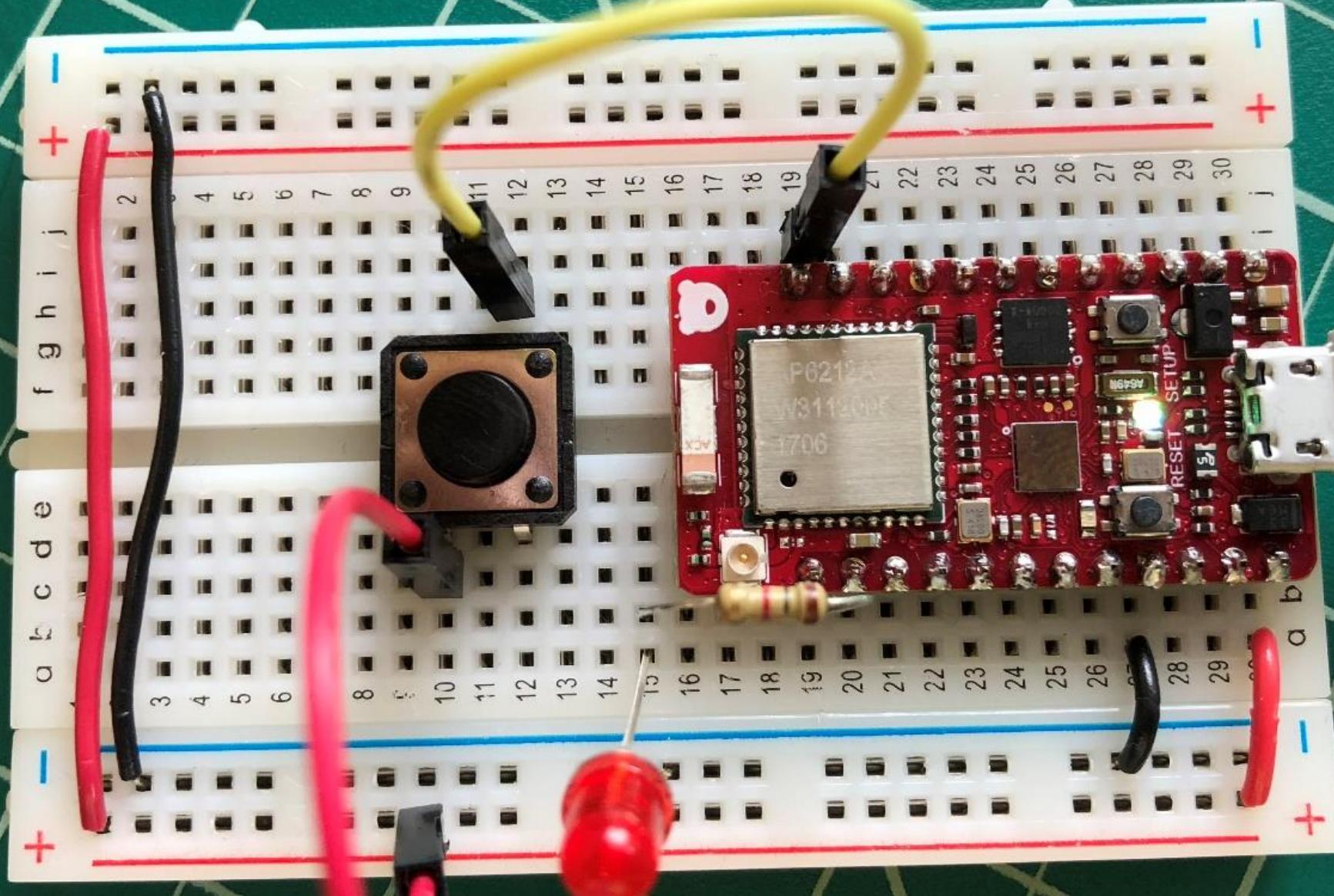
<https://github.com/jonfroehlich/CSE590Sp2018/tree/master/L05-Arduino/RedBearDuoReadButtonSetLED>




DIGITAL INPUT

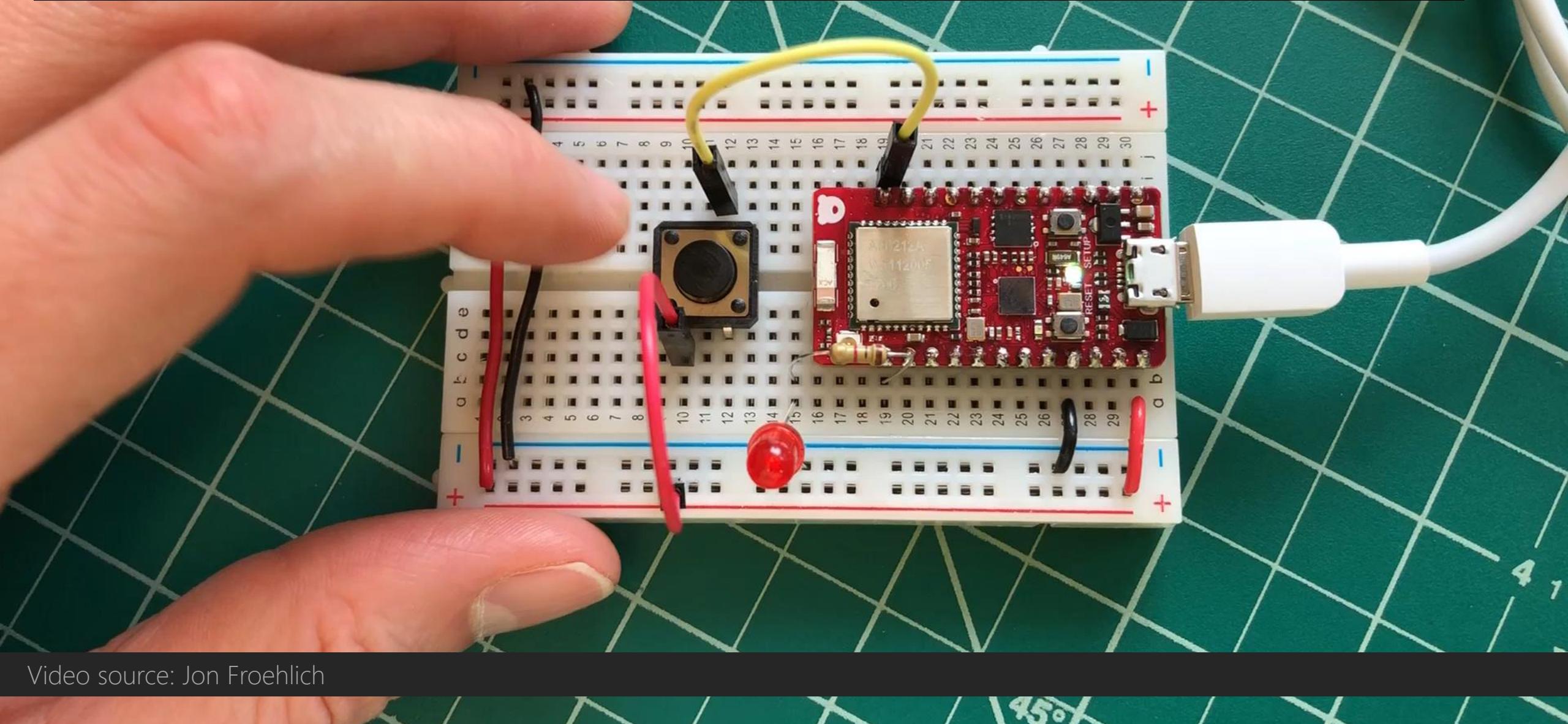DEMONSTRATION OF BUTTON WITH INTERNAL PULL-DOWN RESISTOR




Video source: Jon Froehlich

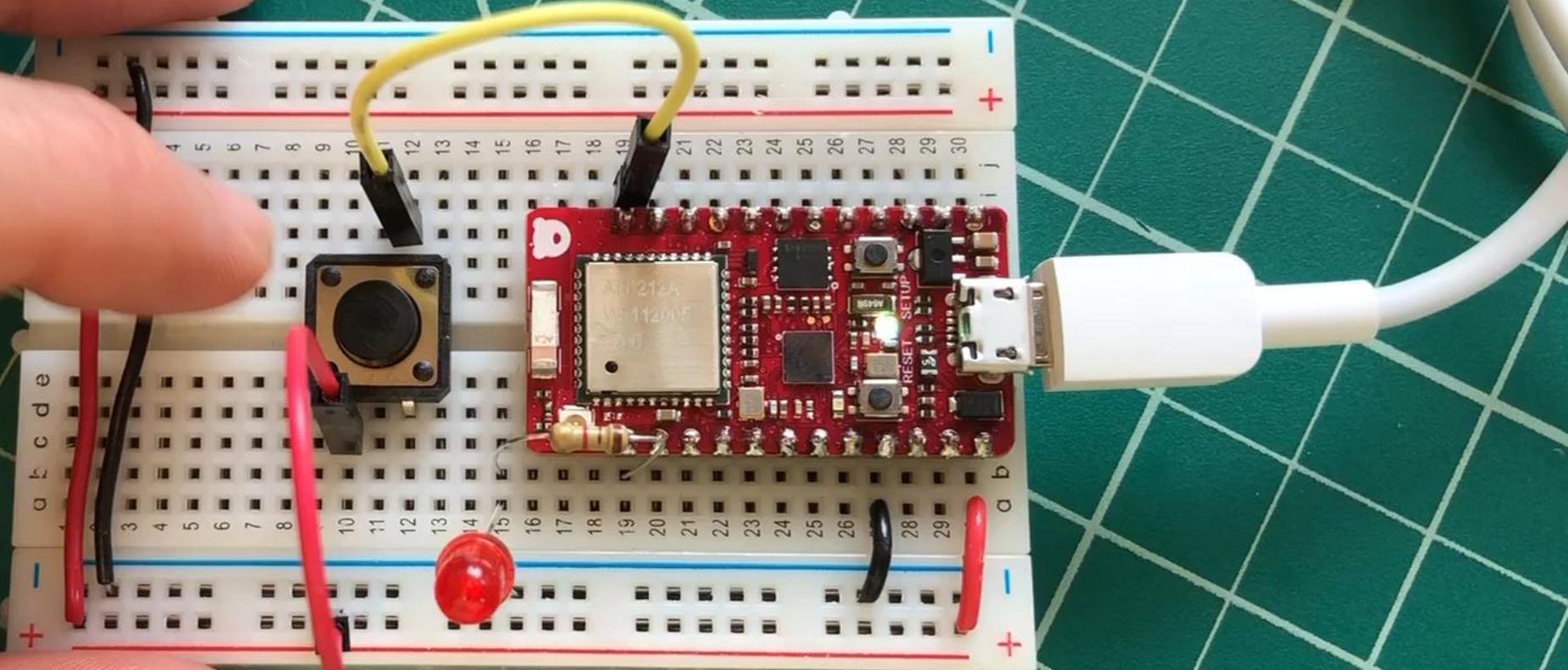

EXPERIMENTING WITH INTERNAL & EXTERNAL PULL-UP AND PULL-DOWN RESISTORS

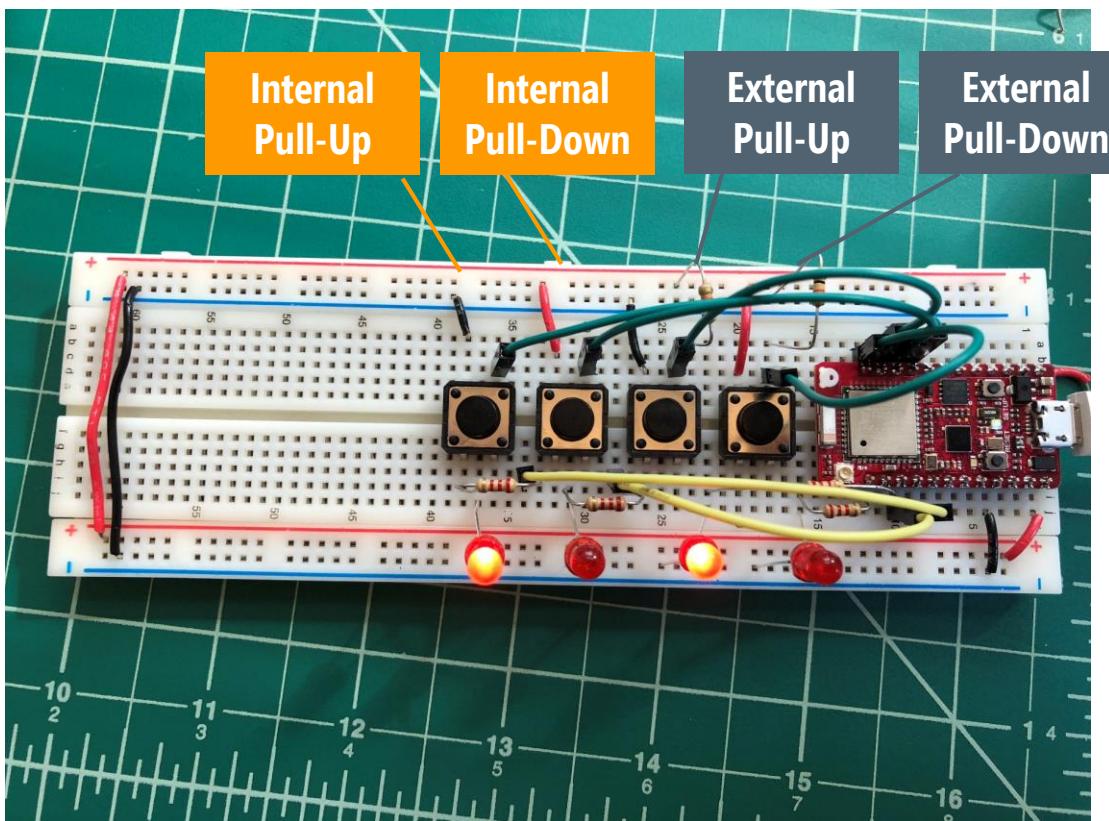Circuit: In left-to-right order of buttons: internal pull-up resistor, internal pull-down resistor, external pull-up, & external pull-down



Code: Demonstrates differences between using internal and external pull-up and pull-down resistors

```
RedBearDuoButtonPullUpAndDown | Arduino 1.8.5
File Edit Sketch Tools Help
RedBearDuoButtonPullUpAndDown
SYSTEM_MODE(MANUAL);

const int LED0_OUTPUT_PIN = D0;
const int LED1_OUTPUT_PIN = D1;
const int LED2_OUTPUT_PIN = D2;
const int LED3_OUTPUT_PIN = D3;

const int BUTTON_EXTPULLDOWN_INPUT_PIN = D8;
const int BUTTON_EXTPULLUP_INPUT_PIN = D9;
const int BUTTON_INTPULLDOWN_INPUT_PIN = D10;
const int BUTTON_INTPULLUP_INPUT_PIN = D11;

void setup() {
  pinMode(LED0_OUTPUT_PIN, OUTPUT);
  pinMode(LED1_OUTPUT_PIN, OUTPUT);
  pinMode(LED2_OUTPUT_PIN, OUTPUT);
  pinMode(LED3_OUTPUT_PIN, OUTPUT);

  pinMode(BUTTON_EXTPULLDOWN_INPUT_PIN, INPUT);
  pinMode(BUTTON_EXTPULLUP_INPUT_PIN, INPUT);
  pinMode(BUTTON_INTPULLDOWN_INPUT_PIN, INPUT_PULLDOWN);
  pinMode(BUTTON_INTPULLUP_INPUT_PIN, INPUT_PULLUP);
}

void loop() {

  // Read the button with an external pull-down resistor. The value will be HIGH when
  // pressed and LOW when not pressed
  int buttonExtPullDownVal = digitalRead(BUTTON_EXTPULLDOWN_INPUT_PIN);


  // Read the button with an external pull-up resistor. The value will be LOW
  // when pressed and HIGH when not pressed
  int buttonExtPullUpVal = digitalRead(BUTTON_EXTPULLUP_INPUT_PIN);

  // Read the button with an internal pull-down resistor. The value will be HIGH when
  // pressed and LOW when not pressed
  int buttonIntpulldownVal = digitalRead(BUTTON_INTPULLDOWN_INPUT_PIN);


  // Read the button with an internal pull-up resistor. The value will be LOW
  // when pressed and HIGH when not pressed
  int buttonIntpullupVal = digitalRead(BUTTON_INTPULLUP_INPUT_PIN);
}
```

DIGITAL INPUT

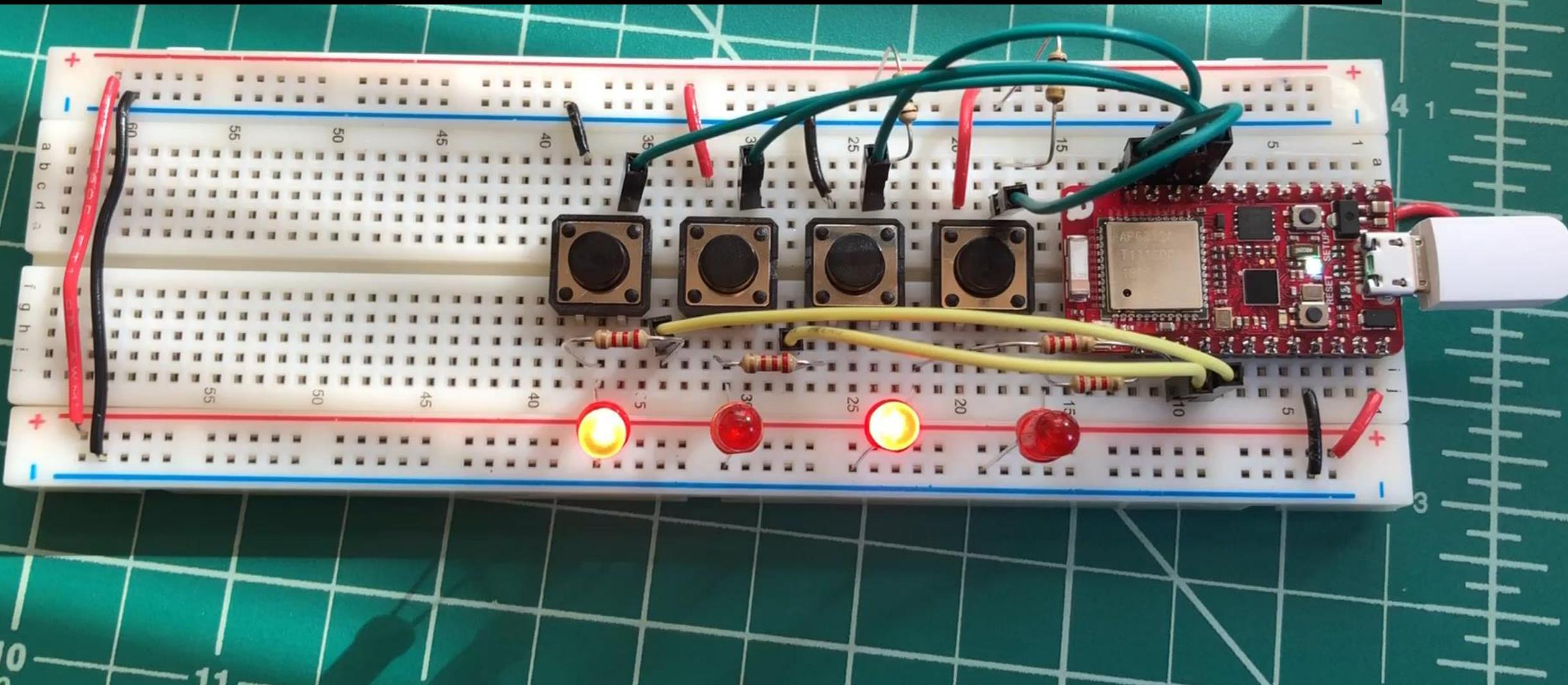DEMONSTRATION OF DIFFERENT PULL-UP & DOWN COMBOS



Video source: Jon Froehlich

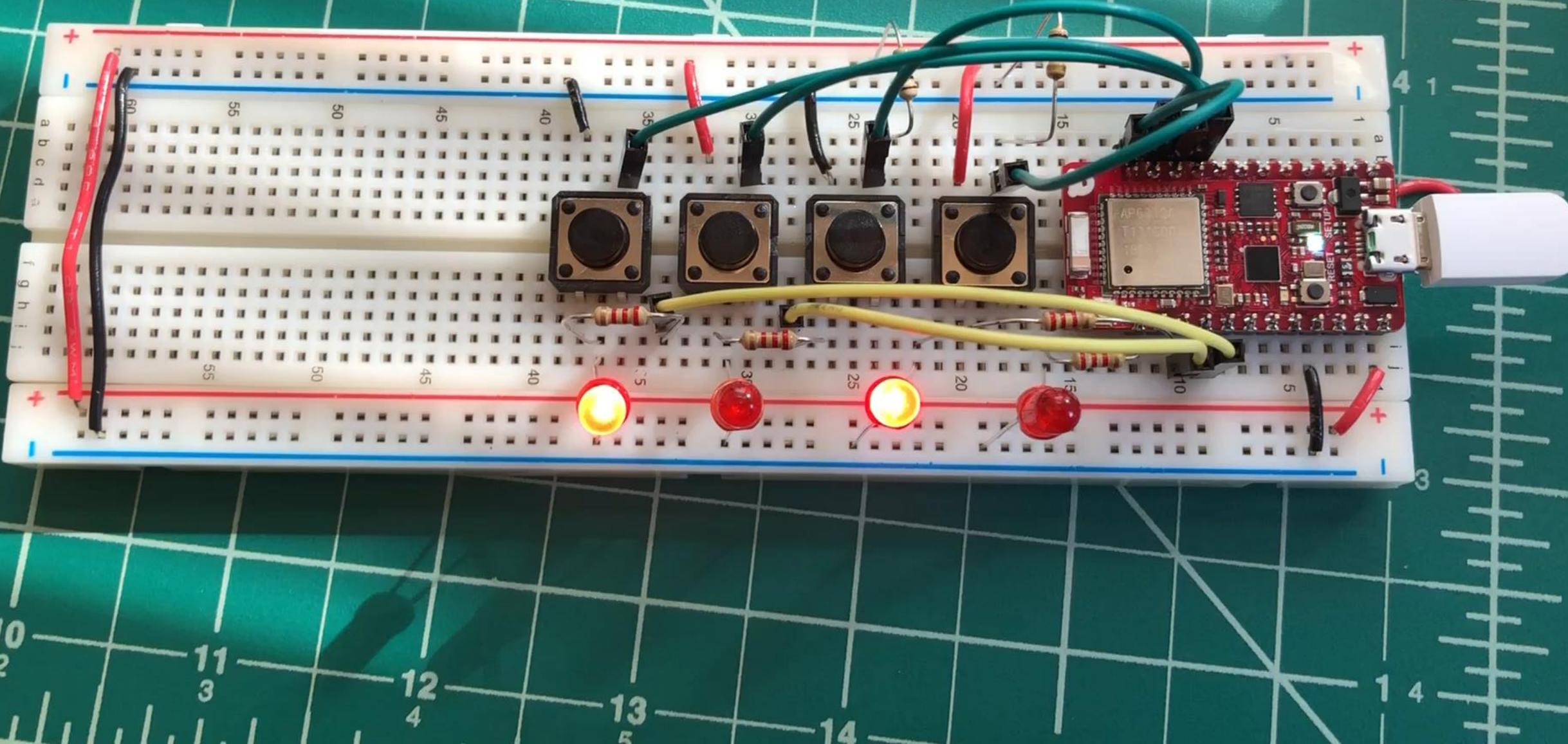

Another issue we have to deal with when working with buttons or switches is **debouncing**—a process of eliminating noise due to transient oscillations from electro-mechanical conductive parts “bouncing” against each other.

DIGI

STOP

H 5.00ms

50.0MSa/s
6.00M pts

D

10.4000000ms

T ↑↓

2.00V

DIGITAL INPUT

CONTACT BOUNCE

Period

Freq

Rise Time

Fall Time

+Width

-Width

BX: = 28.30ms
BY: = 7.440 V
BX-AX: = 28.50ms
BY-AY: = -800.0mV
-- 1/|dX|: = 35.09 Hz

R1

1

CH1

Cursor

Mode

Manual

Select

||

Source

CH1

CursorA

-200.0us

CursorB

28.30ms

CursorAB

↻

Source: <https://youtu.be/jl-rC2FCKo4>

1 2.00V

2 2.00V

3 2.00V

4 5.00V


5

6 5.00V

7 8.00V

DIGITAL INPUT

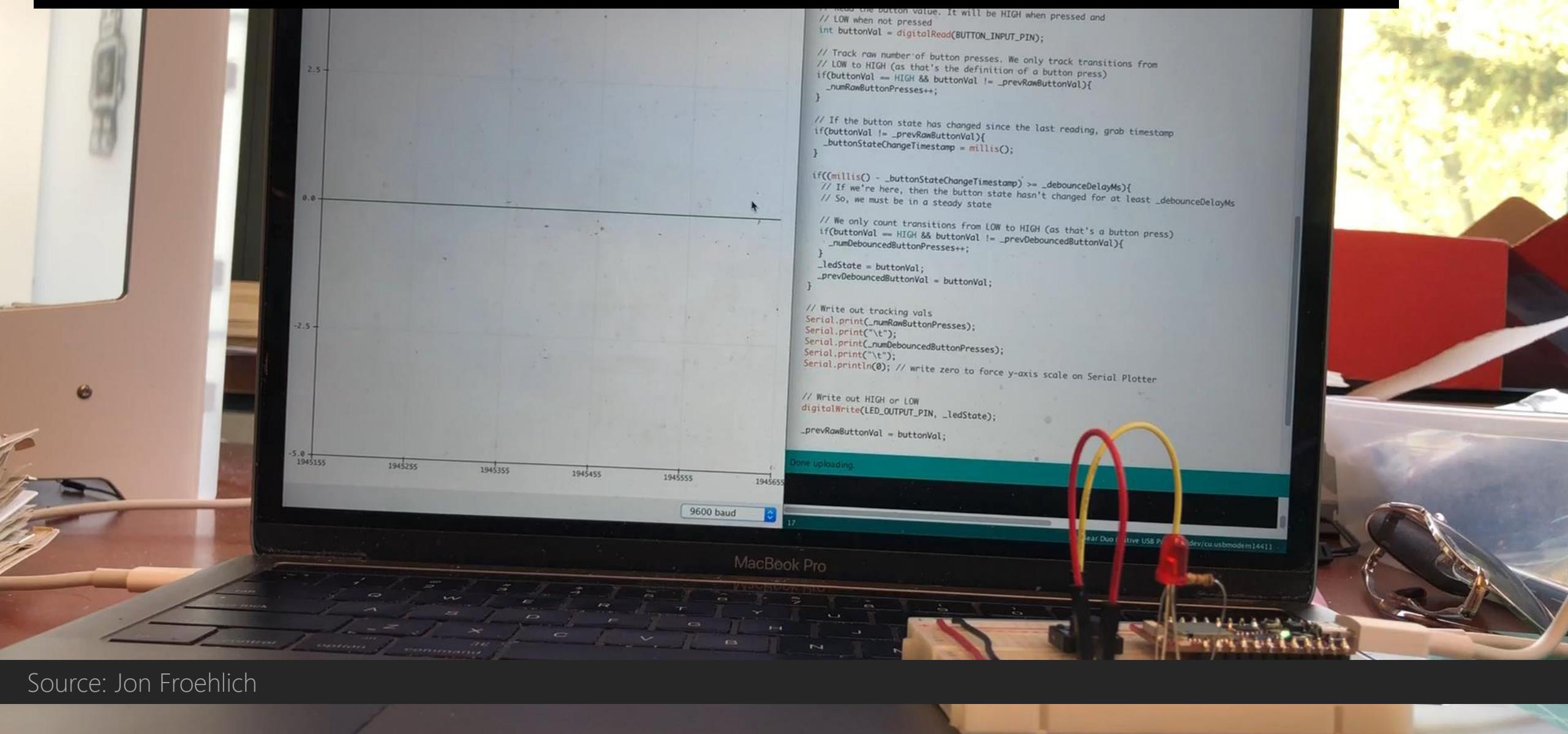EXAMPLE HIGHLIGHTING IMPORTANCE OF DEBOUNCING



Source: Jon Froehlich

```
Arduino
/dev/cu.usbmodem14411
RedBearDuoReadButtonDebounce | Arduino 1.8.5
Thu 9:34 AM May 3
RedBearDuoReadButtonDebounce
void loop() {
    // Read the button value. It will be HIGH when pressed and
    // LOW when not pressed
    int buttonVal = digitalRead(BUTTON_INPUT_PIN);

    // Track raw number of button presses. We only track transitions from
    // LOW to HIGH (as that's the definition of a button press)
    if(buttonVal == HIGH & buttonVal != _prevRawButtonVal){
        _numRawButtonPresses++;
    }

    // If the button state has changed since the last reading, grab timestamp
    if(buttonVal != _prevRawButtonVal){
        _buttonStateChangeTimestamp = millis();
    }

    if((millis() - _buttonStateChangeTimestamp) >= _debounceDelayMs){
        // If we're here, then the button state hasn't changed for at least _debounceDelayMs
        // So, we must be in a steady state

        // We only count transitions from LOW to HIGH (as that's a button press)
        if(buttonVal == HIGH & buttonVal != _prevDebouncedButtonVal){
            _numDebouncedButtonPresses++;
        }
        _ledState = buttonVal;
        _prevDebouncedButtonVal = buttonVal;

        // Write out tracking vals
        Serial.print(_numRawButtonPresses);
        Serial.print("\t");
        Serial.print(_numDebouncedButtonPresses);
        Serial.print("\t");
        Serial.println(0); // write zero to force y-axis scale on Serial Plotter


        // Write out HIGH or LOW
        digitalWrite(LED_OUTPUT_PIN, _ledState);
        _prevRawButtonVal = buttonVal;
    }
}
```

Done uploading.

17

RedBearDuo Native USB Port /dev/cu.usbmodem14411

MacBook Pro

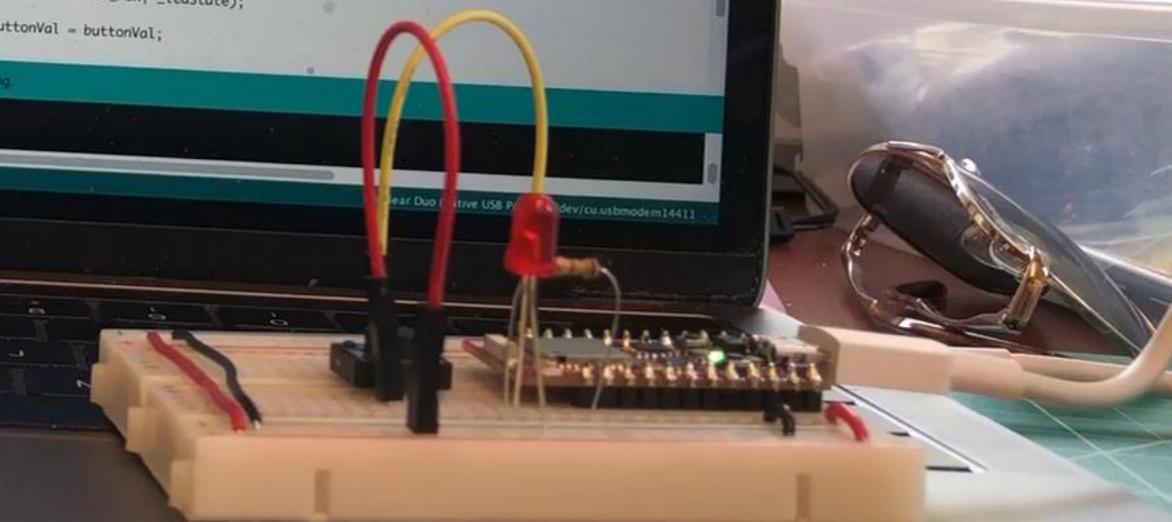

HOW WOULD YOU SOLVE THIS PROBLEM IN SOFTWARE?

With a partner, brainstorm/discuss solutions to this problem


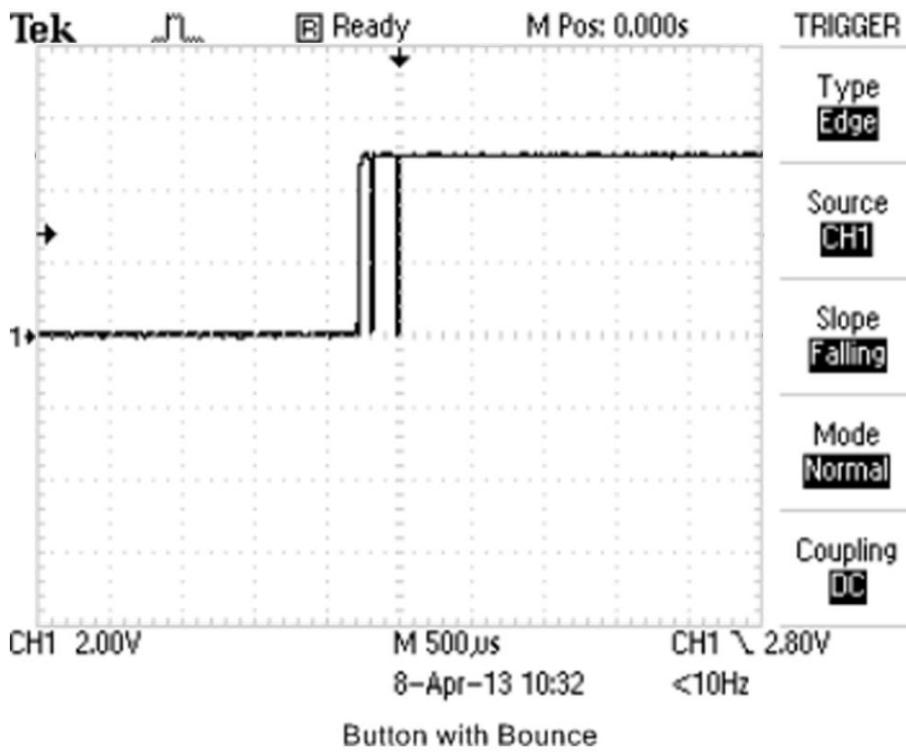


Figure 12-2: Ordinary pushbutton bouncing before settling

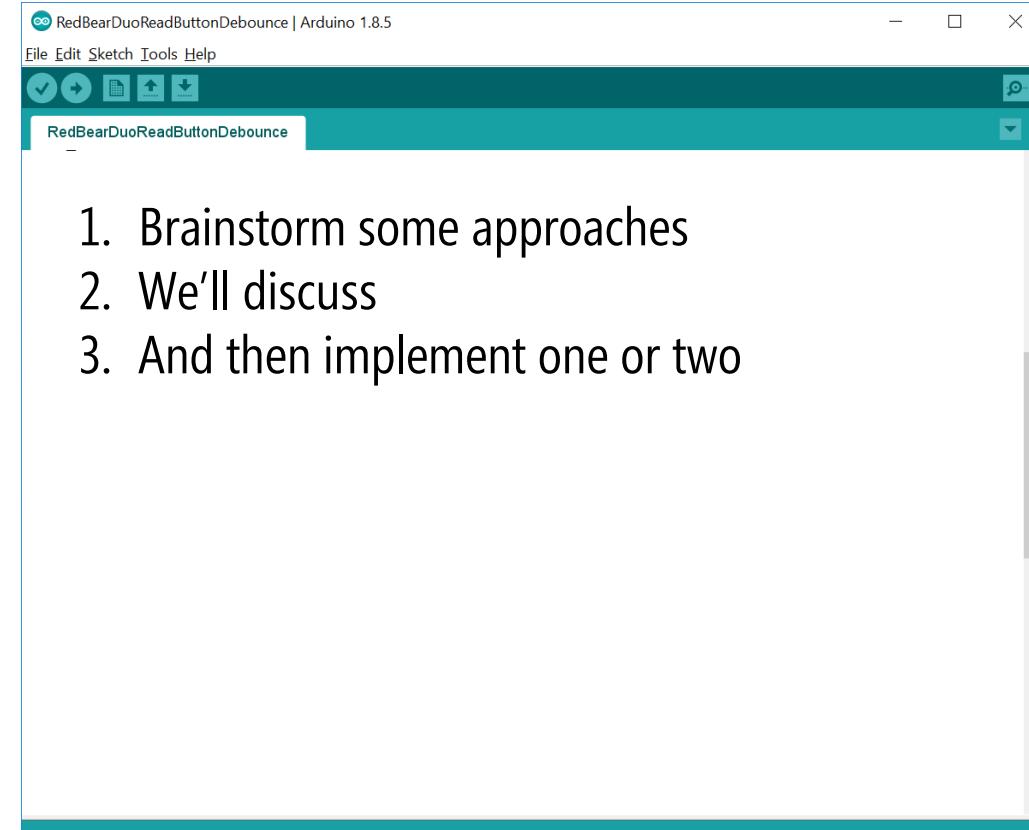


1. Brainstorm some approaches
2. We'll discuss
3. And then implement one or two

DIGITAL INPUT

TWO EXAMPLE SOLUTIONS

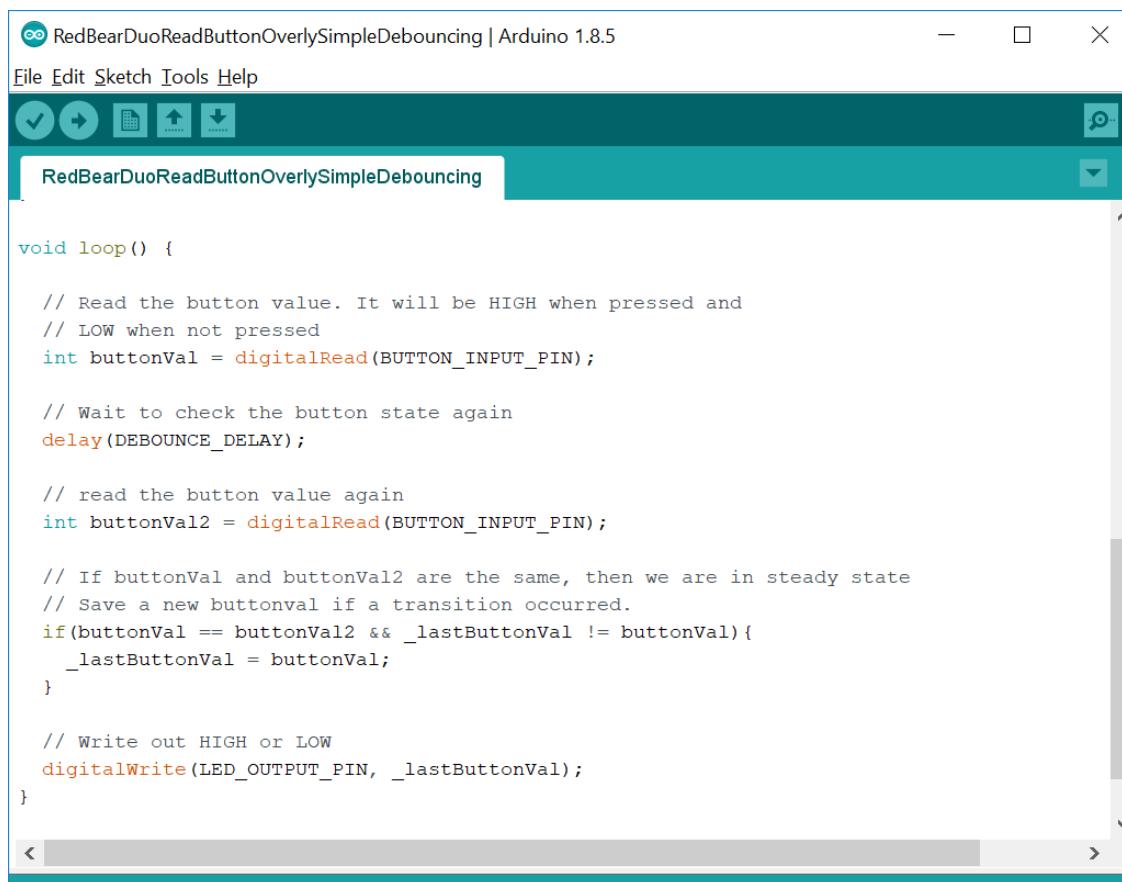Solution 1 (OK): Read button state. Wait via a delay. Read button state again. If both button states agree, then we have steady state.



The screenshot shows the Arduino IDE interface with the title bar "RedBearDuoReadButtonOverlySimpleDebouncing | Arduino 1.8.5". The code in the editor is as follows:

```
RedBearDuoReadButtonOverlySimpleDebouncing

void loop() {
    // Read the button value. It will be HIGH when pressed and
    // LOW when not pressed
    int buttonVal = digitalRead(BUTTON_INPUT_PIN);

    // Wait to check the button state again
    delay(DEBOUNCE_DELAY);


    // read the button value again
    int buttonVal2 = digitalRead(BUTTON_INPUT_PIN);

    // If buttonVal and buttonVal2 are the same, then we are in steady state
    // Save a new buttonval if a transition occurred.
    if(buttonVal == buttonVal2 && _lastButtonVal != buttonVal) {
        _lastButtonVal = buttonVal;
    }

    // Write out HIGH or LOW
    digitalWrite(LED_OUTPUT_PIN, _lastButtonVal);
}
```

<https://github.com/jonfroehlich/CSE590Sp2018/tree/master/L05-Arduino/RedBearDuoReadButtonSimpleDebouncing>

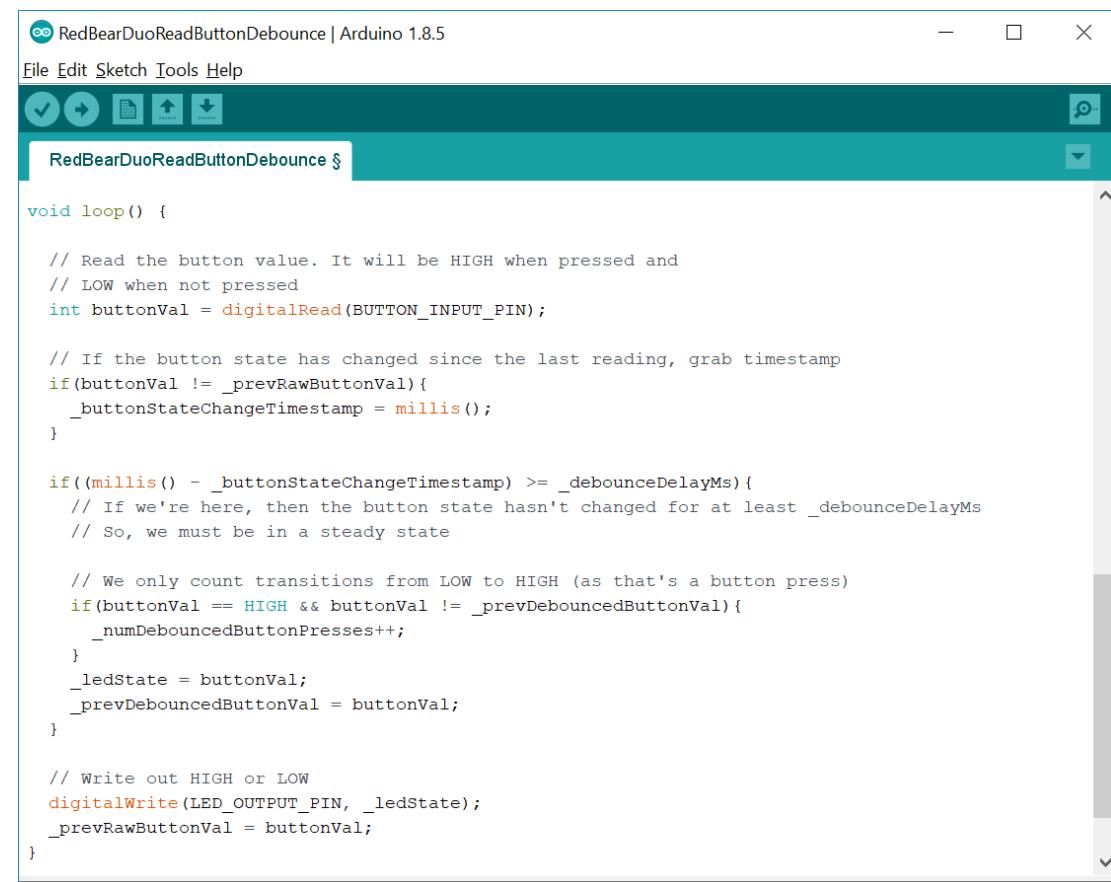Solution 2 (Better!): Similar to Solution 1 but we don't use a delay(). Instead, we track a timestamp. This way, we don't block on a delay() call while we are trying to debounce our signal.



The screenshot shows the Arduino IDE interface with the title bar "RedBearDuoReadButtonDebounce | Arduino 1.8.5". The code in the editor is as follows:

```
RedBearDuoReadButtonDebounce §

void loop() {
    // Read the button value. It will be HIGH when pressed and
    // LOW when not pressed
    int buttonVal = digitalRead(BUTTON_INPUT_PIN);

    // If the button state has changed since the last reading, grab timestamp
    if(buttonVal != _prevRawButtonVal){
        _buttonStateChangeTimestamp = millis();
    }

    if((millis() - _buttonStateChangeTimestamp) >= _debounceDelayMs){
        // If we're here, then the button state hasn't changed for at least _debounceDelayMs
        // So, we must be in a steady state

        // We only count transitions from LOW to HIGH (as that's a button press)
        if(buttonVal == HIGH && buttonVal != _prevDebouncedButtonVal){
            _numDebouncedButtonPresses++;
        }
        _ledState = buttonVal;
        _prevDebouncedButtonVal = buttonVal;
    }

    // Write out HIGH or LOW
    digitalWrite(LED_OUTPUT_PIN, _ledState);
    _prevRawButtonVal = buttonVal;
}
```

<https://github.com/jonfroehlich/CSE590Sp2018/tree/master/L05-Arduino/RedBearDuoReadButtonDebounce>

WORKING WITH SENSORS: LEARNING GOALS

How to use variable **resistive sensors**, including **voltage dividers**,
basic **signal smoothing**

Putting it together: **making a simple theremin**


How to use **buttons**, including **pull-up** and **pull-down resistors**,
and **debouncing**

Working with **interrupts**

Finally, the last concept I want to cover related to input (and most often digital input) is **interrupts**.

INTERRUPTS

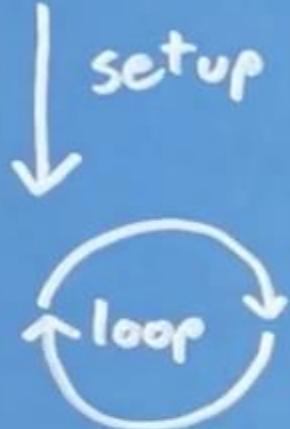WHAT ARE INTERRUPTS? POLLING VS. INTERRUPTS?




```
void setup // Do stuff
{
    void loop () {
        if (button.pushed) {
            // Toggle LED
        }
        // Do other stuff
    }
}
```

Interrupt



```
// Set up
void loop () {
    // Do other stuff
}
ISR () {
    // Toggle LED
}
```

Polling

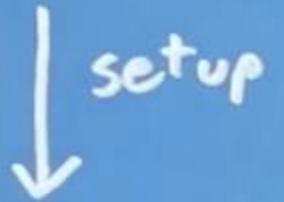

```
void setup() {  
    // Do stuff  
}  
  
void loop() {  
    if (button.pushed()) {  
        // Toggle LED  
    }  
    // Do other stuff  
}
```

Interrupt



```
void setup() {  
    // Do stuff  
    // Set up interrupts  
}  
  
void loop() {  
    // Do other stuff  
}  
  
ISR() {  
    // Toggle LED  
}
```

WHAT ARE INTERRUPTS?

Interrupts allow us to **specify a block of code** (called interrupt service routines or ISRs) that should be **run in response to an event** (e.g., responding to a button press)

Events can be **internal** (like timers) or **external** (like buttons)

Interrupt code **literally interrupts** the **execution** of our main loop

ISRs should be **very fast** and non-blocking

All **variables shared** between an **ISR** and **main** code should be prefixed by **volatile**

attachInterrupt()

Specify a function to call when an external interrupt occurs. pinMode() must be called prior to calling attachInterrupt().

Syntax

```
attachInterrupt(pin, function, mode);
```

```
attachInterrupt(pin, function, mode, priority);
```

Parameters

pin: the input pin number

function: the callback function (must take no parameters and return nothing)

mode: defines how the interrupt should be triggered: CHANGE, RISING, FALLING

priority (optional): defines the priority of the interrupt

Returns

A Boolean indicating whether the ISR was successfully attached (true) or not (false)

Can **interrupts interrupt other interrupts** (*i.e.*, an executing ISR)?
On most Arduino boards, nested interrupts are not enabled.

BASIC EXAMPLE


Setup interrupt to trigger on rising and falling edge of button press

Turn on and off LED accordingly

See: <https://docs.particle.io/reference/firmware/photon/#interrupts>

INTERRUPTS

MY SOLUTION

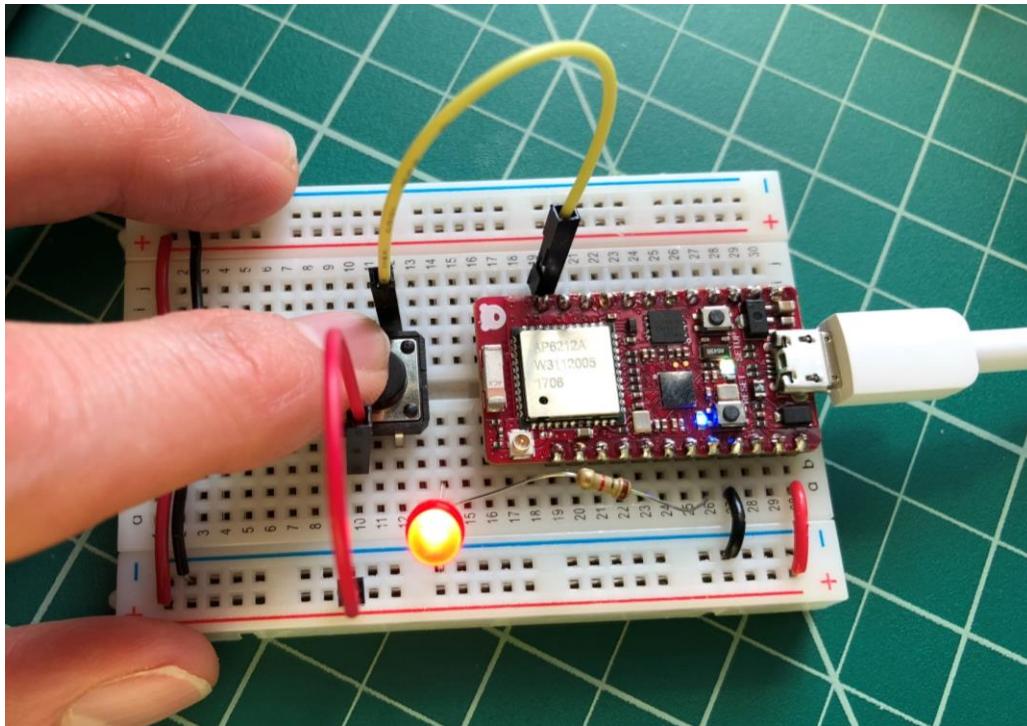

<https://github.com/jonfroehlich/CSE590Sp2018/tree/master/L06-Arduino/RedBearDuoButtonInterrupt>

RedBearDuoButtonInterrupt §

```
/*
 * This example attaches an interrupt to D1, which calls a the function
 * toggle() whenever a RISING or FALLING edge is observed. Toggle turns on/off
 * the internal RedBear Duo LED (which is on D7).
 *
 *
 * By Jon Froehlich for CSE590
 * http://makeabilitylab.io
 *
 * Based on:
 * - https://docs.particle.io/reference/firmware/photon/#interrupts
 * - https://github.com/bjo3rn/idd-examples/blob/master/redbearduo/examples/button\_interrupt.ino
 */
|
SYSTEM_MODE(MANUAL);

// This is the internal LED pin on the Duo
const int LED_OUTPUT_PIN = D7;

// The official Particle Photon documentation states that external interrupts
// should work on all pins except for D0 and A5, see:
// https://docs.particle.io/reference/firmware/photon/#interrupts
const int BUTTON_INPUT_PIN = D8;

void toggle(void); // function declaration for interrupt

void setup() {
    pinMode(LED_OUTPUT_PIN, OUTPUT);
    pinMode(BUTTON_INPUT_PIN, INPUT_PULLDOWN);
    attachInterrupt(BUTTON_INPUT_PIN, toggle, CHANGE); //CHANGE, RISING or FALLING
}

void loop() {
    // intentionally empty
}

void toggle(){
    digitalWrite(LED_OUTPUT_PIN, digitalRead(BUTTON_INPUT_PIN));
}
```

INTERRUPTS

TWO MORE EXAMPLES TO EXPLORE

Interrupt + debouncing example



The screenshot shows the Arduino IDE interface with the title bar "RedBearDuoButtonInterruptWithDebouncing | Arduino 1.8.5". The code editor contains the following C++ code:

```
long _debounceDelay = 50; // the debounce time in ms

// From the Particle Photon documentation:
// "Typically global variables are used to pass data between an ISR and
// the main program. To make sure variables shared between an ISR and the
// main program are updated correctly, declare them as volatile."
// See: https://docs.particle.io/reference/firmware/photon/#interrupts
volatile int _ledState = LOW;

// Function declaration for interrupts
void toggle(void);
void isr(void);

// We will use a software timer to help us debounce.
// See: https://docs.particle.io/reference/firmware/photon/#software-timers
Timer timer(_debounceDelay, toggle, true); // oneshot timer so last param=true

void setup() {
    pinMode(LED_OUTPUT_PIN, OUTPUT);
    pinMode(BUTTON_INPUT_PIN, INPUT_PULLDOWN);

    // Hook up interrupt to button again but this time call the
    // ISR routine, which will start a timer on every rising edge
    // and after a set delay (_debounceDelay), the timer callback
    // is called (which is set to toggle())
    attachInterrupt(BUTTON_INPUT_PIN, isr, CHANGE); //CHANGE, RISING or FALLING
}

void loop() {
    // intentionally empty
}

// Called automatically when a button state change occurs
void isr(){
    noInterrupts(); // temporarily pause the interrupts
    if(digitalRead(BUTTON_INPUT_PIN) == HIGH){
        timer.resetFromISR(); //start or reset timer on every rising edge
    } else {
        timer.stopFromISR(); //stop on falling edge
    }
}
```

<https://github.com/jonfroehlich/CSE590Sp2018/tree/master/L06-Arduino/RedBearDuoButtonInterruptWithDebouncing>

Software timer example



The screenshot shows the Arduino IDE interface with the title bar "RedBearDuoSoftwareTimer | Arduino 1.8.5". The code editor contains the following C++ code:

```
/*
 * IMPORTANT: When working with the RedBear Duo, you must have this line of
 * code at the top of your program. The default state is SYSTEM_MODE(AUTOMATIC);
 * however, this puts the RedBear Duo in a special cloud-based mode that we
 * are not using. For our purposes, set SYSTEM_MODE(SEMI_AUTOMATIC) or
 * SYSTEM_MODE(MANUAL). See https://docs.particle.io/reference/firmware/photon/#system-modes
 */
SYSTEM_MODE(MANUAL);

// This is the internal LED pin on the Duo
const int LED_OUTPUT_PIN = D7;

// From the Particle Photon documentation:
// "Typically global variables are used to pass data between an ISR and
// the main program. To make sure variables shared between an ISR and the
// main program are updated correctly, declare them as volatile."
// See: https://docs.particle.io/reference/firmware/photon/#interrupts
volatile int _ledState = LOW;
volatile int _seconds = 0;

void timer_callback(void); // function declaration for interrupt

Timer _timer(1000, timer_callback);

void setup() {
    pinMode(LED_OUTPUT_PIN, OUTPUT);
    Serial.begin(9600);
    _timer.start();
}

void loop() {
    // intentionally empty
}

// called automatically by software timer
void timer_callback(){
    _ledState = !_ledState;
    digitalWrite(LED_OUTPUT_PIN, _ledState);
    Serial.println(++_seconds);
}
```

<https://github.com/jonfroehlich/CSE590Sp2018/tree/master/L06-Arduino/RedBearDuoSoftwareTimer>

SCHEDULE TODAY: 6:30-9:20

06:30-06:55: Discussion of required reading led by Joe Wandyez

06:55-07:00: Optional discussion led by Abhay Rijhwani ([link](#))

07:00-08:10: Physical Computing 3: Sensors

08:10-08:15: Break

08:15-09:20: Physical Computing 4: Android + Arduino via BLE